BASIC ELECTRICAL AND ELECTRONICS ENGINEERING LECTURE NOTES



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING MALLA REDDY ENGINEERING COLLEGE AUTONOMOUS MAISAMMAGUDA, DULAPALLY– 500014, Hyderabad

SYLLABUS: MODULE I : DC Circuits [09 Periods]

Electrical circuit elements (R, L and C), voltage and current sources, Kirchhoff's current and voltage laws - Series, parallel, series-parallel, star-to-delta and delta-to-star transformationanalysis of simple circuits with dc excitation. Superposition, Thevenin's and Maximum Power Transfer Theorems with DC excitation.

MODULE II: AC Circuits 09 Periods]

Representation of sinusoidal waveforms, peak and rms values, phasor representation, real power, reactive power, apparent power, power factor. Analysis of single-phase ac circuits consisting of R, L, C, RL, RC, RLC combinations (series and parallel).

MODULE III: Introduction to Electrical Machines [10 Periods]

A: DC Machines : Construction & Principle of Operation of DC Generators – E.M.F Equation. Principle of operation DC Motors – Back E.M.F. - Torque equation – Brake Test - Characteristics.

B: AC Machines: Construction and Principle of operation of Transformer- EMF Equation. Construction and Principle of Operation of 3 Phase Induction Motors - Brake test on 3-Phase Induction Motor – Applications

MODULE IV: P-N Junction Diode [10 Periods]

A: P-N Junction Diode: Diode equation, Energy Band diagram, Volt-Ampere characteristics, Temperature dependence, Ideal versus practical, Static and dynami resistances, Equivalent circuit, Diffusion and Transition Capacitances. Zener diode operation, Zener diode as voltage regulator.

B: Rectifiers : P-N junction as a rectifier - Half Wave Rectifier, Ripple Factor – Full Wave Rectifier, Bridge Rectifier.

C: Filters - Inductor Filters, Capacitor Filters, L- section Filters, π - section Filters.

MODULE V : BJT and Junction Field Effect Transistor (JFET) [10 Periods]

A:Bipolar Junction Transistor (BJT): Construction, Principle of Operation, Symbol, Amplifying Action, Common Emitter, Common Base and CommonCollector configurations and Input-Output Characteristics, Comparison of CE, CB and CC configurations

B: Junction Field Effect Transistor and MOSFET: Construction, Principle ofOperation, Symbol, Pinch-Off Voltage, Volt-Ampere Characteristic, Comparisonof BJT and FET.

TEXT BOOKS

1. M.Surya Kalavathi, Ramana Pilla, Ch. Srinivasa Rao, Gulinindala Suresh, "Basic Electrical and Electronics Engineering", S.Chand and CompanyLimited, New Delhi, 1st Edition, 2017.

2. R.L.Boylestad and Louis Nashlesky, "Electronic Devices & Circuit Theory", Pearson Education, 2007.

REFERENCES

1. V.K. Mehtha and Rohit Mehta, "Principles of Electrical Engineering and Electronics", S.Chand & Co., 2009.

2. Jacob Milliman, Christos C. Halkias, Satyabrata Jit (2011), "ElectronicDevices and Circuits", 3 rd edition, Tata McGraw Hill, New Delhi.

3. Thomas L. Floyd and R. P. Jain, "Digital Fundamentals", Pearson Education, 2009.

4. David A. Bell, "Electronic Devices and Circuits", Oxford University Press, 2008.

De State + explain Maximum power transfer théorem:-Scalement:- It states lact monimum power is delivered From a Source to a load when the load subsistence is equal to the source resistance.

<u>Steps to be Zollowed in Maximum power Trensfor Heorem</u>: (1) Remore the variable land subsistence RL (2) Find the open circuit Voltage V_H across points A & B (3) Find the gressistance R_H as seen Zem prints A & B (4) Find the gressistance R_H as seen Zem prints A & B (5) Find the gressistance R_L for maximum power transfor. R_L=R_{TH}

(3) Find the max. power.

TH ZZ RE=RA $\overline{\mathcal{H}} = \frac{\mathcal{H}}{\mathcal{R}_{H} + \mathcal{R}_{L}} = \frac{\mathcal{H}}{2\mathcal{R}_{H}}$ $P_{min} = I_L^2 R_L = \frac{44^2}{4R_{ii}^2} \times R_{TH}$ $P_{mcsx} = \frac{V_{H}^{2}}{4R_{H}}$ Arrent for

10 Dezine currente, Volkage: + power Current: The glow of free electrons through the andultor is called Electrical current. Formulas: - (1) Constant current (2): (1) Instantonicas current p1, buy I= & Domp 64 25. -> The Unit of Current is Ampere - It is denoted by I (F) i(t).

1-2-01 Electrical Voltage:--> Statement: The potential disterence (P.D) between two prints is the energy neguired to more me couling of charge from one print to the other A Constante voltaise; V= 1 (volk) (1) Remain 928 contenors voltage v(t): - OK)= du > The Unit of Voltage is Volt >> It is denoted by V (a) 20(t). Flectrical power:-A Statement: The male out which work is done in an electric circuit is called Electric power. Electric power = Lorradone in electric Gravit C1, D3, F7, F8,69, H2 F8,69, H5. > Formulas: horses - $P = \frac{\lambda}{t} \qquad (:: v = \frac{\lambda}{d})$ $= \frac{v \cdot a}{t} \qquad (:: v = \frac{\lambda}{d})$ 二、是 (::1=是) (a) P = V. 7 wate CERTER - She glive Product is Colle. (b) P = I²R Walt (U and) and for C P= V2/ Late I the unit of power is halt -21 The > It is denoted by P @ Pt. i vi

While Shortes on Resistance, Inductionce & Capillance: 1-3 Resistance :--> Statement: Which opposis the glaw of electrons through the conductor. -> 965 Symbol is M -> 945 Unit is Ohm (-2) -> It is Abbrevialed as R @ IL. Resistance q a conductor depends upon (i) Resistance of a conductor depends upon the material (i) Resistance of a conductor is directly propositional to it's length. Ral->D (iii) Resistance q a conductor is inversity proportional to its area of cross-section RXA-0 (iv) Refistance depends on the temporature of the conductor From equ () + 2 RX 2019 15-R=PL 2 all' Co Nº Com Where P= specific presistence of the conductor. is all is the present of the advertise Carpent D 14 14 1 The section of the section of the section in the section

In du Chance: > Statement: It is property of a loid that opposes any Change in the current glowing through it. -> Formula:- V= L dI volt -> The unit of Inductionic is Henry (H) > It symbol is _00_ -> It is denoted by LODL. Factors on Which Inductionce depends upon: (i) It is directly proportional to be square of the number of tools (iii) It is inversely proportional to the neluclance of the magnetic path. path. Lant -> Scalement :- The property of a material which opposes set change in Volkoge cans be material is finan as capacitance -> a' stored in a capacitor is directly propositional to the potential. sifference acom the capacitor. Qar RECV 1 cz Q) forad. 7965 unit is Farad (F) -> 245 symbol is ++- @; -> 24 is Abbrevialed as c; Factors in slich capacitances depends upon (1) 96 is directly proportional to the Area goldes. TCAA-O (ii) 95 is inverse propositional to the kickness of the d'elatric. Kx - D (iii) The greater the relative permittinity of the insulctions material,

the sun 3 the gadindness number of (ju) Rquivalent Induction is layed to the liv) Recipized of the aquivalent lie [K72 dit late to the sum of the liv) Recipized of the sum of t (iii) that charge is equal to the sum of vigherest individual Charges on capacitalise and the (ir) Reciproved a life's equivale Trolume Crayes on T. Bard to the 23 cgud to the 24 children of the 1 control of the 2 trainder (copacitive of the 1 children of the 1 copacitive different volkege drop i.e V=442442 11-1 11 11 11 11 (ii) Applied voltage agrido the Sone of (iii) Applied voltage agrido the Sum of a le differente voltage doop i.e. (i) Eisterene pulsede hare her individual (i) Eigterent Indiverses hare wer (ii) Eisterent valuere conscience hare war Valuere da da (i) vollage across early lepainter (1) same valeagents across all parts of (1) charge on each capacitors is (1) Same corrects place (2) cane (2) Same correct places (20005) all prode (1) Charge on each capacher & Capacitance in parallel in sovis Puildre C21.01 2015 CLINKI 5 diffuence 50 (iii) Total currat equals to the sun of (ii) they wreads and he sun of (ii) sifferent Inductorse here then Individual corrects is <u>ISAINAL</u> individ correct. Tradindual corrects is <u>ISAINALA</u> individ corrects (ir) Recipred a less equivalent (iii) Toral correct equals to the sun presence is equal to the sun of the different Individual correct recipred of the individual Russiment. 77 parallet ductore in series: 13 4 4 3k 9 9 de g f 5 Inductions 5 34 34 71 ijy Equivalente nebistonies is equal to (ii) siffware subscore have we (1) Same voltage acts across all Revisionie in parallel:-Ĺ Fr + Fr + Fr ----20) Rebarre in sories: ports of the Circuit. てく > Q 4 4

62) Derivation for A-Y and Y-A Trens zorondien: 1-6





The above two tiraits are equal 12 their respective rebistances from the terminals AB, BC & CA are equal.

Consider be star-connected Circuit in FigD, le Menstance from the terminals AB, BC +CA respectively are

RAB(Y)= RA+RS RBC(Y) = RB+RC RCA(Y) = RC+RA

Similarly In the A-connected Nework in Fig(2), the subistance sun gen the terminals AB, BC+ CA nesp. are

 $R_{AB(\Delta)} = R_1 / (R_1 + R_3)$ $= \frac{R_1(R_2+R_3)}{R_1+R_2+R_3}$

 $R_{BC}(\Delta) = R_3 / (R_1 + R_2)$ $= \frac{R_3(R_1+R_2)}{R_1+R_2+R_3}$ RCA(D) = R2//(RITR3) $= \frac{R_2(R_1+R_3)}{R_1+R_2+R_3}$

Delta. Star:

NOW, if we equale the redistances of star & Delta Circuits, we set $R_{A}+R_{B}=\frac{R_{1}(R_{2}+R_{3})}{D}$

Ritheth3

R, tR2tR3

RB+RC = R3(RitR2) - 2

RetRA = Re(Riths) - (3)

Scanned with CamScanner

ve set 1-7 From equation D, Q X3, (n - (2) + (3))RATRS-BB-BC+RC+RA $= \frac{R_{1} + R_{2} + R_{1}R_{3}}{R_{1} + R_{2} + R_{3}} - \frac{R_{3}R_{1} - R_{3}R_{2}}{R_{1} + R_{2} + R_{3}} + \frac{R_{2}R_{1} + R_{2}R_{3}}{R_{1} + R_{2} + R_{3}}$ 2RA = RIR2+ RIR3-RIR, -RIR2+ R2RI+ R/R3 RI+R2+R2 $2R_{A} = \frac{2R_{1}K_{2}}{2R_{1}K_{2}}$ $\frac{R_{i} + R_{2} + R_{3}}{R_{i} + R_{2} + R_{3}} \rightarrow (2)$ $fimilarly: R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3} \rightarrow G \quad R_c = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \rightarrow G$ STAR- Alla:-From equation (3), (5) \$6 We can get (h) x (3 + (3 x (3 + (3 x (3))) $R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A} = \frac{R_{1}^{2}R_{2}R_{3} + R_{3}^{2}R_{1}R_{2} + R_{2}^{2}R_{1}R_{3}}{(R_{1} + R_{2} + R_{3})^{2}}$ $RARS + RBRC + RCRA = \frac{R_1 R_2 R_3 (R_1 + R_2 + R_3)}{(R_1 + R_2 + R_3)^2}$ $R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A} = \frac{R_{1}R_{2}R_{3}}{(R_{1} + R_{2} + R_{3})}$ winded knowpone by RA

RARB+RBRC+RCRA RA K1K2K3 R1+R2+R3 -8 RA RA = RIRZ RytRztRz $\frac{R_A R_B + R_B R_C + R_C R_A}{R_A} = \frac{B_1 R_2 R_3}{R_1 + R_2 + R_3}$ $\frac{R_{A}R_{B}+R_{B}R_{C}+R_{C}R_{A}}{R_{A}} = R_{3}$ fimilarly we can prove that, R2= RARS+RBRC+RCRA R_B RARB + RBRC+RCRA RC R,

2) State & explain KCL & KVL Ans: Kirchoff's current Law: Statement: The algebraic sum of the corrects meeting at a junction in an electrical linuit is zero. Sign convention: - currents floring tonneds a junction point are assumed to be the while converts glowing away from a junction prime assumed to be negative. Explanation: - Consider your conductors camping currents I, J2, J3 + Iy and multing at a print 0, as shown in Fig@. 92 We take the signs of worrents glowing towards print 0' as positive, then worrents glowing away gum point of will be assigned -ve sign. Thus applying KCL to be Junchim O $[I_1 + I_4 - I_2 - I_3 = 0]$ Kirchoff's Voltage Law:-Statement: In any closed circuit, the algebraic Sum of all the electromotive (emps) and voltage drops across circuit elements Sign convention (i) A = B = FE + E + E = CEM2 Sign convention-E + E + E $\begin{array}{c} \textcircled{I} \\ \textcircled{I} \\ = \frac{1}{2} R \end{array} = -IR \cdot \frac{+}{12R} \cdot \frac{1}{7} \left(\begin{array}{c} V_0 / kase \ drop \\ Sign \ conversion \\ \end{array} \right)$ 92 lere currente direction has not given in the Cirtuit, then explanation: follow this method. $E_{1} - IR_{1} - IR_{1} - IR_{2} - E_{2} - IR_{3} = 0$ $E_{1} = 1$ $E_{1} = 1$ $E_{1} = 1$ $E_{2} = 1$ $E_{1} = 1$ $E_{2} = 1$ $E_{2} = 1$ $E_{1} = 1$ $E_{2} = 1$ $E_{1} = 1$ $E_{2} = 1$ $E_{1} = 1$ $E_{2} = 1$ $E_{$

(10) While short notes on Mesh & Nodel Analysis Sol Mesh analylis: > Alpending upon the Sources, We have to select the mesh malysis + nodal analysis. of more no. of Voltage Sources, Use mesh analysis (B) if there are more no. of current sources used nodel analysis. > Mesh analysis is applicable only for planar network. For non-planar Circuit mesh analysis is not applicable In henoral, 92 We have 's' number of branches & N number of nodes including the suprements mode then, the number of linearly Independent mesh equations M - P (144) M = B - (N + 1)-> procedure to sire the problem got a given Neberk; () First Step is to check whether the circuit is planal (ii) Second Step, Select closed bop of currents called mash (ii) Finally writing KVL equations in terms of unknown mesh currents + solving them leads to ginal Solution Solution. - KVL is used you Mesh analysis. NODAL Analysis > In genoral in 'N' node circuit one of the modes is choosen as superence node @ datum node, (hen it is possible to while (N-1) would equations, by assuming (N-1) made voltage. (N-1) node voltage. > The mode voltage is the voltage of a given mode with suspect to one particular mode called the Reference mode which we assume at zero potential. -> KCL is applied to Nodal analysis.

1-11/00 State and explain Superposition Iteolem:-Statement: - In a linear alwork containing more than me Source of emp the resultant current in any branch is the algebraic sum of currents that would be produced by each emp acting alone, all other sources of emp being neplaced manutile by their respective internal rubistances. Explanation: TO Show that this statement is true, Consider the Circuit Shown in fig. The Total Circuit sussicurce Ry is given by - M. Ry= RitkptRy Where Rp = R2Rs/R2+R3 TEI Step1: Consider that emp E, is acting alone by Reptung 62 Lith a shirt Cirwit. Ru ; current due to E, alone, $I_{i} = \frac{E_{i}}{R_{i} t R_{p} t R_{y}}$ Step2: NON consider back emp Ez is alling alone by repting E, Lith a Short Circuit -: current due to Ez alme, $I_2 = \frac{E_2}{R_1 + R_p + R_y}$ <u>Step3:</u>- When both sources are alling at a time, then the resultante currente is I = Algebraic sum q Z, + Z2 $= \left(\frac{E_{i}}{R_{i}+R_{p}+R_{y}}\right) + \left(\frac{-E_{2}}{R_{i}+R_{p}+R_{y}}\right)$ $= \frac{C_1}{R_1 + R_p + R_y}$ E2 RitRptoly JAN GARAN TRA. CKE



1-13 Explain Types of Sources:-There are basically two types of Energy Sources. sley are (1) Independent sources (2) Acpendent Source. (1) Independent sources: Again Independent Sources are divided into 600. They are. (a) Independent Voltage Source. (b) Indipendent current source. (a) Independent vollage Source: There are too types & Independent Volkage Jource, They are (1) I deal vollage Source. (i) practical voltage Source. i practical voltage bowree. U) Ideal Voltage Source:-> A practical voltage source does. not have a unstant treminal -> I deal vollage source is Voltage. As the salpher current (3) the defined as the energy source Load current increases be terminal Luich gives constant vollage across its terminals irrespative vollage: Will drop. of the current drown through Kee ils terminals. a Vit is NIL > But practically every vollege source 7 An Ideal Vollage Source is has small galand gubisterse is one whose internal refistance Sham in Sovies with the Ideal Volte, Source I is represented by Be. is zero. (lse=0). -> By Appry Krl to Loop VS - Iche = VE=0 V2 = V5 - ZRSe

(b) Independent correct source: I.C.S are of two types, 1-14 (1) practical current Source (1) Ideal current source > A practical current source does not have a constant oneput current, As the 7 Ideal current bowrice is the voltage across its terminal voltage Source With gives constant at increases, be onlyne correct decreas. Us terminals putive of the Voltage appearing across its > But practically every currente Source has high increal rubistance, sharm Eliminals. in parallel high current source & it is represented by Rsh. I-13 卫 Logz 5=3 An Ideal current source is NL one whose Internal resistance By apply KCL at node 'A' is infinity , Rehad ふ-み-え=0 Iz= 3-34 (2) Dependent Sources: - A dependente voltage @ current source is one which depends on some other quantity in the circuits which may be either a voltage & correct. -> A dypendent source is nepresented by a diamond shape symbol as sham in Fig. correct Source Voltage Source -> There are your possible dependent Sources. (i) Voltage - dependent voltage Sowers (i) current-dependent voltage bources Voltage- dependent current bource (iii) current- dependent current source.

MESH Analysis 1-15 () calculate the current in each resister white someran any themas the Stoffer for given circuit. 4-22 E2-2 1 40V Applying KrL to Loop 2:-Set Applying Krz to Loop 1:-40-412- (7, +72)2=0 35-37,-2(7,+72)=0 40-472-27,-272=0 35-37, -27, -272=0 40-27,-672=0 35-57-272=0 27, +6 72=40 51,+21,-35=0 $I_1 + 3I_2 = 20 \rightarrow (2)$ 5I+2I, =35 ->(1) 1 40V 35V 5 21 - 40V Solving I, & Iz by crosseis sule:- $\begin{bmatrix} 5 & 2 \\ 1 & 3 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \\ 2 & - \end{bmatrix} = \begin{bmatrix} 3 \\ 2 \\ 2 \\ 0 \end{bmatrix}$ $\Delta = \begin{bmatrix} 5 & 2 \\ 1 & 3 \end{bmatrix} = 15 - 2 = 13 \quad ; \quad \Delta_1 = \begin{bmatrix} 35 & 2 \\ 20 & 3 \end{bmatrix} = 105 - \frac{2}{40} = 65$ $\Delta_2 = \begin{bmatrix} 5 & 35 \\ 1 & 20 \end{bmatrix} = 65$ $I_2 = \frac{\Delta_1}{\Delta} = SAmp$, $I_2 = \frac{\Delta_2}{\Delta} = SAmp$ ". The current thorough 3-2 is I, = 5 Amp Correct Wrough 4-2 is I2 = Sponp 2-2 is (3+2) = 10 pmp. The 11 11 .11 grate &

(12) By Using Super position The overn, and the current in 1-16 4-2 42. 3-2 M__M \$2-2 - 40r. 35V Sil Step 1: - operate Lith one vollage Source i.e. 35 volts and other source i.e. 40 volts is replaced by their internal refistance [Short Grait 3-2 4-2 M__M 2 volkage source i.e v=0] 820 = 3 + 2/14 $= 3 + \left(\frac{2xy}{2ty}\right) = 3 + \left(\frac{8}{6}\right) = 4.3$ $I = \frac{35}{4.3} = 8.1 \text{ Amp.}$ $: I_1 = I \times \frac{2}{4+2} = 8.1 \times \frac{2}{6} = 2.7 \text{ Amp} / .$ Step 2 :- operate Lith one volkage Bource i.e 40 volk + etta Source i.e 35 volts is replaced by their included rubstances [Short Cixuit EM ME of voltage Borre i.e r=0] - 40V $I = \frac{V}{Reg}$ Reg = 4 series with 3/12. = 4 + 3/2 $= \frac{4}{3} + \left(\frac{3\times2}{3+2}\right) = 4 + \left(\frac{6}{5}\right) = 5 \cdot 2 - 2$ I - · I = 40 = 7.7 mp. Step3: - When two sources operating at a time i.e 40+352 then the sussitiont current in 4-2 is []-] = 7.7-2.7 = 50mp. 40-

and the shi iv) Recipiocal of Equivalent resistance is equal to the sum of the reciprocals of individual resistances. 1-17 $\frac{1}{R_{eq}} = \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ Current Division Rule in Panallel Circuit: When two resistons are I W connected in farallel, then the currents I, and Iz are $\frac{1}{12}$ R₂ given by 木I YI. (1) $\hat{I}_1 = \hat{I} \times \frac{R_2}{R_1 + R_2}$ $(11) \hat{1}_{2} = \hat{1} \times \frac{R_{1}}{R_{1}+R_{2}}$ Opposite resultance Individual Current = Total Current x Total resistance Equivalent Circuit (Equivalent Resistance): Problem: 1 Find the equivalent resistance between the terminals - A and B for the given circuit.



Problem: 2

Determine the equivalent resistance between the terminals - A and B for the given circuit.



1-19





$$\frac{1}{2} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2}$$

$$\vec{R}_{eq} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$

-> 3. and 2. are in series

1-22

$$R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A} = \frac{R_{1}^{2}R_{2}R_{3}}{(R_{1+R}+R_{2}+R_{3})^{2}} + \frac{R_{1}R_{2}R_{3}^{2}}{(R_{1+R}+R_{3}+R_{3})^{2}} + \frac{R_{1}R_{2}R_{3}}{(R_{1+R}+R_{3}+R_{3})^{2}}$$

$$R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A} = \frac{R_{1}R_{2}R_{3}}{R_{1}+R_{2}+R_{3}}$$

$$Fividing by R_{A} \text{ on both sides}$$

$$R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A} = \frac{R_{1}R_{2}R_{3}}{R_{1}+R_{2}+R_{3}}$$

$$\frac{F_{1}+R_{2}+R_{3}}{R_{A}} = \frac{R_{1}R_{2}R_{3}}{R_{1}+R_{2}+R_{3}} \times \frac{R_{1}+R_{2}+R_{3}}{R_{1}R_{2}}$$

$$\frac{R_{3}}{R_{3}} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{3}}$$

$$\frac{S_{1}m_{1}av_{1}y}{R_{2}},$$

$$R_{2} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$R_{1} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$I = 23$$

$$\frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$R_{1} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$R_{1} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$R_{2} = \frac{R_{A}R_{B} + R_{B}R_{C} + R_{C}R_{A}}{R_{2}}$$

$$R_{1} = \frac{R_{A}R_{B} + R_{B}R_{A}}{R_{2}}$$

$$R_{2} = \frac{R_{A}R_{A} + R_{B}R_{A}}{R_{2}}$$

$$R_{2} = \frac{R_{A}R_{A} + R_{B}R_{A}}{R_{2}}$$

$$R_{2}$$

$$\begin{aligned} R_{A}P_{B} + R_{B}P_{c} + P_{c}P_{A} &= \frac{P_{1}^{2}P_{2}P_{3}}{(P_{1}+P_{2}+P_{3})^{2}} + \frac{P_{1}P_{2}P_{3}^{2}}{(P_{1}+P_{2}+P_{3})^{2}} + \frac{P_{1}P_{2}^{2}P_{3}}{(P_{1}+P_{2}+P_{3})^{2}} \\ R_{A}P_{B} + R_{B}P_{c} + P_{c}P_{A} &= \frac{P_{1}P_{2}R_{3}}{(P_{1}+P_{2}+P_{3})^{2}} \\ R_{A}P_{B} + R_{B}P_{c} + P_{c}P_{A} &= \frac{P_{1}P_{2}R_{3}}{P_{1}+P_{2}+R_{3}} \\ F_{1}+P_{2}+R_{3} \\ F_{1}+P_{2}+R_{3} \\ F_{1}+P_{2}+R_{3} \\ F_{1}+P_{2}+R_{3} \\ R_{A} \\ &= \frac{P_{A}P_{B} + R_{B}P_{c} + P_{c}P_{A}}{R_{A}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{A}} \\ R_{B} \\ R_{1} &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{A}R_{B} + R_{B}P_{c} + R_{c}P_{A}}{R_{c}} \\ &= \frac{P_{1}-2.3}{P_{0}} \\ R_{A} \\ &= \frac{P_{1}-2.3}{P_{$$







Tep one, 4, 2, 2, 2, and 4, 2, are in
$$\Delta$$

Apply $\Delta - Y$ technique,
 $R_{A} = \frac{4x^{2}}{4t^{2}+4t} = 0.82$
 $R_{B} = \frac{2x4}{4t^{2}+4t} = 0.82$
 $R_{E} = \frac{4x4}{4t^{2}+4t} = 0.82$
 $R_{E} = \frac{4x4}{4t^{2}+4t} = 1.62$
 $Apply \Delta - Y$ dichnique.
 $R_{D} = \frac{4x4}{4t^{2}+4t} = 1.62$
 $R_{F} = \frac{4x2}{10} = 0.82$
 $R_{F} = \frac{4x2}{10} = 0.82$
 $R_{F} = \frac{4x2}{4t^{2}+4t} = 0.82$
 $R_{F} = 0.82$





Sume voltage acts across all pusts of the circuit.
Different inductors have their individual currents.
Total current is equal to sum of the individual currents i.e.,

$$I = T_1 + T_2 + T_3$$

(i) The suciprocal of equivalent inductance is equal to sum of suciprocal of individual inductances i.e., $\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$
Equivalent Inductance:
Trecedure of equivalent inductance = Procedure of equivalent inductance.
I = 30
filly
Mesh Analysis:
(top method)
Troblem:I
Find the current through the resistors and voltage drop across each survitor for the network shown in figure.





Broblem : 2

In the circuit shown in figure, determine the avoients in each of the batteries.



 $\Delta = \begin{vmatrix} 23 & -11 \\ 11 & -13 \end{vmatrix} = -270$

$$\Delta_{1} = \begin{vmatrix} -10 & -11 \\ -20 & -19 \end{vmatrix} = -50 \qquad [-39]$$

$$\Delta_{2} = \begin{vmatrix} 23 & -10 \\ 11 & -20 \end{vmatrix} = -350$$

$$T_{1} = \frac{\Delta_{1}}{\Delta} = \frac{-50}{-290} = 0.18 \text{ Amp}$$

$$T_{2} = -\frac{350}{-290} = 1.29 \text{ Amp}$$

$$T_{2} = -\frac{350}{-290} = 1.29 \text{ Amp}$$

$$T_{2} = 1.29 \text{ Amp}$$

$$T_{1} = current through 20V is $f_{2} - f_{1} = 1.29 - 0.18 = 1.11 \text{ Am}$

$$T_{1} = current through 10V is T_{2} = 1.29 \text{ Amp}.$$
UNded Analysis:-
$$(Tunction method)$$
Roblem:1
Rod the current through the given revisions:

$$T_{1} = \frac{A0}{T_{1}} = \frac{A0}{T_{2}} = \frac{10}{T_{2}} = 0.18 \text{ Amp}$$

$$T_{1} = \frac{A0}{T_{1}} = \frac{100}{T_{2}} = 1.29 \text{ Amp}.$$

$$T_{1} = \frac{A0}{T_{1}} = \frac{100}{T_{2}} = 1.29 \text{ Amp}.$$

$$T_{2} = 1.29 \text{ Amp}.$$

$$T_{1} = \frac{A0}{T_{2}} = 1.29 \text{ Amp}.$$

$$T_{2} = 1.29 \text{ Amp}.$$

$$T_{3} = 1.29 \text{ Amp}.$$

$$T_{4} = \frac{A0}{T_{1}} = \frac{100}{T_{2}} = 1.29 \text{ Amp}.$$

$$T_{5} = 1.29 \text{ Amp}.$$

$$T_{7} = \frac{A0}{T_{1}} = \frac{100}{T_{1}} = 1.29 \text{ Amp}.$$

$$T_{1} = \frac{100}{T_{1}} = 1.29 \text{ Amp}.$$

$$T_{1} = \frac{100}{T_{1}} = 1.29 \text{ Amp}.$$

$$T_{1} = \frac{100}{T_{1}} = 1.29 \text{ Amp}.$$

$$T_{2} = 1.29 \text{ Amp}.$$

$$T_{3} = 1.29 \text{ Amp}.$$

$$T_{4} = 1.29 \text{ Amp}.$$

$$T_{5} = 1.29 \text{ Amp}.$$

$$T_{7} = 1.29 \text{ Amp}.$$$$
$$\begin{aligned} \widehat{T}_{1} + \widehat{T}_{2} + \widehat{T}_{3} &= 0 \\ & \left(\frac{V_{1} - 25 \cdot 0}{3}\right) + \left(\frac{V_{1} - 0}{2}\right) + \left(\frac{V_{1} - u0 - 0}{4}\right) = 0 \\ & \frac{V_{1} - 140 + 6V_{1} + 3V_{1} - 120}{12} = 0 \\ & \frac{4V_{1} - 140 + 6V_{1} + 3V_{1} - 120}{12} = 0 \\ & \frac{4V_{1} + 6V_{1} + 3V_{1} - 360 = 0}{12} \\ & \frac{4V_{1} + 6V_{1} + 3V_{1} - 360 = 0}{13} \\ & \frac{1}{13} \\ & \frac{V_{1} - 360}{13} \\ & \frac{V_{1} = 00V}{13} \\ & \frac{V_{1} = 00V \\ & \frac{V_{1} = 00V}{3} \\ & \frac{S}{3} = \frac{-15}{3} \\ & \frac{S}{3} = \frac{-15}{3} \\ & \frac{S}{3} = -5 \text{Amp} \\ & \frac{40 - u0}{4} \\ & = \frac{40 - u0}{4} \\ & = -\frac{20}{4} \\ & = -5 \text{Amp} \\ & \therefore \text{ The current through } 2 \text{ as is } T_{2} = V_{1} - \frac{0}{2} = \frac{20}{2} = 0 \text{ Amp} \end{aligned}$$



Applying KCL at node B:- $-I_{1} - I_{2} - I_{3} = 0$ $I_{1} + I_{2} + I_{3} = 0$ $\left(\frac{V_{2} - 10 - V_{3}}{1} + \left(\frac{V_{2} - 0}{1}\right) + \left(\frac{V_{2} + 5 - V_{1}}{1}\right) = 0$ $V_{2} - 10 - V_{3} + V_{2} + V_{2} + 5 - V_{1} = 0$ $-V_{1} + 3V_{2} - V_{3} - 5 = 0$ $V_{1} - 3V_{2} + V_{3} = -5$ (1)

$$\begin{aligned} & \text{Applying } KCL \text{ at node } A:\\ & -\Gamma_3 - \Gamma_4 - \Gamma_5 = 0 \\ & \Gamma_3 + \Gamma_4 + \Gamma_5 = 0 \\ & \left(\frac{V_1 - 5 - V_2}{1}\right) + \left(\frac{V_1 - 0}{1}\right) + \left(\frac{V_1 + 5 - V_3}{1}\right) = 0 \\ & V_1 - 5 - V_2 + V_1 + V_1 + 5 - V_3 = 0 \\ & 3V_1 - V_2 - V_3 = 0 - @ \end{aligned} \\ \end{aligned}$$

$$\begin{aligned} & \text{Applying } \text{ KCL at node } C:- \\ & -\Gamma_1 - \Gamma_5 - \Gamma_6 = 0 \\ & \Gamma_1 + \Gamma_5 + \Gamma_6 = 0 \\ & \left(\frac{V_3 + 10 - V_2}{1}\right) + \left(\frac{V_3 - 5 - V_1}{1}\right) + \left(\frac{V_3 - 0}{1}\right) = 0 \\ & V_3 + 10 - V_2 + V_3 - 5 - V_1 + V_3 = 0 \\ & -V_1 - V_2 + 3V_3 + 5 = 0 \\ & V_1 + V_2 - 3V_3 - 5 = 0 \\ & V_1 + V_2 - 3V_3 - 5 = 0 \\ & V_1 + V_2 - 3V_3 = 5 - 0 \end{aligned}$$

$$\begin{aligned} & \text{Solving } @, @ \text{ and } @ \text{ using cramely surflue} \\ & \left(\frac{1 - 3}{3} + \frac{1}{1}\right) \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 0 \\ 5 \end{bmatrix} \\ & \text{A} = \begin{bmatrix} 1 & -3 & 1 \\ 3 & -1 & -1 \\ 1 & 1 & -3 \end{bmatrix} = 1 (8+1) + 3(-9+1) + 1(8+1) \end{aligned}$$

$$A_{1} = \begin{bmatrix} 1 & 1 & 1 \\ n & 1 & 1 \\ n & 1 & 1 \end{bmatrix} = h(h) + h(-1) + h(h) + 1(h) = \begin{bmatrix} 1 & 2 \\ n & 1 & 1 \\ 1 & n & 1 \end{bmatrix}$$

$$= D$$

$$A_{1} = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & 1 & n \end{bmatrix} = 1(h) + h(-1) + 1(1n) + 1(1n)$$



 $\hat{I}_{T} = \frac{35}{4.3} = 8.13 \text{ Amp}$ 1-40 $\underline{\hat{1}}_{2} = \underline{\hat{1}}_{T} \times \frac{4}{4+2}$ I2 = 5.42 Amp Step: 2 Operate with one source ire 40V and remaining sources (i-e., 35 V source) are replaced by their internal resistance (short circuit, r=0) JT, 91=0 V= Ir Req $\hat{I}_{T}' = \frac{v}{R_{eq}}$ Req = 3|12+4 $=\frac{3\times 2}{3+2}+4$ $=\frac{6}{5}+4$ Reg = 5.2.2 $\hat{1}T' = \frac{40}{5.2} = 7.69 \text{ Amp}$ $\hat{1}_{2} = \hat{1}_{1} \times \frac{3}{5} = 4.614 \text{ Amp}$





Step: 2.
Operating one course i.e., 5Amp eurunt source
and armaining sources (i.e., 35 V voltage source)
ore p suplaced by their internal restistance
(short circuit,
$$s_{1=0}$$
).
 $T_1 = 5$ Amp
 $T_2 = 5T_1 \times \frac{3}{5}$
 $= 5 \times \frac{3}{5}$
 $T_2' = 3$ Amp
Step: 3
When two sources acting at a time, therethe
current through 22 is
 $T_2' = 3$ Amp
 $T_2 = \frac{3}{5}$
 $T_2' = \frac{3}{5}$
 $T_2' = 3$ Amp
 $T_2' = \frac{3}{5}$
 $T_2' = \frac{3}{5}$
 $T_2' = 3$ Amp
 $T_2' = \frac{3}{5}$
 $T_2' = \frac{3}$

1 to barrens house . Coursent - through 2-2 is $f_2 + f_2' = 10 \text{ Amp}$ 1-44 Statement of Superposition Theorem :-In a linear network, containing more than one source then, the resultant current in any branch is the algebraic sum of currents that could be produced by when single source acting alone and all other remaining Sources are replaced by their internal resustance (17 v.s, short circuit v=0, 17 c.s, open circuit v=0) Problem:3 Find the current through 2.2 using superposition theorem. 12 \sim \$ 32 100 5V step:1 Operating one source i.e., 5V and remaining sources (i.e., 10v) are replaced by their internal risistance (short circuit, n=0) I. 22 12 3 112 ه ک Y=0 5V T





3.









......



$$V_{TH} = I_{q-2} \neq R_{L} = q_{-2}$$

$$\begin{aligned} \widehat{J}_{L} &= \frac{V_{TH}}{R_{TH} + R_{L}} \\ &= \frac{23}{2+9} \\ &= \frac{23}{11} \end{aligned}$$

$$\mathcal{I}_{\perp} = 2.08 \text{ Amp}$$

Statement of Thevenin's Theorem: In any network having torminals A and B Can be replaced by voltage source (VTH) in series with the single resultance (RTH) -----0 A TH T οB (i) V_{TH} : (V_{PC}) $\sim 10^{-1}$ This is the vollage across the terminals A and B it any load removed i.e., open circuit Voltage across the terminals, (Voc). (ii) RTH :-This is the resistance which measured between the terminals -A and B if load removed and all other sources replaced by their internal resistances (if vollage source short circuit (n=0), if current source - open circuit (1=0))

Peichlem : 3

ж, с

ł

Find Rith when 60 is the load



Ryn:











pehilia Broblem:-

> Find the value of R for maximum power transfer in circuit and find maximum power delivered in R.

1-56











 $= \frac{150 \times 100}{150 + 100}$





Single phase arc. series circuit Ey \$8,63 的人 (1) Generation of Alternating Voltages & coments An alternating Voltage may be generated: (i) by rotating a call at castant angular relating in a viguin magnetic gold as shown in Fig. In eiker case, the generaled voltage will be of Sion sondal Linepum. The magnitude of generated willage will depend upon the 2 minute a finite of generated willage will depend upon the number of turns of cit, the strongth of magness had NESS a R. 2) Important A.C. Terminology:-(1) Where our of the Shape of the Unive obtained by plotting the Instantaneous values of voltage & connect as ordinate against time as asserved its called its Lave-Journ. (ii) Instantaneous value: The value of an allenating diantity at my distant is called Instantaneous Value. The distant values of alterating vollage & consert are represented by + i nespectively. (iii) cycle - one complete Set q pushie + negative values of an alleucking grantity is known as a colle. 90 180 270° 360° 9 WG

- (iv) Alternation: me haf-light of an alternation pumbility is called an alternation.
- (V) Time paiod: The time taken in Seconds to complete one asele of on alternating arendity is called its timeperiod. It is generally propresented by T.
- (Vi) Frequency: De number of coscle that beam in one second the control the greating (4) of the alternating ownship. It is measured for coscles/sec @ Hertz.
- (Vii) Amplitude. The maximum value (tre Cu -ve). (Vii) Amplitude. The maximum value (tre Cu -ve). alterized by in allemaling archtisty is called its amplitude or peak value. The amplitude of an allemating volter. or current is designated by Vm Co Im.

(3) Important redactions:-(i) Time puriod & gleguency:- $T = \frac{1}{2}$

(ii) Ansuke velocity & grequency;- $\int \omega = 2\pi f$

(iii) Frequency & Speed: $f = \frac{pN}{120}$

Define Average value, RMS value, Form Factor & peak factor. Average Value: - The average value of an allowating quantity is defined as the arithmetic mean of all the values over one complete agele. (1) Symmetrical brave :- In case of Symmetrical Waves, Ang. Value means the average value of hay cycle (D) one allom-atom. alsm. " Avg. value = Area q one allewaltin Base length of one allewaltin (ii) Un symmetrical wave form : The arg. value is taken over the guill cycle : Avg value = Area over one cycle. Base length of one cycle. T In general, Arg value, Your = + JUE. de RMS Value := The effective Or rims value of an alleinching current is that steady current (d.c). Which when glowing Grough a given Alsistance gol a given time produces the Same amount of heat as produced by the alternations Current when Horing krough the same redistance for the Same Gme -> In general, RMS value, YRMS = 1 5 y2(t). It Form Factor: - The matio of rms value to the aver value of an alternating quantity is known as form factor. i.e. Form Factor = <u>RMSValue</u> Arg. value. peak factor: - The natio of mon value to ke man of an alleunating Quantity is Known as peak factor i.e. PEAK Factor = Mon. value . RMS value .

(10) Find Average value, RMS value, Jorn faitur & Peat Jactor of Sinuscidal voltage. -> The equation of an allemating volkage varying simusidally is given by U=Vmfineto Avgivalue: Yarg = + Jy(t). dt Where Y(t) = Vmbin @. T .: Yarg = I S Vin Sind: 20: = Im S Sino do = Vm [-USO] $= \frac{V_{m}}{\pi} \left[1 + I \right] = \frac{2V_{m}}{\pi} = 0.637 \, \text{m}$ · Varg = 0,637Vm Where Y= Voltase = V 1.e Varg = 0.637 m RMS Value: - YRMS = (+ Jy (E). dt Where y(E) = Vm Sino. 255 $= \sqrt{\frac{1}{2\pi}} \sqrt{\frac{2\pi}{5570}} \sqrt{\frac{1}{5570}} \sqrt{\frac{1}{5570}}$ $= \sqrt{\frac{V_m}{2T}} \left(\frac{-\frac{1}{2}}{2} \right)$ $= \left(\frac{v_m^2}{2\pi} \left[\frac{0}{2} - \frac{5\pi^2 0}{7}\right]^{-1}\right)$ · Voms= Vm = 0.707Vm = Vm 21 - 0-0+0 = 1 = 0.707m

Scanned by CamScanner

from Factor:-F.F = RMS value Arg. value 1:3 $= \frac{0.707 \times V_m}{0.637 \times V_m} = 1.11$ Peak factor:-P.F= Man. Value RMS value = 1m = 1.414) Find average Value, KMS value, Poras Bater & place Sator of Sinusoidal current Sel The Equation of an allewating current varying Simussidary is given by i= In Sino Avg. value: - Yarg = I Syle)de where y(t)= In sino. $I_{arg} = \frac{1}{\pi} \int I_{m} h h \partial d \partial$ $= \frac{I_{m}}{T} \int_{0}^{0} \frac{J_{m}}{J_{m}} \frac{J_{m}}{J_{m}} \left(-\frac{J_{m}}{J_{m}}\right)^{\prime \prime}$ $= \frac{\mathbf{I}_{m}}{\pi} \left[\mathbf{1}_{+} \mathbf{1} \right] = \frac{2\mathbf{I}_{m}}{\pi} = 0.63 \mathbf{1}_{m}$: Iong = 0.637 Im YRons= I J THE dt RMS value :where YEE Insire.

Scanned by CamScanner

$$\begin{aligned} \overline{J}_{hms} &= \frac{1}{2\pi} \int_{0}^{2\pi} (\overline{J}_{m} \sin a)^{\frac{1}{2}} d\theta \\ &= \int_{0}^{2\pi} \int_{0}^{2\pi} (\overline{J}_{m} \sin a)^{\frac{1}{2}} d\theta \\ &= \int_{0}^{2\pi} \int_{0}^{2\pi} (\overline{J}_{m} \sin a) d\theta \\ &= \int_{0}^{2\pi} \int_{0}^{2\pi} \int_{0}^{2\pi} (\frac{1-(asue)}{2}) d\theta \\ &= \int_{0}^{2\pi} \int_{0}^{2\pi} \left[\frac{\theta}{2} - \frac{sh_{2}\theta}{4} \int_{0}^{2\pi} \right]^{2\pi} \\ &= \frac{J_{m}}{2\pi} \left[\frac{2\pi}{2} - \frac{0-0+\sigma}{4} \right] \\ &= \frac{J_{m}}{\sqrt{2}} = 0.707 J_{m} \\ \hline \overline{J}_{ms} &= 0.707 J_{m} \\ \hline \overline{J}_{ms} &= 0.707 J_{m} \\ \hline \overline{J}_{ms} &= \frac{0.707 J_{m}}{0.637 J_{m}} \\ \hline Penk Factor: PF = \frac{Nusvalue}{Rnsvalue} \\ &= \frac{J_{m}}{0.707 J_{m}} = 1.009 \end{aligned}$$

A Explain andysis of t-b Rebience Gravid Scriptain andysis of 1-b Inductional (C) Explain andysis 2 1-4 copulan. (1) current : the allewating words (1) current : the allevating work volteres in a purchy missive exerce inductive (2) Ware-form - From es 0 20, iti = In sin (200+20°) [- @ = WCV, Sin(20+450) 20 consider a pure capillar C = C de (Ver Sime) vollage & 20 SLOPPIN FIG. Lev be addeen along millerge Where In = WCVM ひ= ひょうしん - 62 C MA COSA g (3) phaser disgram 190 トレー (, ,) 19= Vin Sirve -(1) 5 Et rave 21 () N A RI Gount 01 Compilar a pure Altistar R' Connected alwas (misider a pure Inductor L'innected an allounding voltage source v as across in alternationg voltage U as 34am where the attending to love the the attende (2) Have form :- From eq () 9 (2), it 28 clear that the correct is in prise (2) Liste- 7427 :- From eq () 1 (2) (5) 29 h the volcage in a purely getsting (2) Lister 7427 :- From eq () 1 (2) (5) In 52 (24-1/2 -2) Φ 1 61 (14-11) = <u>L</u>(unsintedt = <u>un</u> (-cesute) = <u>236</u> y=Vm Sinulc. 1= 1 Svale (3) phise dicgram Given by. è l 2 H > Ń in B9 . 21 17 (1) CUTTERL: The alternations current $i = T_m sinul - (2)(n^{-k_m})$ an allenating voldage Source V ab Let be deterrating volege de 0 9= Vinsinut. i' is given by unsind X (3) phetor Diagram :-K V 2 Showin fig. V= Vn Sinder 0 Circul

The granting I is called lepacities preactance, is denoted by XC + is measured in -2. Stis the tongle blas voltage & Lurrers (6) Priver factor :- 36 is durined a The guidese poster per one $Z = \frac{V}{T} = \frac{V_{111}}{V_{111}} = \frac{V_{1111}}{V_{111}} = \frac{V_{1111}}{V_{111}} = \frac{V_{111}}{V_{111}} = \frac{V_$ (1) million leaves pour p is given by the cosine of lea angle 3/2 the 'p' = Vi = Vinsinist Insin(22+1/2) Vo/Laye + Currect phistods. (B) Impedante :-- Vin Shoul In Sin (Ut +53°) complete cycle, D=0. (1) 975 lankarears power Ces & = Costo = 0 = Vin Ing Sinucidue $Z = \frac{1}{\omega c} = X_{c}$ (B) phase difference:-(1) AVEREY POWER'S = Vin Tay Sinzut phasos. 10200 -: TOPACE p=U. (Toductance Grave) the cosine of the angle the the () para Factor :- 91 is defined as \$= 50° }> Cos \$ = Cos 30° = 0 the granting and is called inductive receivered (24) $Z = \frac{V}{I} = \frac{V_{n1}}{2n} = \frac{V_{n1}}{2n} = \frac{V_{n1}}{2n} = \frac{V_{n2}}{2n}$ (5) Phase difference :- Since the phase bitturence :- St is the single Voltage & current are in phase bits the milery & current phases. Isin each other, the phase bits the milery & current phases. difference is Zero. The gracese power but one = -Von Tung Sigur Cosul (C) POWER Factor: 94 is defined volage + current phased = - Vin Sirewle. unplute usue, P=0 |Z = |U| = X|(ii) Avelage power:-(H) Inpedance: (R. Cirwild (A) Impedance: dence. $Z = \frac{V}{I} = \frac{V_{11}}{2n} = \frac{V_{11}}{V_{11}} = R$ - Vin In Martin - Vin Thomas with as lee word of lee sugle the The power consists of a constraint part vintin + philosching part P= 2 2= V7 P = U i = Vinsion Jucies and = "m" m (1- (22 we) = Vor 200 Part and = (i) Averge paret P= Unitin [Cos & = 1030 = 1 (i) meranencas para p : Z=R \$ 20° Uniter USZWE. (f) pover:-

Scanned by CamScanner

PROBLEMS: 2-

5 ~ S.

(10) An A.C. Circuit Consists & a pure resistance of 10-2 and is connected across an A.C. Supply of 230V, SoHz. Calculate (1) correct (11) Power consumed (1111) white down the Equations for voltage & correct

it it it

Sol	R=10-2
	i
	2307,50#3
	Given dala: - R=10-2; V=230V; f=50 HZ.
(i)	$lurrent I = \frac{V}{R} = \frac{230}{10} = 23A$
	$p_{GWU}, P = VI = 230 \times 23 = 5290 M$
(ÌĨ)	$V_{m} = \sqrt{2} V_{rms} = \sqrt{2} \times 230 = 357 325.27V$
	Im= V2 Ims = V2×23 = 3952A
	W = 277f = 277 × 50 = 314 Hz
	. Equations of Vollage & correctare:
	19 = 325.27 Sin3146
	1=32-52 8123146

(1.59 PARENO SUR VIK-MESTA (1.59 PARENO SUR VIK-MESTA (2) A PUTE inductive coils allows a current of 10A to 2000 (2) (2) A PUTE inductive coils allows a current of 10A to 2000 (2) (2) A PUTE inductive coils allows a current of 10A to 2000 (2) grom a 230V, SO H3 supply. Find (1) Inductive reactance @ Inductance of the cost (iii) power absorbed. Write down lese equations for wollage & current. Soli- () Circuite correct, I = V/XL . Inductive reactance, $X_L = \frac{V}{I} = \frac{230}{10} = 23 - 1$ (i) NON, X_ = 2TT+L $L = \frac{\chi_{L}}{2\pi f} = \frac{23}{2\pi \chi_{D}} = 0.073 H$ (iii) power absorbed = zero Vm = V2 × 230 = 325.27V (Ì) Im=V2×10 = 14,14 A W= 277 × 50 = 314 :. 0 = 325,27 Sin 3146 i = 14.14 Sim (314E-11/2) A 318 MF capacitor is connected across a 235V, 50Hz. [1.63 page No. 545 Wikinenta pr. system. Determine () the tapalitive reactance (3)@ soms value of worke (ii) equations for voltage + Current. Sol: O capacitive reactance, XC = 1000 = 10-2 (i) R.H. S value 2 correct, $I = \frac{V}{X_c} = \frac{230}{10} = 23A$ (III) Vm = V2X230 = 325.27 Volks 7m = V2X23 = 32.53 A W = 277×50 = 3/4 . equations for vollage & correct are 19=325.27 55 3146 i= 32.53 Sin (3146+11/2)

Ag. Shous a pure susseen R, me grander L. + pure C & connected in sovies يا در R-L-C Sovies Circlet away an allewating U= 4 Sinch. 2 لين ×د ۲[×]د ≯ 2⁄1 (ii) $x_{C} > x_{L}$ (il)san ounsisede. 2 () phild bidgen 2) 1016al mansle 16 5 1-1-1 J V = XI > VE= Itc Ľ > UR=IR エ 大 U XL7XL () X 24 ¥ -> volceye abop alors relicion = V= TXc -> volceye abop alors source = V= TXc a = var (x) where it. > IL VOLLENCE VE IS IN prese with I a R-C Scores Limuir 2) roland marghe 's Impediate 2000 a) don't any allemating where in sever with a pure capacitor Fig. Groves a pire suductor concilied V= しかと= Rユーグシビス = (&j×(-)] 50 12 = N ANDR Z = VR4X6 (2) volley tringle (1) phabar diagram: Ч М < Nr - 1 - 1 > 10 = Vin Sinut «Ş FX V levels be wrrest 2 30°. R- L Series crawit In series with a pure inductor 'L' $7 \times 7 = 7 = 78$ mpcet 11 Fig Shows a pure gubiller R conscient > voleax drop away quester = 1/2 2 R A The relaye of is in phase with I acres an allen ating 10 = Un Sinul H $V = V_R + V_L = RITIJIX_L$ V = Y(L) + JMU, CHASK Cleg XX JAVI VETZY 14 -: manpo diagram :triansle (S)(3) Impedance:-Ř \propto 1 (2) vollax : = 介

XCXL given by U= VerSind then current equality will be in In (Bin (244)) 5) Current: So be applied voltant is Ø Cabelin - XCJYL Case(ii) XC>XL (3) Impedince R-L-C- Series Circuit I sign is used when X_XL - Bin is valed when XUTKC 4 (4) Impedance Thransleir $= I \left[n + j (x + y) \right]$ = IR+J IX-J IXC $Z = \sqrt{R^2 + (3_1 - 3_2)^2}$ \$ = len (XLXC) $V = V_R + V_L + V_C$ X X Xc 0 V = T Z(6) LISYE POLT: cale(): X >Xc COLE U X XC 4 Were R-C- Seques lixue X CUPCR BYPRIAL ROLL S=1=22 that the correct I leads the by angle of. Active power, P=VI 1289 Reachine posed, & = VISing = 72R -7×C (S) CUNTERL: St is clear i = Jn Sin (21+4) Ø 4 2 cm () (4) Impedance Triengle Were June 2 1 (9) LIGNEL JOURNIL (7) POLICI (S) CUTTERLE: 94 is Clear that R-L Segues Cirmic 70 × (13 9= 2 that current I leas behind and $\phi = en^{-1}(\frac{h}{k})$ (= 7 m & 1/ (11- b) Ø ゆこめっ」(XL) When z=/R7x2 (4) Impedenc Tringle: Where In = Vr HLAR X = WC (C) Ware-garai 1 ak Ð

Scanned by CamScanner

springer I front From poult gen vollege Realise power Q=VIShy=IX Case () XL 7Xc Case () XCXL \bigotimes (6) POLIER: Rever Sevies UTUNI Appared pover S = VI=I2 ANG. PONOR P=VILLEG=IR (Z) power Triangle: (8) Pava factor. CS & = K 70 Ces \$ = . Ø (A)= From vollax From Z toringle, Cold 2 R From pover briengle UNG 2 a cut = l R-C- Sevies Limit (8) parer mangle: (d) power factor: = 42 (20(4) - 42 (20(4) P Cosp 2 0 part and = des at an int in = un In [1034- 103(246-4)] (9) paren Jacled's From miker terriste, 19.4= 4 1. Ingelore " Pit= 2 fluctuality _ United (2216-4) R-L Series Wrunit B=VILUAD = Un In Sinut Six (46-4) Apparent power, S = VZ = IZ = Vin Binute In Sin (ut-b) muce consists of the parts Crustert = Virger (130 Seather pour, Q = VISit OS#= F + V=IZ Alle price, P=VZ Let (i) Average power, P (E) PAIR brianslein (1) grat. power (P) in =d (I) Power:
110 Define Impedance, admittance, reactance, SUSCEptance () Impedance: -(Z): - The total opposition officed to the glow of alternating current is called Impedance. → It is represented by Z → It is measured in ohm (-2) Z= R+j×L Where $|z| = \sqrt{R^2 + \chi_2^2}$ 4 = 4515-1(XL) (1) Admittance (Y) :- Admittance is defined as the Reciprical of the Impedance. > It is denoted by Y. > It is measured in who (25) 「Y==」-ひ Y=G=jB)-> In complex Form. (III) Susceptance (B) > The reciproral of reactance is called susceptance > The susceptance of an Inductive is called Inductive Cusceptance of an Inductive is called Inductive SUS ceptance (BL) where as that of a capacitance is Called Capacitive Susceptance (B) $|B = \frac{1}{X} | - \nabla$ -> BL&BC are measured in J. (iv) <u>Reactance</u> (X):--> Inductive reactance: - The opposition oppred by Inductive to current flow is all this putshing we is called Indultive reactionce X' of the coil. -> It is measured in a $X_{L} = 2\pi I L = \omega L$

-> Capacitive reactance: The opposition offered by Capacitance to current glow is the . This auntity the is willed the Capacitive reactance X of the capacita. -> 96 is measured in a $X_c = \frac{1}{\lambda c} = \frac{1}{2\pi f c} - \Omega_{-}$ The power factor (i.e. casp) of a Circuit can be defined in one of the Dollowing ways. Power factor: -(i) (430 = (obine of angle between vollage & current (ii) poverfactor = cosp= R/2 (iii) power factor = $\frac{V_{1}(z)}{V_{1}} = \frac{P}{S}$ (00) Comparsion between arc sories & parallel tirtuit A.C. Series limite A.C. parallel circuite O voltage is same () current is some 2) There is current division in (2) There is voltage drup in series circuit Par-Ilel Coscil-(3) Admittanic (4) conse (3) Impedance (2) an be calchded Calculated G susceptance (B) can be calculated. (4) Reactance (X) Lan Se calculated () Here Y = G 7 jB (3) Here z = RtjX De Admittance Susceptance + conductance is meas used in U. 6) Impedance, readance, resistance Ø connection goe RL serves (7) connection yor RL series listing Ð Cirait 12 com y2 V 2 2 2 2 L

Scanned by CamScanner

Problem: 1 Proprietation
An AC circuit convists of a pure precision of
10.2 and is connected across an AC supply of
2300, 50Hy. Calculate is current in Power
consumption (ii) vorite the equations for voltage
and current:

$$I = \frac{V}{R}$$

 $I = \frac{230}{10}$
 $I = 23 \text{ Amp}$
(i) Power Consumption:-
 $P = VP \cos \varphi$
 $P = VP$
 $= 30000$
(ii) Power Consumption:-
 $P = VP \cos \varphi$
 $P = VP$
 $= 30000$
(iii) $V = Vmsincut$
 $i = 2msincut$
 $V = 20000$
 $V = 20000$
 $V = 20000$
 $V = Vms \times VI = 23000$
 $V = 20000$
 $V = Vms \times VI = 32.52 \text{ Amp}$

and the second s

2-19 as = 2715 = 314 $V = 325.24 \sin(314t)$ i = 32.525in (314t) Pure inductor Roblem: 2 A pure inductive coil allows a current of 10 Amp to flow from a 230v, 50 Hz supply. Find is Inductive reactance (XI). (i) Inductance of coil (L), (ill, Rower consumed (iv) write the equations for vollage and curren L. 9 = 230 v , += 50hz ; Given data:garAFS T V=230V instrantion in a fin f=50 Hy peosiv P T = 10 A ΰ×ι:-86×086 V= PZ 0,019,00 V=IXL fraction - $X = \frac{v}{T} = a 3 n$ Junien? - 1 6, Xz = WL L= 2 = 0.073 Henry qmActiste lix unit mC

(i)
$$P=0$$
 (\cdot P = $\mathbb{P} \times \cos \phi$)
 $i = 2 \mod \cos \phi = -0$
 $i = 2 \mod (\cos \phi - \pi/2) - 0$
 $V_{m} = V_{rms} \times \sqrt{2} = -325 \cdot 27V$
 $I_{m} = 2 \mod \sqrt{2} = -100 \operatorname{Tr} + 314$
 $CO = \partial \pi f = d \times \pi \times 50 = 100 \operatorname{Tr} + 314$
 $V = 32 \cdot 52 + \sin(314 + \pi/2)$
 $i = 14 \cdot 14 \sin(314 + \pi/2)$

Problem: 3 to Rivericapàculance A 318 par capacitor is connected across a 2300, solty Supply. Calculate (i) Capacitive reactance (xc) (i) RMS value of courrent (iii) Power consumed Br) Write the equations for vollage and current. Given data:-C = 318×10-6 F V=230V f = 50 Hy w= 2117f = 314 的 Xc :- $X_c = \frac{1}{\omega c} = \frac{1}{3! \omega \times 3! 3 \times 10^{-6}} = 10 \Omega$

(i)
$$f_{rms}:$$
 (product the second s

•

14.5

R-L Series Concuit. 5/2/19 2-22 Problem:-An alternating vollage (30+j60) v is applied to The V: a scinquit and the current flowing is (4-j2) Am I find (a) Impedance (b) Phase angle (c) Power factor 5u (d) Power consumed. (C) Co (i) Împedance (z):-)× V=12 Guiven data:-V = (80 + 160) = shift Rol(80,60) = 100 (36.86 I = (a -j2) = shift Pol(4, -2) = 4.47 L=26.56 ů For mulliplication & division V=92 use polar form $Z = \frac{V}{T_{2}} = \frac{100 [36.86]}{4.44 - 26.56}$ Z = 22:37 (63.42 2=22:37-2 (ii) Phase angle (\$):-\$= 63.42 (From impedance) (ii) Power factor :-COS \$= cos (63.42) = 0.447 (Lags), (M) Power consumed:-P = VI cost = 100 2000 × 4 47 × 044 = 196.68W

Problem :-

The voltage trad current in a circuit is given by V=150 L30° in polar form and current I = 21-15°. Pf. the circuit works on a 50Hy Supply Determine (a) Impedance (b) Resistance (c) Reactance (d) Power Factor (e) Power loss. Considering the circuit as a simple series circuit.

Given data, V = 150 L30° = 129,90 + j 75 = 130 + 75 j 1 = 2 L-15 = 193 - 10.517 f = 50Hy (a) Impedance (z):-V=IZ $Z = \frac{V}{T} = \frac{150 \lfloor 30}{21 - 15} = 75 \lfloor 45 \rfloor$ Z= 53:03 + j 53:03 $Z = 53 + j53 = R + JX_{L}$ ·. Z= 75.0 (b) Resistânce (R) :-From Impedance, R = 53

XL= 53 -2 (03 + to) - 1 - 1

(d) power factor :- $\cos \phi = \cos u5 = 0.707 [lags].$ (e) Power loss or Power Consumption:- $P = V I \cos \phi$ = 300×0. 101 P= 212.1 W (H) Phason Diagram: T 150€35 0 [-15] ,] ≓ = [165 R-C Series Cincuit Problem:-XE14 61 1.63 The voltage applied lo a circuit is e=100 sinfect and the current is i=155in (art +60). Determine +30) (a) Impedance (b) Resistance (c) Reachance (d) Power ballor (e) Power consumed. > 6 - 5 C 4 Griven data: $e = 100 \sin(\omega t + 30')$ $i = 15 \sin(\omega t + 60')$

2-25 state in Vm = 100V, i = 15 Amp $V_{\text{rms}} = \frac{V_{\text{m}}}{\sqrt{2}} \begin{bmatrix} 30' = 30, 31 \end{bmatrix} = 61.2 + j 35.3 V$ $f_{rms} = \frac{T_m}{\sqrt{2}} \frac{160}{160} = 10.60 \ L60^\circ = 5.3 + 99.1 \ Amp$ ne it si 19-22-10-10 JOUSTY P (a) Impedance:- $\mathcal{I} = \frac{\mathcal{V}}{\mathcal{I}} = \frac{40.71}{10.60} [30^{\circ} - 6.64] - 30^{\circ} = 5.74 - 30^{\circ} - 30^{\circ} =$ V= SZ 20-30 6 TATSIEL : , Z = 6.67-2 -: AVX (d) (b) Resistance :-R= 5-77-2 7 - 4.00 (c) Reactance :-1 de la Xc = 3.33 (d) Power factor: - AVSII - AVSOUL - 2 $\cos \phi = \frac{\sqrt{3}}{2} = 0.86 \text{ (leads)}$ (e) Power consumed :- print ? P=VI cosp = 644.5920 -Sav Suic Kung Problem :-A series circuit consumes 200010 at 0.5 leading Power-factor when connected to a 230V, 50 hy supply - Calculate (a) current (b) KVA (E) KVAR

-26 Given data :good is in a source of P= 2000W Veder + Sile - OSTH-OF - 081 mv - emv profil = 50 Hy & 63, 63-01 . 14 mil ... $\cos\phi = 0.5 \Rightarrow \phi = 60^{\circ}$ -1 sinch ward in (1) Current :-P= VICOSO 0000 = 030 1 × 0.5 081 14 00. v r おという- 「う-10 60 160 $I = \frac{v_{000}}{230 \times 0.5}$ 1. Z = 0. 64.2 1 = 17.39 Amp : State not (b) KVA :-R. FF-d . 9 $\cos \varphi = \frac{P}{8}$ - madaay (1) $S = \frac{P}{\cos\phi}$ 5 . 3 33 S = 4000VA = 4KVA. KVAR:- (about) ou a ever to a (C) Q=VIsing through the second of the = 3463 (284 - 12) - portiv 1 = 3.46 KVAR and the second of the second and the second of the second

Roblem:
Roblem:
A service of vesiltance of 20.01, inductor of 0.05H,
A service of 50,4F are connected in services.
A supply voltage 2300, 50Hy is connected
across services combination. Calculate
(a) Impedance (b) current (c) Thase difference
(a) Power factor (c) -Active and reactive power.
Curren data:

$$R = 20.0-$$

 $L = 0.05H$
 $C = 50,4F = 50 \times 10 \text{ eff}$ (100 C . . fro
 $V = 2000^{-1}$
 $L = 50.4F$
 $C = 50,4F = 50 \times 10 \text{ eff}$ (100 C . . fro
 $V = 200^{-1}$
 $L = 0.05H$
 $C = 80,4F = 50 \times 10 \text{ eff}$ (100 C . . fro
 $V = 200^{-1}$
 $L = 0.05H$
 $C = 80,4F = 50 \times 10 \text{ eff}$ (100 C . . fro
 $V = 200^{-1}$
 $L = 0.05H$
 $C = 80,4F = 50 \times 10 \text{ eff}$ (100 C . . fro
 $V = 0.00^{-1}$
 $L = 0.05H$
 $C = 80,4F = 50 \times 10^{-1} \text{ for } 1000^{-1} \text{ for } 10$

(b) Current !-

V=IR $I = \frac{V}{R}$ I = H. 42 L-67.37 1 = 4.42 6-67.37 (c) Phase difference :ver lata. 67.34 10.00 9 (d) Power factor :-11200 - 1 C05\$ = 0.384 (leads) - 7.00 (e) Active and Reactive Power:-Relive P=VIcos\$ = 391.16 W Reactive $P = V I \sin \phi = 938.33 \psi_1$, 9 5. Kiel - 100 . K - (2 69 - (2) X (+ 30 + j (+ 4 - 68 - 69) 7 = 20 - 1 HA. 99 · FE- FO J EF-10 = 5 9-P-10-2

D. C. Grenerators 9 nston · Principle & operation of a D.c. generator: 3-1 ab, Statement: - It states that, Whenever the number of magnetic lines & zouces i.e. zlux linking with a conductor or a loid changes, an electromotive purce is set up in that conductor or coil.



Instant 1: - Let the Initial position of the cirk as shown in Fig. The plane of the cirk is puppedicular to the direction of the magnetic field. The Instantioneous component of relocity magnetic field. The Instantioneous component of relocity of conductors as a col, is paulled, to the magnetic field of conductors as a col, is paulled, to the magnetic field as shown and there cannot be the cutting of the flux lines by the conductors. Hence no emp will be generated lines by the conductors at a col and no current will be generated in the conductors at a col and no current will glow through the external publicance R. This position can be separated by considering the funct view of Fig U as shown in Fig Q.

Instant 2: - When the cirk is rotated in an hiclockinse direction through some imple of than the velocity will have are components visno perpendicular to gue lines + visino paulla to be gue lines. the to visino component, there will be to be gue lines. the to visino component, there will be cutting of the guine & proportionally there will be as induced emp in the conductor gs & cd.

E



Instant 3: - As angle & Increases, the component of Velocity along perpendicular to Hux, tincs increases, hence induced emp also increases. At 0=50°, the plane of the chil is prushed to the plane of the magnetic field while the component of relacity lutting the lines of flux is at its maximum. So Induced emp in this position, is at its maximum value.

Instant 4: As the Chil Continues to notate jurner Jean 0=90° to 180°, the component of velocity, perpendicular to magnetic field starts decreasing here. gradually decreasing be magnitude. I the induced emf. This is shown in the Fig D

Instants: - In this position, the relating component is Jully phiallel to the lines of glux similar to the Instant 1. Hence there is no cutting of flux shere no Induced emp in both the conductors. Hence the current torough external circuit is also zelo.

9rstant 6: - As the call notates beyond 0=180°, the conductor QE Upfill now cutting zun lines in me particular direction hereises the direction of withing the glun lines. Similar is the betaniour of the conductor ed. So direction of Induced empin conductor as is opposite to the direction of induced emp in it for the notation go =0° to 180°. Similarly be direction of induced emp in conductor Cd also reverses this change in direction of induced emp occurs because the direction of rolation Conductors as A cd reverses Lin respect to the field as a varies from 150° to 360°. A Induced emb + Em 150° 220° > O 900 Construction of a practical D.C. Machine:-- Yoke FX SF Flux produced Commutation Poleshe. > Armalure Linding Brush PHe core

Yoke:-

Function :-

Dit surves the purpose of outermost lover of the d.c. machines so that the insulating materials get protected zen harmond atmospheric elements like moisture, dust + various groce like So, acidic gomes étc.

(2) 96 providus mechanical support to the poles.

Choice q matorial:-Cast ison For Small machines :-CASESEL, Silicon Steel. For large machines :-

POLES:-Each pole is divided into too parts namely (i) pole care @ pole shoe.

- Function à pole core 2 pole shoe: (2) pole core babically carries a filled winding which is necessary to produce the glun.
- (2) 96 directs the Hun produced through air 34p to armatine cole, to the signe pole.

(3) pole shoe :- It enlarges the area of armalure core to come across the zuna, which is secondary to produce lærger induced emz.

Choice of material:-96 is made up of magnetic material like cast Irm @ Cast Steel.

Field Linding: - (FI-F2) 3-3 3 The gier () to carry current due to which pole Lole, on Which the field winding is placed becares as an electromagnet, producing necessary glun. Choice of material: - aluminium of Copper Amature:-He is gurker divided into two parts namely. () Armature Core (2) Armature Londing (J) Armaline core: - Armaline cole is cylindrical in shape mounted in the shapt. It consists of slots on its periphery & the air ducts to pensit the air flow Wrough amature which serves cooling purpose. Functions: - Armatine core provides house for amature Linding i.e. amature conductors, Choice of material: - Cast iron () Cast Steel. (I) Armaline Linding:-Functions:-() Creseration of enor lakes place in amature winding in case of generators. Choice Z malarial: - Copper. Commutatol:-Functions:-() to facilitate the collection of correct glan the armature conductors. (2) to convert internally developed alternating emb to unidirectional (d. c) emp. Choice of material i- Coppler beginents.

Brushes:
Function: to collect current ferm commutate I make it
available to be stationary external circuit
Choice of material: Brushes are somewhy made 40°7
Soft material like cuben.
EMF Equation of D.c. Generalois:

$$Let P = Number g poles g be generaled
d = Flux produced by tack peter in sectal (45)
d = Flux produced by tack peter in sectal (45)
 $Z = total minder g handline in ripin
N = Speed g handline in ripin
N = Speed g handline in ripin
A = P gen lap type g winding
A = P gen lap type g winding
 $A = P$ gen have type g winding
 $From Feradacies law g tend
in ductors we produced by all the poles.
i.e. $\phi \times P$
 $dt = Mile the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to the poles.$
 $R = for the gray break to complete the
 $R = hill the the gray break to complete the
 $R = hill the the gray break to the poles the terms the form the terms form the f$$$$$$$$$$$$$$$$$

3-4 ". Total comp can be expressed as $S^{-\gamma}$ $E = Arg. Value g emp induced in each <math>\chi Z$ $E = e \chi Z$ armalia A Crodulan $F = 4 \frac{pN}{60} \times \frac{2}{A}$

proskins:-

(A) A 4 pole, Lap wound, d.c. Generator has a useful guin of 0.07 We per pole. Calculate the generated emore when it is notated at a speed of 900 rpm with the help of prime more. Armature consists of 440 worker of conductors. Also calculate the generated mumber of conductors. Also calculate the generated emore if less wound armature is replaced by worke wound armature.

Sol Given deta: P=4, Z=440, \$=0.07116, N=900 Ypm $: E = \frac{\partial PNZ}{\partial A}$

(i) For lap wound,

$$A = P = 4$$

$$E = \frac{607 \times 500 \times 440}{60} = 462V$$
(ii) For wave wound:

$$A = 2$$

$$E = \frac{0.07 \times 900 \times 4 \times 440}{120} = 924V$$

(2) A 4 pole, Lep wound, d.c. generalow. has 42 wills with
8 torms per coils. It is driven at 1120 mpm. 92,
Useque zhor per pole is 21 merb, Calulate the generated

$$2m_{3}$$
. Find the speech at which it is to be driven
to generate the same emp as calculated above, with
 $2m_{3}$. Find the samature.
Set: Given data:
 $P = 4g$, $\phi = 21m_{3}Mb = 21 \times 10^{3}Mb$, $N = 1120$ mpm.
Cids = 42 + torms/cid = 8
Total torms = cids x torms/cid = 42x8=33b
 $Z = 2x$ total torms = 2x33b = 672

(i) For
$$lep hound := A = P$$

 $F = \frac{\phi P N Z}{60A} = \frac{21 \times 10^{-3} \times 41 \times 1120 \times 672}{60} = 263.42V$

(ii) For Like wound:
$$A = 2$$

 $E = 263.42V$
 $E = \frac{\Phi PNZ}{60A}$
 $263.42 = \frac{21\times10^{-3}\times4\times10\times672}{60\times2}$
 $N = 560 \text{ Spm}$

D. C. Molor Principle of operation of a D. c. Motor (3) STATMENT: When a current carrying conductor is placed in a magnetic field, it experiences a mechanical zone. Consider a single anductor placed in a magnetic field as shown in Fig. The magnetic field is produced by a painting the magnetic field is produced by a paimanent magnet but in a practical d. c.motal. It is produced by the field winding when it carries a current. Conductar N F3B N F3B Now this conductor is excited by a separate supply So that it corries a current in a particular direction. Christer that it comies a current away from an observe as shown in Fig a. Any correct carrying conductor produces its our magnetic field. around it, hence this conductor also Produces its own flux, wound, the direction of this zlox (an be determined by sight hand through fule. For direction of wreak considered, the direction of glass around a conductor is Clarkinse. NOW leve are two flores present () the flux produced by the plumanent mappet Called main £1-2 2) The flux produced by the current- carrying conductor. These are shown in Fig(). from this it is clear that me one side of the conductor, both the flores are in the same direction. In this case, on the left of the conductor there is galaxing of the flux lines is the flux help end other. As against this, on the hight of the Conductor, the two flunes are in opposite direction & here try to contact cach

Duce to this, the density of the flux lines in this wea Its Weakened. So in the life, there exists high flux. Density area while in the night of the Linchulter there exists low flux density area as shorm in Fig. (2)



This flow distribution around the Lonductor acts like a stretched rubber band under tension. This exacts a mechanical Joke on the Conductor Which alls floor bigh flow density area tourids low flow density area, i.e. flow density area tourids low flow density area, i.e.

Rg.O Direction of Rotation of Motor The magnitude of the force experienced by the conductor in a motor is sizen by F= BLI Newtons B = Flux density due to the flux

L = Active length of the conductor I = Magnitude og he worrent passing Errough the conductor.

Fleming's Left Hend rule:-It states that " outstretch the three fingers of the left hand namely the first firser, middle tinger & think such that key are mutually perpendicular to each other. Now Print- the first finger in the direction of mapsetic filled & the middle tinger in the direction of Current then the thumb indicates growthin.

Scanned by CamScanner

Significance of Back CMF:-DAHer a motoring action, there exists a generating action. There is an induced comp in la rotating armature conductors according to Faraday's law of Olettomappetic Induction. This Induced emp in the armature always acts in the opposite direction of the Supply voltage. This is according to be len's Law. Don a d. C. motor, electrical impat i.e. the Supply voltage is the cause + here this induced emp opposes the supply voltage. This emp trics to set up a current tragh the almature which is in opposite direction to hat which supply voltage is goring knows? the conductor. (3) So as this emp opposes the supply voltage. it is Called "back comp" and denoted as Eb. magnitude can be determined by the EMF equation ('4) So**b** its TEG = OPNZ Volk. < −0 + Ia , + In A 1+ ---- V T-== Km) V Supply Vo Hege ERa J In -(a) Back emp in a (b) Equivalent livenit D.C.Motor Voltage equation of a D.C. Molor Applying KVL to loop equivalent circuit above Fa In V V-65-Jek = 0 V = E6 + Jaka V. ERa Ja o-

Scanned by CamScanner

(10) A 220V, d.c. Holor has a armatine sussistance of 0.752 96 is draking an armatine arrent of 30A, driving a certain load. Calculate the Induced comprinte motor under this condition.

Sul: V=200V, Ia=30A, Ra=6.75-2 $V = E_b + Z_a Ra$ 220 = E6+30×0,75 Eb= 197.5 Volts

20 A 4-pole d.C. Motor has tap connected armtin Linding, Jle flux per pole its 30 math. The sumer of armatum conductors its 250. When connected to 230V, d.C. Supply it draws an ampatule current of 40 A. Calculate the back compt the speed with which motore is grunning. Assume armatume subistance its 0.6-2

From voltage equation

$$V = E_{b} + J_{a}R_{a}$$

 $230 = E_{b} + 4000.6$
 $\overline{E_{b}} = 206V$
 $\overline{C} = \frac{\phi p_{N} Z}{60A}$
 $206 = \frac{3000^{-3} \times 4000}{6000}$
 $\overline{N} = 1648 = 0000$

POWER Equilier of a D.C. Model (1)
Jle roltage equilier of a. d.c. model is given by

$$V = E_{L} + I_{R}R_{R}$$

Multiplying toh sides by Ia, be set
 $\boxed{VI_{R} = E_{L}I_{R} + I_{R}R_{R}} - O$
Jhis equation is called power equilier & a
active
Multiplying to the electrical power lower equilier & a
 $E_{L}I_{R} = O$
 $VI_{R} = O$ and the electrical power lower equilier P_{R}
 $E_{L}I_{R} = O$ and $P_{R}OUTE (P_{R}OUTE to the armative
 $P_{R}OUTE to the grandine $P_{R}OUTE to the armative
 $P_{R}OUTE to the formative to the grandine $P_{R}OUTE to the armative
 $P_{R}OUTE to the formative to the grandine $P_{R}OUTE to the formative
 $P_{R}OUTE to the formative to the grandine $P_{R}OUTE to the formative to the grandine to $P_{R}OUTE to the formative to the formative to the grandine to $P_{R}OUTE to the formative t$$$$$$$$$$$$$$

Totique Equilien
$$z = D.C. Moloi:$$

It is the turning (D) thisting porce Rotation
about an aria is called torque.
(Asidor a likel of radius R melus
acced upon by a Circumperential
Doce F mextures as shown in Fig.
The Wheel is rotating at asped of Nrpm
 $D = \frac{2\pi N}{60}$ radige.
So Workdone in one Revision in
 $W = Fadistance travelled in one revolution
 $= F \times 2\pi R$ Tolles.
 $P = Prover developed = \frac{Vorkdone}{6me primerout}$
 $= \frac{F \times 2\pi R}{60}$
 $= (F \times R) \times (\frac{2\pi N}{60})$
 $F = T \times W$
 $F = Ta \times \frac{2\pi N}{60}$
 $T_{2} = 0.159 \phi T_{4} \cdot \frac{PZ}{A}$ N-M$

TRANSFORMER (Working Principle of a Gransformer). A transformer is a istatic piece of requipment used wither for valising or lowering the woltage of an a.c. isupply with a corresponding decrease or increase in convent. It ressentially consists of two windings, the primary rand recordary, would ion a rommon ilaminated magnetic core as shown in fig. The winding connected to the a.c. source is called primary winding (or primary) and the one connected to load is called secondary winding (by secondary). The alternating voltage V1 whose magnitude is to be changed is applied to the primary. Depending upon the number vop twins of the primary (N1) and iscandary (N2), ran valtoinating e.m.f Ez is induced in the secondary. This induced esm.f. Ez in the secondary rauses a secondary consequently, terminal voltage 1/2 will rappear racross the load. of 1/2 > 1/2 it is realled in 1stepup transformer. On the other hand, if $V_2 < V_1$, it is realled a istep-idown transformer. Working: when an alternating voltage V1 is applied to the primary, an alternating flux of is in the the windings wit core. This alternating flux links both and induces e.m.f. is E1 land E2 in the



according to Faraday & laws of electromagnetic induction. the e.m.f. Ej is tormed as primary e.m.f. and e.m.f. Ez is termed ias iscondary e.m.f. $E_1 = N_1 \frac{d\phi}{d}$ is the set of the set clearly,

$$E_{2} = -N_{2} \frac{d\phi}{dt}$$

$$\frac{E_{2}}{E_{1}} = \frac{N_{2}}{N_{1}}$$

$$\frac{1}{N_{2}}$$

Note that magnitudes of E2 and E1 depend upon the number of twins ion the tecondary and primary resp. If $N_2 > N_1$, when $E_2 > E_1$ (or $V_2 > V_1$) and use get a step up transformer. On the other hand, if N2 < N1 then E2 < E1 (or V2 < V1) rand we get a step down transformer. of load connected across the secondary winding, the reconderry e.m.f. Ez will cause a convent I2 to flow.

Scanned by CamScanner

Wisting the new

ithrough the load. Thus is transformer renables us to transfer a.c. power from one circuit to isnother with is change in voltage devel.

The following points may be noted conefully: (i) The transformer action is based on the laws of electromagnetic induction

- ii) There is no electrical connection between the primary and secondary. The a.c. power is transferred from primary to secondary through magnetic flux.
- iii, There is no change in frequency i.e, output power that the same frequency is the input power.
- (iv) The losses that voccuse in a transformer are:
 a) wore losses uddy current and hysteresis closses.
 b) wopper losses in the resistance of the windings.
 (t) In practice, these losses rare very remain so that .
 (t) sh practice, these losses rare very remain so that .
 (t) sh practice, these losses rare very remain so that .
 (t) sh practice, these losses rare very remain so that .

•

al a state a st

problems on EMF Equ. of a Transformer

Q2 A 2000/200r, 20K the secondary. Calculat and scandary gull-lo	ira t te ()) F ad cu	mary turns (ments . Neglect	s 66 turns in iv primory the losses.
Sil Given Jala $V_1 = 2000V$ $V_2 = 200V$ S = 20KVA	<u>ن</u>)	$\frac{N_2}{N_1} = K$ $\frac{N_2}{N_1} = \frac{N_2 \times 10}{N_1}$	= 66 ×10 = 660 torns
N2 = 66	Ŵ	43=23=-	$\hat{>}$
$K = \frac{V_2}{V_1} = \frac{200}{2000} = \frac{1}{10}$	ί ,	$V_{1} = 20 \text{ KVA}$ $T_{1} = \frac{20 \times 10^{3}}{2000}$ $T_{1} = 10 \text{ A}$	$V_{2} = \frac{1}{2} = \frac{20 \times 10^{3}}{200}$ $T_{2} = \frac{100 \times 10^{3}}{200}$

(1) A Single phase 2200/50, soll 3 transgomer has a
net lire area of 36 cm + a maximum glux density
of 625/mt. Calculate the number of turns of primory
f second dry.
Sol: Given data

$$V_1 = 2200 = C_1$$

 $V_2 = 250 = C_2$
 $f = 50H2$
 $a = 36 cm^2 = 36 \times 10^{6} m^2$
 $B_m = 6 \times 5/m^2$
 $Q_m = B_m \times A = 6 \times 36 \times 10^{6} Y$
 $= 0.0216 \times 16^{4}$
 $M_2 = \frac{E_2}{4.444} M_2 \Phi_m$
 $M_2 = \frac{E_2}{4.444} M_2 \Phi_m$

EMF Equations q a transformer:

Consider that an alternating voltage V, of frequency f is applied to the primory as shown in Fig. The Sinussidal flux of produced by the primory can be supresented as:

9 = & SinNE



The instantaneous $em_{i}^{2} e_{i}$ induced in the printing is $e_{j} = -N_{i} \frac{\partial \theta}{\partial t}$ $= -\lambda_{i} \frac{\partial (\phi_{m} \sin t)}{\partial t}$ $= -\lambda_{i} \phi_{m} \cos t$ $= -\lambda_{i} \phi_{m} \cos t$ $= -\lambda_{i} \phi_{m} \cos t$ $= -2\pi i f N_{i} \phi_{m} \sin(\lambda t - 50^{\circ})$ $= 2\pi f N_{i} \phi_{m} \sin(\lambda t - 50^{\circ})$

It is clear flow the above equation, that maximum value of Induced empine the primary is Emi= 2715 Ng Ang

The nomes value E, of the primery $\frac{E_{m}}{\sqrt{\beta_{-}}} = \frac{2\pi f n_{i}}{1/2} \frac{\phi_{m}}{\phi_{m}}$

E, = 4.44 fr, &m. Volt R2 = 4.44 fr2 dm / Volt

Sim, Tally

Voltage Transgormation Ratio (k)
From the above equations of induced end, we have

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$
The constant k is called Voltage Transformation
gradio.
For an ideal T/F:-
(i) $E_1 = V_1 + E_2 = V_2$ as there is no volky drop in
 $\frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = K$
(ii) There are no losses,
Shart price = outprice
 $y = \frac{V_2}{V_1} = \frac{V_1}{V_2} = \frac{J}{V_1}$

Construction of a Transformer:

Design of a transformer is such that it approaches the characteristics of an ideal transformer.

→ The core is made of silicon steel which has low hysterisis loss & high permeability. Core is laminated inorder to echieve reddy current loss. These features considerably reduce iron losses and no load current.

→ Instead of placing primary on one limb and secondary on the other, it's usual practise to wind one-half of each winding on one limb. This ensures tight coupling b/w two windings. consequently, leakage flux is considerably reduced.

→ Winding resistance R, & R, are minimised to reduce IR MAR loss and resulting rice in temperature & to ensure. high efficiency.

TYPES: Depending upon manner in which primary & secondary are wound on core, transformers are of two types

(i) core-type transformer.

(ii) Shell type transformer

CORE TYPE TRANSFORMER: Half of primary winding & half of secondary winding are placed round each limb. This reduces leakage flux. Generally low voltage winding below the high voltage winding for mechanical considerations.



SHELL-Type TRANSFORMER: Involves use of a double magnetic voircuit. Both windings are placed found central limb. Other two limbs acting simply as a low reluctance path -> Choice of type (either core or shell) will not effect the efficiency of transformer greatly. Core type is generally more suitable for high voltage and small or while shell type is more suitable for row voltage and high output. → Heat is produced in a transformer by iron losses in core § I°R loss in winding to prevent undue temperature rise, heat is removed by cooling. > In small transformer (Below 50 KVA) Natural air cooling is employed. -> Medium size cooling is done by housing them in tanke filled with oil. -> Large transformer, external radiators are added. LV winding HV winding

Three phase Induction Motor (

Working principle of 30 Induction Motor

When a three phase supply is firen to the 3-\$ Stator Winding, a motaling magnetic filld of constant magsitude is produced. The speed of this rotating magnetic zield is synchronous speed, Ng J.p.m.

This notating filld produces an effect of rotating poles around a notor. Let direction of votation of this votating mignetic field is clockwise as shown in Fig.



FISO

NOW at this motor is stationary & State flox RMF is rotating. So its obrious that there easts a relative motion 6/W the RMF & rober conductors, wow the RMF gets Weby rolar Unductors as KMF sweeps over Erder Conductors. Whenever Unductors cuts be zwa, end gets induced in it. So end gus induced in the rolar Conductors called gerter Induced emp. This is electro-magnetic Induction. As noter gorns cluscel circuit, induced lang circulates current krough note called no be correct as shown in Fige


Any current comping conductor produces its orm flox. So rolor produces its zux child notor flox. Por assumed direction of notor corrent, the direction of retar flure is Clockinse as shown in Fig 3. This direction. CAN be easily determined using tright-hand thurs stude. NON there are bro stones, me RMF & other notor flox. Both the flores interact with each as shown in Fig. on left of rotor Undullal, two shores are in Some direction hence add up to get high flux area on gright side, two Stures Cancel each other to produce low flor orea. As flux lines alt as strucked rubber band, Ligh flux density area exists a push in notor conductor towards low flux desiry area so notion conductor experiences a zorce zum left to night in this Case as shown in the Rig D due to interaction of the two flores. As all be notor conductors experience a Zorce, the overall rolor experiences à taque & Starts Rotating . NS = Speed of rotating magnetic field in rom 80, N = Speed of rotal i.e. motor in rom NS-N = Relative Speed b/w he two ", Rolar always notates in some direction as that of RMF. Ship of Induction Motor :-Ship of Induction motor is defined as the difference. We be synchronous speed (NS) & actual speed of rolor 1. l. motor (N) expressed us a graching of the sym. Speed NS. This is also called absolute slop a praching Ship of is denoted as 's $S = \frac{N_{S} - N}{N_{S}}$

Scanned by CamScanner

QI) A 4 pole, 3-& Induction motor is Supplied Jon SOHZ Supply. Extermine its synchronors speed. on ZUII Load, its speed is obscured to be 1410 oppos. Caludate its ZUII load ship.

bol Given data P=4, f=50H3, N=1410 mm. $N_{S} = \frac{120f}{p} = \frac{1200 \times 50}{9} = 1500 \text{ Spin}.$ $S = \frac{N_{S}-N}{N_{S}} = \frac{1500-1410}{1500} = 0.06.$ 1/5 = 0.06×10 = 6%

Rotor current Frequency: For a notor speed N, the relative speed the the notating jun + the notor is No -N. Consequencity of is is given weathy, the noton current grequencity of is is given f = SfSame Land Contra

(2) A 3-phase Induction motor is wound for: 4. poles and is supplied from so H3 system. Calculate is the synchronors speed (i) the speed of the motor when slip is 4%. (iii) the notor current grequency when the motor nuns at 600mm.

Shiren dala

$$p=4$$
 poles
 $f=50HR$
(i) $M_S = \frac{120f}{g} = \frac{120\times50}{4} = 1500 \text{ rpm}$
(ii) $S=4Y$. then $S = \frac{M_S-M}{4} \times 160$
 $h = \frac{15m-M}{1500} \times 160$
 $f=1.N-1440 \text{ rpm}$

(i) when N = 600 rpm, then $S = \frac{NS-N}{N_s}$ $S = \frac{15N-610}{1510} = 0.6$ $i \cdot f = Sf = 0.6 \times 50$ = 30H3

Scanned by CamScanner

and a cardina :-(03) A 6-pole allemator summing at 1000 rpm. Supplies an 8 pole Induction motor. Find the actual speed of the. motor 12 be slip is 25%. 64) The frequency of 3-& Supply ged to be Faduction motor is determined germ be speel of the alternation and it's number of polls. . Supply grequency, f= NP = Unox6 = 50HQ. (i) $N_S = synchronons sped = \frac{120f}{p} = \frac{120\times 50}{8} = 750 \text{ rpm}.$ $S = \frac{N_S - N}{N_c} \times 100$ 9 * 1 j 🕐 2.5 = 750-N×160 750 N=731,25 rpm (by) A SOHZ 4-pole, 3-\$ Induction motor has a rotar correre grequency 2HZ: Actensive i) be slip and (i) speed of the motor. (ii) speed of the motor (N) Solir Girm date f=50+12 Ng = 120f = 1200150 P = 4 1'=2HZ = |Svo r.p.m. P=4 11) S=NS-N NS (i) f=sf $S = \frac{4}{T} = \frac{2}{50} = 0.64 \textcircled{0}4\%$ 0.04 = 1500-N N=1440 rpm

Scanned by CamScanner

CONSTRUCTION:



→ The states is made up of a no. of stampings with alternate slot & tooth. stamping are insurated from each other. No. of stampings are stamped togenther to succest shuild stater core.

 \Rightarrow Stater core is then fitted in a casted or fallericated stall frame. Slots have the $3-\phi$ winding just like $3-\phi$ alternator. $3-\phi$ winding is called stater winding



ROTOR :

-> Two types of rotols are used in induction motor squirrel cage & slip ring. SQUIRREL CAME ROTOR:



> This is made of cycindrical commated core with slots to carry solor conducte Roter conductors are heavy bass of copper or aluminium short circuited at Both ends by end sings Hence called as short circuited rotor.

- -> Homes gntise gotol sozietance is very snall. External soziestance cannot be connected in sole circuit. such notes are extremely sugged in construction. notes using such soles are called squissel cage induction notes. majority of induction notes. are squissel cage roles. APPLICATIONS:
 - -> squierel cage induction notoes are used in lathos, doubling machines, fans, Blowers, water pumps, grinders, printing machines etc.

Scanned by CamScanner

E)

Aduantages: of squined (age Rotor

- 1 cheaps.
- 2. sight awight.
- 3. Rugger construction (strong).
- 4. higher ensidency.
- 5. requiers less maintenenance
- 6. It can lie apprated in disty & explosive environment.

Disaduantages:

- 1. moderate starting toque.
- 2. External roustance cannot be connected to rotor ciecult. so starting tarque connot be controlled.



-> In this type of rotor, rotor windings are similar to stater winding. Rotor winding may be star or delta connected, distributed winding, wound for as many no. of poles as stater.

-> 3-\$ are borrow Brought out & connected to slip rings mounted on rotor shaft. Voriable eatomal resistance can be connected in rotor circuit, with the help of Brushes & slip ring arrangements.

-> By varying external resistance in rotor circuit, motor speed & toloque can

be controlled.

APPLICATION: -> slip sing induction notors are employed only user speed control or high starting torque is sequired. Examples are lists, horists, cranes, elevators, compresses ate.

.(2)

P-N junctim biode: 4-1 -> It is gormed by too blocks of semiconductor material, one of p-type material + other is n-type material. -> On p-region holes are majority carriers and electrons are minority corners. > In N-type negion holes are minority carriers & electrons are majority carriers. > In P-type negion holes are represented by small circles + in noregin electrons are represented by dots. > Since the concentration of electrons in n-negion is more Compared to p-side, Free electrons from n-side dizzuses across the junction & gill the holes on p-side. > Diguision is a natural process through which charges glow from higher to lower concentration until the diggeneric in Concentration is eliminated. -> Similarly, lose holes from p-side dizzuse across junction + recombine with electrons in miside. - The free electrons that cross junction create positive ins on N-side. Similarly diffusion of holes in the pomatorial creakes negative ions. -> Since negative ions are created on proide of junction, the region close to junction acquires negative charges. Similarly positive ims created on n-side give a positive charge near junction. N-type. P-type 0.000.0 t, to t t t > election Holes E 0 0 0 0 0 0 0 0 0 0 0 0 , + t + of + > Donor ot ot ot ot ot atons Accepter N-matchial P-material alons P-type N-WPC 0000 00000 1 1 0000 0000 PN junction (Depletion region)

E	4-2
Formation of septetion Region:	indicat new
In p-n iversion there exist a concentration J	
junction.	very Sarall
-> There are large no. of holes on p-side white	s start
no. of holes on n-side near junchan. only	con lestabon
moring from p-side to n-side 1.2.	, ie
this is diffusion.	pside ic,
-> Similarly electrons Starte moning	The
high to low concentration they hind no. of don	or atoms of
As holes enter noregion engrations. As demor al	ens Like
holes recombine with courses positively charged	m mer
additional sorres englished	
1028.	acceptor
As electrons cher precombine with acceptor a	Lecones
alcenter atoms accept additional electrons to	ny see
negatively changed immobile 10mb.	
As more no. of holes dizzuse on n-side Lorge po.	Shre Charge
accumulated on n-side near junchim.	all prepelled
> The diffusing holes which are positively changed	+ the diffusion,
due to accumulated positive charge on norme	,
of holes stops.	e negebre
As more no. g elections diffuse on prove, mg	junction.
chorge gets accumulated on prode ment	+ monelled
> The diffusing electron's which are -vely charged g	1'221600 7
due to acconviate negative charge on piside + a	260000000
electrons stop.	1. When
this in themal equilibrium, in the region new	L'Ge Juncing
there exist a wall of -ve immosile charges on	p-side 7
wall of the immobile changes on side.	
> In this region, there are no. mobile charges	carriers, Such
a region is depicted of the gree mobile charge	- camiels +
hence called depletion region (or) depletion	ayor
> an equilibrium condition the dedition measures &	els Lodered
upper a print where no worker electrons (3) ho	les Lan
(2000 be junction, Thus depletion negion allo a	Barner
	(commo

> News the junction, one one side there are many positive charges on other side there are many positive Charges, on other side there are many negative charges > According to coulomb's Law, there exist a golie 6/2 these opposite charges. And this zone produces an electric field 6/4 the charges. The direction of electric field is from positive to negative. > The opposite changes existing near the junction creates a pokential difference across the junction. > This potential difference has a gized polarity & it acts as a barrier to the glow of electrons + holes, across the > Hence, this potential is called barrier potential, Junchin potential or builterin potential barrier of a p-re junction the set of the set of the set of the set of the a she and an and and a start of and the share of the second states of the 12.00 a new production for the state of the strength Anode Callode N- type.

Bialing & P-N junction Diode: Applying enteend Dc voltage to any electronic denices is called Bialing Applied to ite, the polarity of the Dc voltage enternally Applied to ite, the biasing is classified as golword biasing + Reverse biasing
Forward biased P.N junction: 4-4
When an external potential 'V' is applied across the p-N when an external potential 'V' is applied across the p-N junction such that the positive terminal is connected to pitype material + negative material is connected to pitype material then the disde is said to be gorward biand N-type material then the disde is said to be gorward biand N-type material then the disde is said to be gorward biand N-type material then the disde is said to be gorward biand N-type material then the disde is said to be gorward biand N-type material then the disde is said to be gorward biand N-type material then the disde are supelled by the -ve
> Similarly, the electors in more towards the junction. Eleminals of the balkery + more towards the junction.
The electrons & holes that are with boundary & reduce hidth of depletion green on
> The reduction in width of depletion layer reduces the barrier potential.
> 92 the applied voltage is increased zurber, a serpens preached where the barrier potential effectively disappears I charge cansers can easily zers across the junction.

Reverse Binsed PN junction;

1254 30

→ 9% an enternal potential V is applied across the pN junction that the positive terminal of diode its connected to in-side material + negative material its connected to pside material, then the diode said to be verense biased



> The neverse bias gorces gree electrons in the n-negion to more away gran the junction towards the terminal. Thise electrons leave more positive ions near the junction

> Similarly, the holes in the p-side also more away from the junction towards negative terminal of the battory,

These holes leave more negative ims near the junction -

As a nesule the tridter of the depletion region increases. The greater the neruse bias, the tride the depletion layer. This increases in the tridth of depletion region effectively reduces the majority camer flow.

- > Hovever due to themal energy dimited no. 9 gree electrons + holes are generated in p-side + N-side of pN junction suspectionly.
- > Electrons in p-side more towards right + cross the junction + holes in n-side more towards left & cross the junction.

> The movement of Minority carriers constitute a current known as "muruse saturation current". It is denoted by "Ico".

Hence Ico is due to thermally generated mimority tarries if it hall not increase with increase in neverse voltage. gt increase with increase in temperature.

> Normally Ico doubles gor every loc rise in temperature. The neverse Saturation current to is typically tes than IMA gor Silicon, while gor germanium it may exceed IOMA. Breakdown Voltage:

-> 32 the Reverse biased voltage is increased, the velocity of minority charge carriers crossing the junction increases. -> The greater the newse bias the gaster the electron movement. - Since velocity increased, the associated, kinetic energy (1/2 mrz) also increases -> When these camiers with high trincic energy collide with atom the valence electron in the atom absorbs sufficient energy + leave the parent stom. > These additional carriers also jet suggicient energy from the applied neverse bias & collide with other atoms 4-6 + generate some more carriers. His Collision + generation of corners is a cumulative effect Which results in large amount of reverse current. -> This phenomena, Know as neverse breakdown occurs at particular neverse voltage zor a p-N junchim .- This a Voltage is known as "Reverse Breakdown voltage." Bias A, velocity A, KEA High Atom elector > Collide Lity oker atoms No No V Collide genuchin of carriers Collision + generation = large revene and the second second 135 6 14

Voll-ampore characteristics of a triode (V-I characteris 60):-

The suspense 2 a diode when connected in an edubital Circuic, can be budged gram its characteristics known as voltampore commonly called V-I chars.

→ The V-I characteristics in the golward biased & Reverse biased condition is the graph of voltage across the diode against the diode current.

(b) CKE diagram to obtain zorward bias.

- The circuit diagram to obtain the v-Ich's of the diode at . - Shown in tig.

- ->. It consists of a dc voltage source & a resistor connected in
- . . . Series with a diode.
- > The desigeog is used to limit the torward current to a value that will not over heat the diode trause damage.
- -> An ammeted is Connected in Series with the diode to measure the diode current ID & voltmeter is connected across the diode to measure voltage across it.
- -> By varying the dc voltage source the voltage VD across the diode and current ID through the diode can be measured.
- When the applied Voltage is zero, the Voltage across the diode remains zero; hence there is no togiciand current.
- > When the applied voltage increased gradually, the borward current & the voltage across the diode gradually increase.
- → When applied Voltage increases to a value which increases the voltage across diode to barrier potential (0.7V tor silicon, 0.3V tog gegmanium), the tograard current begins to increase slapidly.

→ We can see that bosward current is very low until the Voltage across p-n Sunction reaches approximately 0.7V. Atten this point the current If increase rapidly. But to bostward voltage semains at 0.7V.



- -> TO bind VI ch's of a diode in reverse bias, we simply reverse the position of diode as shown.
- -> The Reverse bias increases baom zero, a Smaller reverse saturation Ourrent blows through the diode 4 the voltage across the diode increases.
- -> When the applied reverse bias reaches a certain Value, a reverse avalanche breakdown would occur, then the magnitude of the current increases rapidly as shown. 4-8.
- > This voltage at which the diode current increases rapidly is . known as reverse breakdown Voltage.



2.4. Diode Current Equation

The mathematical equation, which describes the forward and reverse characteristics of a semiconductor diode is called the diode current equation.

Let *I* = Forward (or reverse) diode current,

 I_{RS} = Reverse saturation current,

- V = External voltage (It is positive for forward bias and negative for reverse bias),
- $\eta = A \text{ constant}$
 - = 1 for germanium diodes, 2 for silicon diodes for relative low value of diode current (i.e., at or below the knee of the curve)
 - = 1 for germanium and silicon for higher levels of diode current (i.e., in the rapidly increasing section of the curve), and

 $V_T =$ Volt-equivalent of temperature. Its value is given by the relation, $\frac{T}{11600}$,

where T is the absolute temperature

= 26 mV at room temperature (300 K).

For a *forward-biased diode*, the current equation is given by the relation,

$$I = I_{RS} \left[e^{V/(\eta \times V_T)} - 1 \right]$$

Substituting the value of $V_T = 26 \text{ mV}$ or 0.026 V (at room temperature) in eqn. (i), we get $I = I_{RS} \ (e^{40V/\eta})$

: Diode current at or below the knee, for germanium,

$$I = I_{RS} (e^{40V} - 1) \qquad (\because \eta = 1)$$
$$I = I_{PS} (e^{20V} - 1) \qquad (\because \eta = 2)$$

...(i)

1)

and, for silicon, $I = I_{RS} \, (e^{20V} - 1)$

When the value of applied voltage is greater than unity (i.e., for the diode current in the rapidly increasing section of curve), the equation of diode current for germanium or and silicon, $I = I_{RS} \cdot e^{20V}$ $(:: \eta = 2)$

The current equation for a reverse biased diode may be obtained from eqn. (i) by changing the sign of the applied voltage (V). Thus the diode current for reverse bias,

$$I = I_{RS} \left[e^{-V/(\eta \times V_T)} - 1 \right]$$

When $V >> V_T$, then the term $e^{-V/(\eta \times V_T)} << 1$. Therefore $I = I_{RS}$. Thus the diode current under reverse bias is equal to the reverse saturation current as long as the external voltage is below its breakdown value.

Example 1. The current flowing in a certain P-N junction diode at room temperature is 1.8×10^{-7} A, when large reverse voltage is applied. Calculate the current flowing, when 0.12 V forward bias is applied at room temperature.

Solution. Given : I_{RS} = 1.8 \times 10^{-7} A ; V_{F} = 0.12 V

The current flowing through the diode under forward bias is given by,

or

 $I = I_{RS} (e^{40V_F} - 1)$ $I = 1.8 \times 10^{-7} (e^{40 \times 0.12} - 1) = 21.69 \times 10^{-6} A = 21.69 uA.$ (Ans.)

Example 2. Determine the germanium P-N junction diode current for the forward bias voltage of 0.2 V at room temperature 24°C with reverse saturation current equal to 1.1 mA. Take $\eta = 1$. **Solution.** Given : $V_F = 0.2 \text{ V}$; T = 24 + 273 = 297 K; $I_{RS} = 1.1 \text{ mA} = 1.1 \times 10^{-3} \text{ A}$; $\eta = 1$

We know that, $V_T = \frac{T}{11600} = \frac{297}{11600} = 0.0256 \text{ V} (i.e., 25.6 \text{ mV})$

$$\therefore \text{ The diode current,} \qquad \mathbf{I} = I_{RS} \left[e^{V_F / (\eta \times V_T)} - 1 \right]$$

= $1.1 \times 10^{-3} [e^{0.2/(1 \times 0.0256)} - 1] = 2.717$ A. (Ans.)

I = winde erhouse 1) A silicon diode has a reverse saturation current of 7.12 nA at room temperature of arc. calculate its borward current it is bosward blased with a voltage of orivi

Soli- Geven data,

$$I_0 = T \cdot I \ge nA = T \cdot I \ge \times I0^9 A$$

 $V = 0 \cdot Tv$
 $Q = 2 \text{ bog silicon diode}$
 $T = 27^{\circ} = 27 \cdot 273 = 300^{\circ} K$
NOW $V_T = KT = 8 \cdot 62 \times 10^5 \times 300 = 0.026V$
Accossing to diode : Custont equ
 $I = T_0 \left[e^{V | n \cdot V_T - 1} \right]$
 $I = T_4 \ge \times 10^9 \left(e^{0.97 / 2 \times 0.026} - 1 \right)$
 $I = 5 \text{ mA}$

2) The voltage across a silicon deade at room temperature of () 300 K 39.0.71V when 2.5mA current thous through it. It voltage increases to o.gv, calculate new clide current! 4-9 Jol --

Guven data,

AL 300%, VT= 26MV = 26x103V

The current equ of a dlode is

$$I = I_0 \left(e^{V | \eta_V r} \right)$$

$$\frac{Q \cdot 5 \times 16^3 = I_0 \left(e^{(0 \cdot 71) / 2 \times 2.6 \times 16^3} \right)}{I_0 = Q \cdot 9 \times 10^9 A}$$

$$N_0 \iota_0, V = 0.8 V$$

$$I = 2 \cdot 9 \times 10^9 \left(e^{0 \cdot 6 / 2 \times 2.6 \times 16^3} \right)$$

$$I = 2 \cdot 9 \times 10^9 \left(e^{0 \cdot 6 / 2 \times 2.6 \times 16^3} \right)$$

$$I = 14 \cdot 1100A$$

1 14.

Effect of temperature on PN junction diode.

- PN junction diode parameters like cut in voltage, forward current in the forward bias and reverse current, reverse breakdown voltage and reverse saturation current in the reverse bias are dependent on temperature.
- The current that a PN junction diode can conduct at a given voltage is dependent upon the operating temperature. An increased temperature will result in a large number of broken covalent bonds increasing the large number of majority and minority carriers. Rise in temperature generates more electron-hole pair thus conductivity increases and thus increase in current. This amounts to a diode current larger than its previous diode current. The above phenomenon applies both to forward and reverse current.
- Mathematically diode current is given by

$$I = I_{RS} \left[e^{V/(\eta \times V_T)} - 1 \right]$$

Hence from equation we conclude that the current should decrease with increase in temperature but exactly opposite occurs, there are two reasons:



Effect of temperature on avalanche diodes

Forward bias region :

- The effect of increased temperature and decrease in temperature on the forward characteristics curve of a PN junction diode is as shown in above figure. It may be noted that the forward characteristics of silicon diode shift to the left at rate of 2.5 m V per centigrade degree increase in temperature and shift towards right at rate of 25 m V per centigrade degree decrease in temperature.
- The cut-in voltage decreases as the temperature increases. The diode conducts at smaller voltage at large temperature.
- The cut-in voltage increases as the temperature decreases. The diode conducts at larger voltage at lower temperature.

Example:

At 25° C $V_D = 0.7V$ for 100° C Rise in temp. i.e., at 25+100=125°C now we will find new V_D at 125° C then 100*2.5mV =0.25 V the new V_D will be reduce by 0.25 V therefore new $V_D = 0.7$ - 0.25= **0.45 V** At 25° C $V_D = 0.7V$ for 100° C decrease in temp. i.e., at 25-100= -75°C now we will find new V_D at 75° C then 100*2.5mV =0.25 V the new $V_D = 0.7$ - 0.25= **0.45 V** therefore new $V_D = 0.7$ + 0.25= **0.95 V**

Reverse bias region:

- The effect of increased temperature and decrease in temperature on the reverse characteristics curve of a PN junction diode is as shown in above figure. It may be noted that in the reverse bias region characteristics reverse current of silicon diode shift downwards with the increase in temperature and shift upward with decrease in temperature.
- > In the reverse bias region the reverse current of diode doubles for every 10°C rise in temperature.

. Example:



Therefore for 100° C Rise in temp. i.e., at 25+100=125 °C the reverse saturation current increases to greater than 10nA

For 100° C decrease in temp. i.e., at 25-100 = -75°C the reverse saturation current reduces to less than 10nA

Static and Dynamic Resistance of a Diode

Static forward resistances $(\mathbf{R}_{\mathbf{F}})$. A diode has a definite value of resistance when forward biased. It is given by the *ratio of the D.C. voltage across the diode* to *D.C. current flowing through it.*

Mathematically,
$$R_F = \frac{V_F}{I_F}$$

 R_F may be obtained graphically from the diode forward characteristics as shown in Fig. : From the operating point P, the static forward resistance,

$$R_F = \frac{0.8}{16} = 0.05 \ \Omega.$$

Dynamic or A.C. resistance. In practice we don't use static forward resistance, instead, we use the dynamic or A.C. resistance. The A.C. resistance of a diode, at a particular D.C. voltage, is *equal to the reciprocal of the slope of the characteristic at that point ; i.e,* the A.C. resistance,

$$r_{\text{A.C.}} = \frac{1}{\Delta I_F / \Delta V_F} = \frac{\Delta V_F}{\Delta I_F} = \frac{\text{Change in voltage}}{\text{Resulting change in current}}$$

Owing to the non-linear shape of the forward characteristic, the value of A.C. resistance of a diode is in the range of 1 to 25Ω . Usually it is *smaller than D.C. resistance of a diode*.

Reverse resistance. When a diode is *reverse biased*, besides the forward resistance, it also possesses another resistance known as *reverse resistance*. It can be either D.C. or A.C. depending upon whether the reverse bias is direct or alternating voltage. Ideally, the reverse resistance of a diode is infinite. However, in actual practice, the reverse resistance is never infinite. It is *due to the existence of leakage current* in a reverse biased diode.



esistances of a diode from the characteristic curve.

Ideal Diode and Practical Diode

Ideal Diode	Practical Diode
1)A diode is said to be an Ideal Diode when it is forward biased and acts like a perfect conductor, with zero voltage across it. Similarly, when the diode is reversed biased, it acts as a perfect insulator with zero current through it.	1)A Practical diode contains barrier potential V_0 (0.7 V for silicon and 0.3 V for Germanium) and a forward resistance R_F of about 25 ohms. When a diode is forward biased and conducts a forward current I_F flows through it which causes a voltage drop I_FR_F in the forward resistance. Hence, the forward voltage V_F applied across the Practical diode for conduction, has to overcome the following. (i) Potential barrier (ii) Drop in forward resistance i.e., $V_F = V_0 + I_FR_F$
2) When the Ideal diode is forward biased it acts like a closed switch as shown in the figure below. An Ideal diode also acts like a switch	2)The equivalent circuit of the Practical diode under forwarding bias condition is shown below. This circuit shows that a Practical diode still acts as a switch when forward biased, but the voltage required to operate this switch is V_F
Ideal Forward Biased Forward Biased Closed Switch Closed Switch	Real V _F V _O R _F Forward Biased
Diode resistance is zero i.e., R _D =0 from ohms law V _D = I _D R _D Therefore V _D =0	$V_F = V_0 + I_F R_F$
3) Where as, if the diode is reversed biased, it acts like an open switch as shown in the figure below. Ideal Reverse Biased Diode resistance is infinity i.e., $R_D = \infty$ from ohms law $V_D = I_D R_D$ Therefore $,I_D = 0$	3)For all the practical purposes, a diode is considered to be an open switch when reversing biased. It is because the value of reverse resistance is so high ($R_R > 100 \text{ M}\Omega$) that is considered to be an infinite for all practical purposes. Reverse Biased Open Switch
4) The V-I characteristics of the Ideal diode are shown in the figure below	4) The V-I characteristic of the Practical diode is shown below. $ \begin{array}{c} $

Equivalent Diode Circuits

An equivalent circuit is nothing but a combination of elements that best represents the actual terminal characteristics of the device. In simple language, it simply means the diode in the circuit can be replaced by other elements without severely affecting the behavior of circuit.

The diode can be modeled in three different ways depending on the accuracy required. Three models with increasing accuracy are listed below:

- 1. Ideal Diode Equivalent Circuit:
- 2. Constant voltage drop (or) Simplified Equivalent Circuit
- 3. Piece-Wise Linear Equivalent Circuit

1. Ideal Diode Equivalent Circuit:

Figure indicates that the voltage drop across the diode is zero for any value of diode current. The ideal diode does not allow any current to flow in reverse biased condition. The current flowing through the diode is zero for any value of reverse biased voltage. Taking this into consideration, the ideal diode can be modeled as open or closed switch depending on the bias voltage.

- a) Ideal diode allows the flow of forward current for any value of forward bias voltage. Hence, Ideal diode can be modeled as closed switch under forward bias condition. This is shown in the figure.
- b) Ideal diode allows zero current to flow under reverse biased condition. Hence it can be modeled as open switch. This is indicated in the figure.



2. Constant Voltage Drop (or) Simplified Equivalent Circuit

The equivalent circuit in this case consists of a battery and an ideal diode. Consider the horizontal line from (0 to 0.7 V) in the curve. The horizontal line indicates that the current flowing through diode is zero for voltages between 0 and 0.7 V. To model this behavior, we put a battery of 0.7 V in the equivalent diode model. This does not mean that diodes are a source of voltage. When you measure the voltage across an isolated diode, the instrument will show zero value. The battery simply indicates that it opposes the flow of current in forward direction until 0.7 V. As the voltage becomes larger than 0.7 V, the current starts flowing in forward direction.



3. Piece-Wise Linear Equivalent Circuit

The piece-wise linear circuit, as the name suggests, is a model in which the characteristics of diode is approximated by "piece-wise linear" line segments. Now consider the straight line in the piece-wise linear characteristics. This straight line indicates constant slope. Slope in the V-I graph indicates resistance. So we add a resistor in the diode model. The value of resistance can be found from the graph. We can see from the graph that the diode current changes from 0 to 15 mA for a voltage change from 0.7 to 0.8 V. Thus the average value of resistance is (0.8 V-0.7 V)/(15 mA - 0 mA) = 6.67 Ω . Thus the value of resistance in the equivalent model is approximately 6.67 Ω . The figure given below shows piece-wise linear characteristics of diode along with its model.



In the graph shown on left, the actual characteristics of diode is superimposed by piece-wise linear characteristics (shown in amber color). It is clear that the piece-wise linear characteristics do not exactly represent the characteristics of diode, especially near the knee of the curve. However it provides a good first approximation to the actual characteristics of the diode. Piece- wise linear characteristics can be obtained by replacing the diode in the circuit with a resistor, a battery and an ideal diode. This is shown in the right side of the above figure.

Energy band diagram

is higher than conduction band edge Ecp in p-type.

-> Gimilarly, the valence band edge Evp in the p-type material is highest than valence band edge Evn in the n-type.

> EI & E2 indicates shibt in berni level from intrinsic conditions in p& n type materials.

> Then total shift in energy level to is given by Eo= EI+E2

= Ecp-Ecn (conduction band)

= Evp- Evn (Valence band)

ED= EI+E2= ECP-ECD= EVP-EVD

-> This energy Eo (in ev) is potential energy of the electrons at p-n sunction, fis equal to vo, where vo is contact potential (in Volt), or contact diff of potertial of barrier potential.

Space charge of Transition capacitance (CT):consider a reverse, biased p-n sunction diode as W= width of depletion region . p-region, Shown. マシ 1001001 30100 00100 DOIDE DO the notifier would write splatel i Dielectrict HCT. 343 1-4 (1 V (Reverse bias Vollage). > As seen earlier, When a diode is reverse biased, reverse currents Hows due to minorty conniers. > Masorily charged particles ie, electrons in n-region thole in p-region more away brom sunction. > This increases width of depletion region. > The width of depletion region increases as reverse bias Voltage Increases. -> As the charged particles move away brom the sunction there exists a change in charge w.r.to applied reverse vollar > so change in charge da with respect to the change in Voitage du is nothing but a capacitive effect. -> Such a capacitance which comes in to picture under reverse biased condition is called "Transition capacitance, Space-Charge Capacitance, barster capacitance " Or depletion layer capacitance" Edenoted as CT. The magnitude of CT is given by the CT= dQ equ, This Capacitance is very impostant as it is not constant but depends on magnitude of reverse voltage. 4-13 if the width of depletion region then the transition

· · Capacitance is

1100

CT=EA W

Where, A= Area of cross_section of Sunction E = permiterity of semiconductors.

Diffusion capacitance (CD:-(03) storage capacitance:-

- -> During torward blased condition, an another capacitance comes in to exist called "diffusion capacitance" or "storage capacitance", denoted as "Co."
 - -> An borward blased condition, the width of depletion region decreases & holes from p-side get dittused in n-side while electrons move brom n-side to p-side.
- -> As applied voltage increases, concentration of insected charged particles increases.
- -SThis rate of change of insected charge with applied vollage is defined as a capacitance called diffusion capacitance.

· CD=da

-> The dibbusion capacitance can be determined by the expression

 $CD = \underline{TT}$ where, $T^{e} = Mean$ life time for holes. \underline{NT}

dia las

-> 50 diffusion capacitance is proportional to current. Fog tosward biased condition, the value of diffusion capacitance is of the osdes of nono tarads to microtarads cohile transition capacitance is of the order of pico farads. so, CD 93 much larges than CT.

Power and Current Ratings of a Diode

The power dissipation for a forward biased diode is given by,

$$P_{DF} = V_F \times I_F$$

where, P_{DF} = Power dissipated by the diode,

 $V_{\it F}=$ Forward voltage drop, and

 $I_F =$ Forward current.

Similarly, power dissipation for a reverse biased diode,

 $P_{DR} = V_R \times I_R$

where, $V_R =$ Reverse voltage drop, and

 I_R = Reverse current.

The maximum value of power, which a diode can dissipate without failure, is called its **rating**. Thus the power dissipation should not exceed power rating in any case, otherwise the diode will get destroyed.

The diode manufacturers more oftenly list the maximum current, which a device can handle, (called *current rating*), rather than power rating. It is because of the fact that it is *easy to measure current rating than power rating*.

Applications of a Diode

An important characteristic of the *P*-*N* junction diode that it conducts well in forward direction and poorly in reverse direction has made it useful in several applications listed below :

1. As zener diodes in voltage stabilizing circuits.

2. As rectifiers or power diodes in D.C. power supplies.

3. As a switch in logic circuits in computers.

4. As signal diodes in communication circuits.

5. As varactor diodes in radio and T.V. receivers.

6.P-N junction forward bias condition is used in all LED lighting applications

7. The voltage across the **P-N junction** biased is used to create Temperature Sensors, and Reference voltages.

ZENER DIODE

A properly doped P-N junction crystal diode which has a sharp breakdown voltage is known as Zener diode.

The voltage-regulator diode is commonly called a **'Zener' diode**. It is a voltage limiting diode that has some applications in common with the older voltage-regulator gas tubes but serves a much wider field of application, because the devices cover a wide spectrum of voltages and power levels.

Performance/Operation

The electrical performance of a zener diode is based on the *avalanche characteristics* of the *P-N* junction. When a source of voltage is applied to a diode in the *reverse direction* (negative to anode), a reverse current I_R is observed (see Fig. ⁻⁻). As the



reverse potential is increased beyond the "Zener knee" avalanche breakdown becomes well developed at zener voltage V_Z . At voltage V_Z , the high counter resistance drops to a low value and the junction current increases rapidly. The current must of necessity be limited by an external resistance, since the voltage V_Z developed across the zener diode remains essentially constant. Avalanche breakdown of the operating zener diode is not destructive as long as the rated power dissipation of the junction is not exceeded.

Externally, the zener diode looks much like other silicon rectifying devices, and electrically it is capable of rectifying alternating current.

The following points about the *Zener diode* are worth noting :

 $(i) \mbox{ It looks like an ordinary diode except that it is properly doped so as to have a sharp breakdown voltage.$

(ii) It is always reverse connected *i.e.*, it is always reverse biased.

(iii) It has sharp breakdown voltage, called Zener voltage V_Z .

(iv) When forward biased, its characteristics are just those of ordinary diode.

(v) It is not immediately burnt just because it has entered the breakdown region (The current is limited only by both external resistance and power dissipation of Zener diode).

- The location of Zener region can be controlled by varying the doping levels. An *increase in doping, producing an increase in the number of added impurities, will decrease the Zener potential.*
- Zener diodes are available having Zener potentials of 1.8 to 200 V with power ratings

from $\frac{1}{4}$ to 50 W. Because of its higher temperature and current capability, silicon is usually

preferred in the manufacture of Zener diodes.

. Equivalent Circuit of Zener Diode

The complete equivalent circuit of the Zener diode in the Zener region includes a small dynamic resistance and D.C. battery equal to the Zener potential, as shown in Fig. :



Fig. Zener equivalent circuit : (a) Complete ; (b) Approximately.

"ON" state. When reverse voltage across a Zener diode is equal to or more than breakdown voltage V_Z , the current increases very sharply. In this region curve is almost vertical; it means that voltage across Zener diode is constant at V_Z even though the current through it changes. Therefore, in the breakdown region, an ideal Zener diode (this assumption is fairly reasonable as the impedance of Zener diode is *quite small in the breakdown region*) can be represented by a battery of voltage V_Z as shown in Fig. (b). Under such conditions, the Zener diode is said to be in the "ON" state.



Fig. :

"OFF" state. When the reverse voltage across the Zener diode is less than V_Z but greater than 0 V, the Zener diode is in the "OFF" stage. Under such conditions, the Zener diode can be represented by an open circuit as shown in Fig. (b).



3.3. Applications of Zener Diode

Zener diode serves in the following variety of applications :

1. Voltage reference or regulator element :

The primary use of a zener diode is as a voltage reference or regulator element. Fig. 22 shows the fundamental circuit for the Zener diode employed as a shunt regulator. In the circuit, diode element and load R_L draw current through the series resistance R_S . If E_{in} increases, the current through the Zener element will increase and thus maintain an essentially fixed voltage across R_L . This ability to maintain the desired voltage is determined by the temperature coefficient and the diode impedance of the zener device.



 R_{S} = Series resistance,

 R_{r} = Load resistance

Fig. 22. Basic Zener-diode regulator circuit.

2. Shunt transistor regulator :

The Zener diode may also be used to control the reference voltage of a transistor regulated power supply. An example of this in a shunt transistor regulator is shown in Fig. 23, where Zener element is used to control the operating point of the transistor. The advantage of this circuit over that shown in Fig. 22 are *increased power* handling capability and a regulating factor improved by utilizing the current gain of the transistor.



Fig. 23. Shunt transistor regulator.

3. Audio or r-f applications :

The Zener diode also finds use in audio or r-f (radio frequency) applications where a source of stable reference voltage is required, as in bias supplies. Frequently, Zener diodes are connected in series package, with, for example, one junction operating in the reverse within a single direction and possessing a positive temperature V_Z coefficient; the remaining diodes are connected to operate in the forward direction and exhibit negative temperature V_Z coefficient characteristics. The net result

is close neutralization of V_Z drift versus temperature change ; such reference units are frequently used to replace standard voltage cells.

4. Computer circuits :

Zener diodes also find use in *computer circuits designed for switching about the avalanche* voltage of the diode. Design of the Zener diode permits it to absorb overload surges and thereby serves the function of protecting delicate circuitry form overvoltage.

- The usual voltage specifications V_Z on Zener diodes are 3.3 to 200 V with \pm 1, 2, 5, 10 or 20% tolerances.
- Typical power dissipation ratings are 500 mW, 1, 10 and 50 W.
- The temperature coefficient range on V_Z is as low as 0.001% °C.

Example 4. Determine the current flowing through the Zener diode for the circuit shown in Fig. 24, if $R_L = 4000 \Omega$, input voltage is 50 volts, $R_S = 1800 \Omega$ and output voltage is 32 volts.



Fig. 24

Solution. Input voltage, $V_{in} = 50 \text{ V}$ Output voltage, $V_{out} = 32 \text{ V}$ Voltage drop in series resistor, $R_S = V_{in} - V_{out} = 50 - 32 = 18 \text{ V}$ Current through series resistance, $I = \frac{V_{in} - V_{out}}{R} = \frac{18}{1800} = .01 \text{ A or } 10 \text{ mA}$

Load current,
$$I_L = \frac{V_{out}}{R_L} = \frac{32}{4000} = 0.008 \text{ A or } 8 \text{ mA}$$

Current through Zener diode, $I_Z = I - I_L = 10 - 8 = 2 \text{ mA.}$ (Ans.)

Example 5. Determine the maximum and minimum values of Zener current if in the circuit shown in Fig. 24 the load resistance, $R_L = 4000 \Omega$, series resistance = 8000 Ω , output voltage = 32 V and source voltage varies between 100 V and 128 V.

 $\begin{array}{ll} \mbox{Solution. Refer to Fig. 23. } Given: & R_L = 4000 \ \Omega \ ; R = 8000 \ \Omega \ ; V_{out} = 32 \ {\rm V} \ ; \\ \mbox{Load current,} & I_L = \frac{V_{out}}{R_L} = \frac{32}{4000} = 0.008 \ {\rm A \ or \ 8 \ mA} \\ \end{array}$

The Zener current will be maximum when input voltage is maximum *i.e.*, 128 V Corresponding current through series resistance,

$$I = \frac{V_{in(max)} - V_{out}}{R_S} = \frac{128 - 32}{8000} = 0.012 \text{ A or } 12 \text{ mA}$$

Corresponding Zener current, $(I_Z)_{max.} = I - I_L = 12 - 8 = 4 \text{ mA.}$ (Ans.)

The Zener current will be minimum when input voltage is minimum i.e., 100 V. Corresponding, current through series resistance,

$$I' = \frac{V_{in(min)} - V_{out}}{R_S} = \frac{100 - 32}{8000} = 0.0085 = 8.5 \text{ mA}$$

Corresponding Zener current, $(I_Z)_{min.} = I' - I_L = 8.5 - 8 = 0.5 \text{ mA.}$ (Ans.)

Example 6. In the simple Zener-diode based voltage regulator shown in Fig. 25, a 5.6 V, 0.25 W Zener diode is used. For reliable operation, the minimum I_Z should be 1 mA. The load R_L varies between 20 Ω and 50 Ω . Find the range of R_S for reliable and safe operation of the voltage regulator.



 \therefore R ranges from 16 Ω to 39 Ω . (Ans.)

$$\frac{1}{2\pi} \int_{1}^{1} \int_{1}$$

$$= \sqrt{m} \sqrt{\frac{1}{2\pi} \left(\frac{hk}{2} - \frac{fin_2 uk}{4}\right)^{th}} \qquad 4-20$$

$$= \sqrt{m} \sqrt{\frac{1}{2\pi} \left(\frac{\pi}{2} - 0\right)} = \sqrt{m} \sqrt{\frac{1}{4}} - \frac{\sqrt{m}}{2}$$

$$\int \frac{1}{\sqrt{m_s}} - \frac{\sqrt{m}}{2}$$

$$\int \frac{1}{\sqrt{m_s}} \frac{1}{\sqrt{m_s}} = \frac{1}{2}$$
(3) Ripple factor: -(1)
Jhe stabio q rms value q ac components to dc components
to de comparative in the $0/p$ is known as supple Factor
 $\sqrt{m_s} = \sqrt{\frac{Vac}{2} + \frac{Vac}{2}}$

$$\frac{V_{m_s}^2 - \sqrt{\frac{1}{2}c}}{\sqrt{4c}} = \sqrt{\frac{V_{m_s}^2 - \sqrt{\frac{1}{2}c}}{\sqrt{4c}}}$$

$$\int \frac{V_{m_s}^2 - \sqrt{\frac{1}{2}c}}{\sqrt{4c}} = \sqrt{\frac{V_{m_s}^2 - \sqrt{\frac{1}{2}c}}{\sqrt{\frac{1}{2}c}}}$$

$$\int \frac{V_{m_s}}{\sqrt{\frac{1}{2}c}} - \frac{1}{\sqrt{\frac{1}{2}c}} = \sqrt{\frac{1}{\sqrt{\frac{1}{2}}}} = \sqrt{\frac{\pi}{\frac{1}{2}}}$$
Substitute $V_{m_s} = \frac{V}{\sqrt{\frac{1}{2}}} = \sqrt{\frac{\pi}{\frac{1}{2}}} = \sqrt{\frac{\pi}{\frac{1}{2}}} = \frac{\pi}{\sqrt{\frac{1}{2}}} = \frac{\pi}{\sqrt$

from the expression; it is clear tout the alg-ware present ofp is 121%. of Le Voltage. So half-ware present ofp is 121%. of Le Voltage. So half-ware acto succifier is not practically used in conversing acto de

(4) <u>Eddiciency(n)</u>: The matio of de ofp to ac ifp power is known as the meetigier efficiency. 4-21 n= Pdc. Per= Idi. RL = (m). RL Pac = Imis (y+RL) = (Im) ~ (y+RL) $\mathcal{T} = \frac{\left(\frac{T_{m}}{T}\right)^{*} \mathcal{R}_{L}}{\left(\frac{T_{m}}{T}\right)^{*} \left(\frac{\mathcal{Y}}{\mathcal{R}_{L}}\right)^{*}} = \frac{0.406 \mathcal{R}_{L}}{1 + \left(\frac{\mathcal{Y}}{\mathcal{R}_{L}}\right)^{*}}$ The efficiency will be more. if I is neglisible as Companed to RL Mon. rectifier ezpicency = 40.6%. (5) <u>Peak Inverse voltage (PIV):-</u> It is defined as max. nevers a voltage trate a diode Can withstand Lothout des broging the junction. The peak inverse voltage alos a diode is the peak of -ve half cycle. :. PIV= Vm (6) From Factor :- $F_{i}F = \frac{\gamma_{ms} \, value}{av_{g} \, value} = \frac{\nu_{m}}{\frac{2}{2}} = \frac{T}{2} = 1.57$ (7) Peak Factor:-P.F= <u>Peak Value</u> = <u>Vm</u> = 2 <u>Rms value</u> = <u>vm</u> = 2

problem

4-22 (12) A crystal divide having internal presistance by = 20-2 is used for have signed precification. If the applied voltage is U= 50 Sincet + load substance RL = 800 -2 gind (i) Im, Jac, Irms (ii) Circ. power Input and dec. pover endput (iii) d.c. oneque vollage and (ir) ezpiciency of neclification. (i) $I_m = \frac{V_m}{\eta_{+R_1}} = \frac{50}{20+800} = 0.061 \text{ A}$ Sul: Given data ng = 20-2 V= 50 SinNE $I_{dc} = \frac{J_m}{T} = \frac{61}{T} = \frac{19.4mA}{1000}$ $J_{ms} = \frac{J_m}{2} = \frac{61}{2} = \frac{30.5mA}{1000}$ 1. Vm = 50 R = 800-2 (1) Pac = I'ms (THRL) = (30,5 × 16-3)2 × (20+800)=0.7634) Pdc = Idc XR = (19.4×10-3) × 800 = 0,301W (ili) d. c. onlyput voltage = Ide X Rz = 19.6mA × 800-2 = 15.52V (iv) Ezziciency = 0.301 ×100 = 39.5%



Operation(1): During the positive half-lycle of secondary voltage, the End A of the Secondary Winding became positive & end B negative. This makes the diode D, Jonward brased + diode b2 revense brased. Therefore diode D, Conductor Litile diode b2 revense brased. Therefore diode D, Conductor Litile diode b2 does not. The Conventional current glow is through diode D, load guildistor R.
(2) 'RMS Value:

$$V_{Inrs} = \int \frac{1}{\pi} \int_{0}^{\pi} V_{In}^{V} Sin^{T} Mt d(Mt)$$

$$= V_{Inn} \int \frac{1}{\pi} \left[\frac{1 - (KS2Mt)}{2} d(Mt) \right]$$

$$= V_{Inn} \int \frac{1}{\pi} \left[\frac{Mt}{2} - \frac{Sin2Mt}{4} \right]_{0}^{T}$$

$$= V_{Inn} \int \frac{1}{\pi} \left[\frac{\pi}{2} - 0 \right] = V_{Inn} \int \frac{1}{2} = \frac{V_{Im}}{\sqrt{2}}$$

$$(3) : \frac{R'_{IDDLe} Fincton! :- (I'')}{V_{Rec}} \int_{-1}^{\infty} = \int \left[\frac{V_{Im}}{\sqrt{2}} \right]_{-1}^{T} = \int \frac{V_{Im}}{\sqrt{2}}$$

$$(3) : \frac{R'_{IDDLe} Fincton! :- (I'')}{V_{Rec}} - 1 = \int \left[\frac{V_{Im}}{\sqrt{2}} \right]_{-1}^{T} - 1 = \int \frac{\pi}{8} - 1$$

$$= 0.48L$$

$$(4) Killing':$$

$$T = \int Ris$$

(4) Klfdiency

$$\begin{aligned}
\eta = \frac{P_{dL}}{P_{nc}} \\
P_{dC} = \frac{1}{2L_{c}} \chi R_{L} = \left(\frac{2\pi_{m}}{\pi}\right)^{n}, R_{L} \quad \text{Where} \quad \overline{T_{m}} = \frac{V_{m}}{\frac{2}{3}tR_{L}} \\
P_{dC} = \frac{1}{2m_{s}} \chi \left(r_{f} + R_{L}\right) = \left(\frac{1}{m_{s}}\right)^{2} \left(\frac{\eta}{2}tR_{L}\right) \\
\vdots \quad \eta = \left(\frac{2\pi_{m}}{\pi}\right)^{n}, R_{L} \quad \frac{0.812 \ R_{L}}{\frac{1}{2}tR_{L}} = \frac{0.812 \ R_{L}}{1 + \left(\frac{2}{R_{L}}\right)} \\
\vdots \quad \eta = \left(\frac{2\pi_{m}}{\pi}\right)^{n} (\eta + R_{L}) = \frac{0.812 \ R_{L}}{2tR_{L}} = \frac{0.812 \ R_{L}}{1 + \left(\frac{2}{R_{L}}\right)} \\
\vdots \quad \eta = \frac{2\pi_{m}}{(\pi_{m})} (\eta + R_{L}) = \frac{0.812 \ R_{L}}{2tR_{L}} = \frac{0.812 \ R_{L}}{1 + \left(\frac{2}{R_{L}}\right)} \\
\vdots \quad \eta = \frac{2\pi_{m}}{(\pi_{m})} (\eta + R_{L}) = \frac{0.812 \ R_{L}}{2tR_{L}} = \frac{0.812 \ R_{L}}{1 + \left(\frac{2}{R_{L}}\right)} \\
\vdots \quad \eta = \frac{2\pi_{m}}{2tR_{L}} = \frac{0.812 \ R_{L}}{2tR_{L}} = \frac{0.812 \ R_{L}}{1 + \left(\frac{2}{R_{L}}\right)} \\
\vdots \quad \eta = \frac{2\pi_{m}}{2tR_{L}} = \frac{1}{2R_{L}} = \frac{1}{2R_{L}} = \frac{1}{2R_{L}} = \frac{1}{2R_{L}} = \frac{1}{2R_{L}} \\
\vdots \quad \eta = \frac{1}{2R_{L}} = \frac$$

(5) Peak inverse voltage (PIV):-PIV = 2KmConstant in a second of the (6) Form Factor :-F.F = RHS value = 1.11 Avg. value (7) Peak factor:- $\overrightarrow{P:F} = \frac{Peak value}{R^{MS} value} = \frac{V_{13}}{V_{2}} = \sqrt{2}$ = 1.41prosens 4-26 (12) A Bull-ware succession uses two diodes, the internal sussistered of each is assumed constant at 20 2. The transformer mus secondary voltage from centre-lap to each end of secondary is 50V + load guissbance is 950-2 Find (1) the mean load count (i) the rms value of load current. Sul Given dula: Vm = 50 XV2 = 70.7V $I_{in} = \frac{v_{in}}{v_{4+R_i}} = \frac{70.7}{20+980} = 70.7m_A$ U Ide = Jarg = 2In = 2X 70.7 = 45mA (ii) $I_{ms} = \frac{I_m}{\sqrt{2}} = \frac{70.7}{\sqrt{2}} = 50 \text{ mA}$ 1-1



20 The zour diodes used in a bridge rectifier circuit have gorvered resistances which may be considered constant at 1-and an minite resistance. The alternating Supply voltage is 2400 rims & rusistive load is 48-2. Calculate (i) mean loud tomente (ii) rectifier ezpicency -(III) power dissipated in each diode. Sel: (1) Max, load correct, Im = 1/m = 1/2×240 24+R = 2×1+48= 6.79 ". Mean load current, $\overline{Tac} = \frac{27m}{T} = \frac{2\times 6.79}{T} = 4.32$ (ii) RMS value of load correct $I_{ms} = \frac{I_m}{V_2} = \frac{6.79}{V_2} = 4.8 A.$

5. Filter Circuits

5.1 Introduction

A power supply must provide ripple free source of power from an A.C. line. But the output of a rectifier circuit contains ripple components in addition to a D.C. term. It is necessary to include a filter between the rectifier and the loads in order to eliminate these ripple components. Ripple components are high frequency A.C. Signals in the D.C output of the rectifier. These are not desirable, so they must be filtered. So filter circuits are used.

Many types of passive filters are in use such as.

- Shunt capacitor filter
- Series inductor filter
- Chock input (LC) filter
- Pi(π) section filter or CLC filter or capacitor input filter.

5.2 Shunt capacitor filter

This type of filter consists of large value of capacitor connected across the load resistor R_1 as shown in figure 5.1. This capacitor offers a low reactance to the a.c. components and very high impedance to d.c. so that the a.c. components in the rectifier output find low reactance path through capacitor and only a small part flows through R_L , producing small ripple at the output as shown in figure.

Here Xc (=1/2 π fC, the impedance of capacitor) should be smaller than R_L. Because, current should pass through C and C should get charged. If C value is very small, Xc will be large and hence current flows through R_L only and no filtering action takes place.

The capacitor C gets charged when the diode (in the rectifier) is conducting and gets discharged (when the diode is not conducting) through RL. When the input voltage $v = Vm \sin \omega t$ is greater than the capacitor voltage, C gets charged. When the input voltage is less than that of the capacitor voltage, C will discharge through R_L. The stored energy in the capacitor maintains the load voltage at a high value for a long period. The diode conducts only for a short interval of high current. The waveforms are as shown in figure 5.2. Capacitor opposes sudden fluctuations in voltage across it. So the ripple voltage is minimized.



Fig 5.1 CT FWR with shunt Capacitor filter





The discharging of the capacitor depends upon the time constant $C.R_L$. Hence the smoothness and the magnitude of output voltage depend upon the value of capacitor C and R_L . As the value of C increases the smoothness of the output also increases. But the maximum value of the capacitor is limited by the current rating of the diode. Also decrease in the value of R_L increases the load current and makes the time constant smaller. These types of filters are used in circuits with small load current like transistor radio receivers, calculators, etc. The ripple factor in capacitor filter is given b $\gamma = 1/4\sqrt{3}fCR_L\gamma$.

Advantages

Disadvantages

Capacitor draws more current

- Low cost
- Small size and weight
- Good characteristics
- Can be connected for both HW and FW rectifiers
- Improved d.c. output

5.3 Series inductor filter

The working of series inductor filter depends on the inherent property of the inductor to oppose any variation in current intend to take place. Fig 5.4 shows a series inductor filter connected at the output of a FWR. Here the reactance of the inductor is more for ac components and it offers more opposition to them. At the same time it provides no impedance for d.c. component. Therefore the inductor blocks a.c. components in the output of the rectifier and allows only d.c. component to flow through $R_{\rm L}$.



The action of an inductor depends upon the current through it and it requires current to flow at all time. Therefore filter circuits consisting inductors can only be used together with full wave rectifiers.

In inductor filter an increase in load current will improve the filtering action and results in reduced ripple. Series inductor filters are used in equipments of high load currents. The ripple factor in series inductor filter $\gamma = R_L/3\sqrt{2}\omega L$

Advantages

- Sudden changes in current is smoothen out
- Improved filtering action at high load currents

Disadvantages

- Reduced output voltage due to the drop across the inductor.
- Bulky and large in size
- Note suite for HWR

5.4 LC filter

It is a combination of inductor and capacitor filter. Here an inductor is connected in series and a capacitor is connected in parallel to the load as shown in fig 5.6. As discussed earlier, a series inductor filter will reduce the ripple, when increasing the load current. But in case of a capacitor filter it is reverse that when increasing current the ripple also increases. So a combination of these two filters would make ripple independent of load current. The ripple factor of a chock input filter is given by



Fig 5.6 Rectifier with LC filter

Fig 5.7 output waveform of Rectifier with LC filter

Since the d.c. resistance of the inductor is very low it allows d.c. current to flow easily through it. The capacitor appears open for d.c. and so all d.c. component passes through it. The capacitor appears open for d.c. and so all d.c components passes through the load resistor R_1 .

5.4.1 Bleeder resistor

For optimum functioning, the inductor requires a minimum current to flow through, at all time. When the current falls below this rat, the output will increase sharply and hence the regulation become poor. To keep up the circuit current above this minimum value, a resistor is permanently connected across the filtering capacitor and is called **bleeder resistor**. This resistor always draws a minimum current even if the external load is removed. It also provides a path for the capacitor to discharge when power supply is turned off.

Advantages

- Reduced ripples at the output
- Action is independent of load current

Disadvantages

- Low output voltage
- Bulky and large in size
- Not suit to connect with HWR.

5.5 π – filter (Capacitor input filter) or CLC filter

This filter is basically a capacitor filter followed by an LC filter as shown in fig 5.8. Since its shape (C-L-C) is like the letter π it is called π – filter. It is also called capacitor input filter because the rectifier feeds directly into the capacitor C_1 . Here the first capacitor C_1 offers a low reactance to a.c. component of rectifier output but provide more reactance to d.c components. Therefore most of the a.c. components will bypass through C_1 and the d.c. component flows through chock L. The chock offers very high reactance to the a.c. component. Thus it blocks a.c. components while pass the d.c. The capacitor C_2 bypasses any other a.c. component appears across the load and we get study d.c. output as shown below. The ripple factor in a π -section filter is given by $\gamma = \sqrt{2} X_{c1} X_{c2} / X_L R_L$



• Suitable to be used with both HWR and FWR

UNIT V

BIPOLAR JUNCTION TRANSISTOR AND JFET

5.1 INTRODUCTION

> The transistor was invented in 1947 by John Bardeen, Walter Brattain and William Shockley at Bell Laboratory in America. A transistor is a semiconductor device, commonly used as an Amplifier or an electrically Controlled Switch.

- > There are two types of transistors:
 - 1) Unipolar Junction Transistor
 - 2) Bipolar Junction Transistor
- In Unipolar transistor, the current conduction is only due to one type of carriers i.e., majority charge carriers. The current conduction in bipolar transistor is because of both the types of charge carriers i.e., holes and electrons. Hence it is called as Bipolar Junction Transistor and it is referred to as BJT.
- BJT is a semiconductor device in which one type of semiconductor material is sand witched between two opposite types of semiconductor i.e., an n-type semiconductor is sandwiched between two p-type semiconductors or a p-type semiconductor is sandwiched between two n-type semiconductor.
- ➤ Hence the BJTs are of two types. They are:
 - 1) n-p-n Transistor
 - 2) p-n-p Transistor

The two types of BJTs are shown in the figure below.



- The arrow head represents the conventional current direction from p to n. Transistor has three terminals.
 - 1) Emitter 2) Base 3) Collector

- Transistor has two p-n junctions. They are:
 - 1) Emitter-Base Junction
 - 2) Collector-Base Junction

Emitter: Emitter is heavily doped because it is to emit the charge carriers.

Base: The charge carriers emitted by the emitter should reach collector passing through the base. Hence base should be very thin and to avoid recombination, and to provide more collector current base is lightly doped.

Collector: Collector has to collect the most of charge carriers emitted by the emitter. Hence the area of cross section of collector is more compared to emitter and it is moderately doped.

Transistor can be operated in three regions.

1) Active region.

2) Saturation region.

3) Cut-Off region.

Active Region: For the transistor to operate in active region base to emitter junction is forward biased and collector to base junction is reverse biased.

Saturation Region: Transistor to be operated in saturation region if both the junctions i.e., collector to base junction and base to emitter junction are forward biased.

Cut-Off Region: For the transistor to operate in cut-off region both the junctions i.e., base to emitter junction and collector to base junction are reverse biased.

Transistor can be used as

1) Amplifier 2) Switch

For the transistor to act as an amplifier, it should be operated in active region. For the transistor to act as a switch, it should be operated in saturation region for ON state, and cut-off region for OFF state.

5.2 TRANSISTOR OPERATION:

Working of a N-P-N Transistor:



The n-p-n transistor with base to emitter junction forward biased and collector base junction reverse biased is as shown in figure.

As the base to emitter junction is forward biased the majority carriers emitted by the n type emitter i.e., electrons have a tendency to flow towards the base which constitutes the emitter Current I_E . As the base is p-type there is chance of recombination of electrons emitted by the emitter with the holes in the p-type base. But as the base is very thin and lightly doped only few electrons emitted by the n-type emitter less than 5% combines with the holes in the p-type base, the remaining more than 95% electrons emitted by the n-type emitter cross over into the collector region constitute the collector current.

The current distributions are as shown in fig $I_E = I_B + I_C$

Working of a P-N-P Transistor:



The p-n-p transistor with base to emitter junction is forward biased and collector to base junction reverse biased is as show in figure. As the base to emitter junction is forward biased the majority carriers emitted by the type emitter i.e., holes have a tendency to flow towards the base which constitutes the emitter current IE. As the base is n-type there is a chance of recombination of holes emitted by the emitter with the electrons in the n-type base. But as the base us very thin and lightly doped only few electrons less than 5% combine with the holes emitted by the p-type emitter, theremaining 95% charge carriers cross over into the collector region to constitute the collector current. The current distributions are shown in figure.

$$\mathbf{I}_{\mathbf{E}} = \mathbf{I}_{\mathbf{B}} + \mathbf{I}_{\mathbf{C}}$$

5.1 TRANSISTOR CIRCUIT CONFIGURATIONS:

Following are the three types of transistor circuit configurations:

- 1) Common-Base (CB)
- 2) Common-Emitter (CE)
- 3) Common-Collector (CC)

Here the term 'Common' is used to denote the transistor lead which is common to the input and output circuits. The common terminal is generally grounded. It should be remembered that regardless the circuit configuration, the emitter is always forward-biased while the collector is always reverse-biased.



Fig. Common – Collector Configuration

5.1.1 Common – Base (CB) Configurations:

In this configuration, the input signal is applied between emitter and base while the output is taken from collector and base. As base is common to input and output circuits, hence the name common-base configuration. Figure show the common-base P-N-P transistor circuit.



Fig. Common - Base PNP transistor amplifier.

Current Amplification Factor (α) :

When no signal is applied, then the ratio of the collector current to the emitter current is called dc alpha (α_{dc}) of a transistor.

$$\alpha_{dc} = \frac{\Delta I_C}{\Delta I_E}$$

(Negative sign signifies that I_E flows into transistor while I_C flows out of it). ' α ' of a transistor is a measure of the quality of a transistor. Higher is the value of ' α ', better is the transistor in the sense that collector current approaches the emitter current. By considering only magnitudes of the currents, $I_C = \alpha I_E$ and hence $I_B = I_E - I_C$ Therefore,

$$\mathbf{I}_{\mathrm{B}} = \mathbf{I}_{\mathrm{E}} - \boldsymbol{\alpha} \ \mathbf{I}_{\mathrm{E}} = \mathbf{I}_{\mathrm{E}}(1 - \boldsymbol{\alpha})$$

For all practical purposes, $\alpha_{dc} = \alpha_{ac} = \alpha$ and practical values in commercial transistors range from 0.9 to 0.99.

Total Collector Current:

The total collector current consists of the following two parts i) I_E current due to majority carriers ii) I_{CBO} current due to minority carriers

Total collector current $I_C = \alpha I_E + I_{CBO}$ The collector current can also be expressed as $I_C = \alpha (I_B + I_C) + I_{CBO} (Q I_E = I_B + I_C)$

$$\Rightarrow I_C(1-\alpha) = \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C = \left(\frac{\alpha}{1-\alpha}\right) I_B + \left(\frac{1}{1-\alpha}\right) I_{CBO}$$

5.1.2 COMMON-EMITTER (CE) CONFIGURATION:

In this configuration, the input signal is applied between base and emitter and the output is taken from collector and emitter. As emitter is common to input and output circuits, hence the name common emitter configuration.

Figure shows the Common-Emitter P-N-P transistor circuit.



Fig. Common-Emitter PNP transistor amplifier.

Current Amplification Factor (β):

When no signal is applied, then the ratio of collector current to the base current is called dc beta (β_{dc}) of a transistor.

When signal is applied, the ratio of change in collector current to the change in base current is defined as base current amplification factor. Thus,

From equation (1), $I_C = \beta I_B$

Almost in all transistors, the base current is less than 5% of the emitter current. Due to this fact, ' β ' ranges from 20 to 500. Hence this configuration is frequently used when appreciable current gain as well as voltage gain is required.

Total Collector Current:

The Total collector current $I_C = \beta I_B + I_{CEO}$ (3) Where I_{CEO} is the leakage current.

But, we have,
$$I_C = \left(\frac{\alpha}{1-\alpha}\right)I_B + \left(\frac{1}{1-\alpha}\right)I_{CBO}$$
(4)

Comparing equations (3) and (4), we get

Relation between α and β :

5.1.3 COMMON – COLLECTOR (CC) CONFIGURATION:

In this configuration, the input signal is applied between base and collector and the output is taken from the emitter. As collector is common to input and output circuits, hence the name common collector configuration. Figure shows the common collector PNP transistor circuit.



Fig. Common Collector PNP transistor amplifier.

Current Amplification Factor (γ):

When no signal is applied, then the ratio of emitter current to the base current is called as dc gamma (γ_{dc}) of the transistor.

$$\gamma_{dc} = \gamma = \frac{I_E}{I_B} \tag{1}$$

5.4 CHARACTERISTICS OF COMMON-BASE CIRCUIT:



Fig. Circuit to determine CB static characteristics.

Input Characteristics:

To determine the input characteristics, the collector-base voltage V_{CB} is kept constant at zero volts and the emitter current I_E is increased from zero in suitable equal steps by increasing V_{EB} . This is repeated for higher fixed values of V_{CB} . A curve is drawn between emitter current IE and emitter- base voltage V_{EB} at constant collector-base voltage V_{CB} . The input characteristics thus obtained are shown in figure below.



Fig. CB Input Characteristics.

Output Characteristics:

To determine the output characteristics, the emitter current I_E is kept constant at a suitable value by adjusting the emitter-base voltage V_{EB} . Then V_{CB} is increased in suitable equal steps and the collector current I_C is noted for each value of I_E . Now the curves of I_C versus V_{CB} are plotted for constant values of I_E and the output characteristics thus obtained is shown in figure below.



Fig. CB Output Characteristics

From the characteristics, it is seen that for a constant value of I_E , I_C is independent of V_{CB} and the curves are parallel to the axis of V_{CB} . Further, I_C flows even when V_{CB} is equal to zero. As the emitter-base junction is forward biased, the majority carriers, i.e., electrons, from the emitter are injected into the base region. Due to the action of the internal potential barrier at the reverse biased collector-base junction, they flow to the collector region and give rise to I_C even when V_{CB} is equal to zero.

It is the slope of CB output characteristics I_C versus V_{CB}.

5.5CHARACTERISTICS OF COMMON-EMITTER CIRCUIT:

The circuit diagram for determining the static characteristic curves of the an N-P-N transistor in the common emitter configuration is shown in figure below.



Fig. Circuit to determine CE Static characteristics.

Input Characteristics:

To determine the input characteristics, the collector to emitter voltage is kept constant at zero volts and base current is increased from zero in equal steps by increasing V_{BE} in the circuit. The value of V_{BE} is noted for each setting of I_B . This procedure is repeated for higher fixed values of V_{CE} , and the curves of I_B versus V_{BE} are drawn.

The input characteristics thus obtained are shown in figure below.



Fig. CE Input Characteristics.

When $V_{CE}=0$, the emitter-base junction is forward biased and he junction behaves as a forward biased diode. When V_{CE} is increased, the width of the depletion region at the reverse biased collector-

base junction will increase. Hence he effective width of the base will decrease. This effect causes a decrease in the base current I_B . Hence, to get the same value of I_B as that for $V_{CE}=0$, V_{BE} should be increased. Therefore, the curve shifts to the right as V_{CE} increases.

Output Characteristics:

To determine the output characteristics, the base current I_B is kept constant at a suitable value by adjusting base-emitter voltage, V_{BE} . The magnitude of collector-emitter voltage V_{CE} is increased in suitable equal steps from zero and the collector current IC is noted for each setting of V_{CE} . Now the curves of I_C versus V_{CE} are plotted for different constant values of I_B . The output characteristics thus obtained are shown in figure below.



Fig. CE Output characteristics

The output characteristics of common emitter configuration consist of three regions: Active, Saturation and Cut-off regions.

Active Region:

The region where the curves are approximately horizontal is the "Active" region of the CE configuration. In the active region, the collector junction is reverse biased. As V_{CE} is increased, reverse bias increase. This causes depletion region to spread more in base than in collector, reducing the changes of recombination in the base. This increase the value of a dc . This Early effect causes collector current to rise more sharply with increasing V_{CE} in the active region of output characteristics of CE transistor.

Saturation Region:

If V_{CE} is reduced to a small value such as 0.2V, then collector-base junction becomes forward biased, since the emitter-base junction is already forward biased by 0.7V. The input junction in CE configuration is base to emitter junction, which is always forward biased to operate transistor in active region. Thus input characteristics of CE configuration are similar to forward characteristics of p-n junction diode. When both the junctions are forwards

biased, the transistor operates in the saturation region, which is indicated on the output characteristics. The saturation value of V_{CE} , designated $V_{CE}(Sat)$, usually ranges between 0.1V to 0.3V.

Cut-Off Region:

When the input base current is made equal to zero, the collector current is the reverse leakage current ICEO. Accordingly, in order to cut off the transistor, it is not enough to reduce IB=0. Instead, it is necessary to reverse bias the emitter junction slightly. We shall define cut off as the condition where the collector current is equal to the reverse saturation current ICO and the emitter current is zero.

5.5 Characteristics of common collector circuit:

The circuit diagram for determining the static characteristics of an N-P-N transistor in the common collector configuration is shown in fig. below.



Fig. Circuit to determine CC static characteristics.

Input Characteristics:

To determine the input characteristic, V_{EC} is kept at a suitable fixed value. The base collector voltage V_{BC} is increased in equal steps and the corresponding increase in I_B is noted. This is repeated for different fixed values of V_{EC} . Plots of V_{BC} versus I_B for different values of V_{EC} shown in figure are the input characteristics.



Fig. CC Input Characteristics.

Output Characteristics:

The output characteristics shown in figure below are the same as those of the common emitter configuration.



Fig. CC output characteristics.

Transistor as an Amplifier :

The transistor raises the strength of a weak signal and hence acts an amplifier. The transistor amplifier circuit is shown in the figure below. The transistor has three terminals namely emitter, base and collector. The emitter and base of the transistor are connected in forward biased and the collector base region is in reverse bias. The forward bias means the P-region of the transistor is connected to the positive terminal of the supply and the negative region is connected to the N-terminal and in reverse bias just opposite of it has occurred.



The input signal or weak signal is applied across the emitter base and the output is obtained to the load resistor R_C which is connected in the collector circuit. The DC voltage V_{EE} is applied to the input circuit along with the input signal to achieve the amplification. The DC voltage V_{EE} keeps the emitter-base junction under the forward biased condition regardless of the polarity of the input signal and is known as a bias voltage.

In the collector circuit, a load resistor R_C of high value is connected. When collector current flows through such a high resistance, it produces a large voltage drop across it. Thus, a weak signal (0.1V) applied to the input circuit appears in the amplified form (10V) in the collector circuit.

FIELD EFFECT TRANSISTOR

INTRODUCTION

- 1. The Field effect transistor is abbreviated as FET, it is an another semiconductor device like a BJT which can be used as an amplifier or switch.
- 2. The Field effect transistor is a voltage operated device. Whereas Bipolar junction transistor is a current controlled device. Unlike BJT a FET requires virtually no input current.
- 3. This gives it an extremely high input resistance , which is its most important advantage over a bipolar transistor.
- 4. FET is also a three terminal device, labeled as source, drain and gate.
- 5. The source can be viewed as BJT's emitter, the drain as collector, and the gate as the counter part of the base.
- 6. The material that connects the source to drain is referred to as the channel.
- 7. FET operation depends only on the flow of majority carriers ,therefore they are called uni polar devices. BJT operation depends on both minority and majority carriers.
- 8. As FET has conduction through only majority carriers it is less noisy than BJT.
- 9. FETs are much easier to fabricate and are particularly suitable for ICs because they occupy less space than BJTs.
- 10. FET amplifiers have low gain bandwidth product due to the junction capacitive effects and produce more signal distortion except for small signal operation.
- 11. The performance of FET is relatively unaffected by ambient temperature changes. As it has a negative temperature coefficient at high current levels, it prevents the FET from thermal breakdown. The BJT has a positive temperature coefficient at high current levels which leads to thermal breakdown.

CLASSIFICATION OF FET:

There are two major categories of field effect transistors:

- 1. Junction Field Effect Transistors
- 2. MOSFETs

1. Junction Field Effect Transistors

- Junction Field Effect Transistors are further sub divided in to P- channel and Nchannel devices.
- When the channel is of N-type the JFET is referred to as an N-channel JFET, when the channel is of P-type the JFET is referred to as P-channel JFET.

CONSTRUCTION OF N-CHANNEL JFET

A piece of N- type material, referred to as channel has two smaller pieces of P-type materialattached to its sides, forming PN junctions. The channel ends are designated as the drain and source . And the two pieces of P-type material are connected together and their terminal is called the gate. Since this channel is in the N-type bar, the FET is known as N-channel JFET.



The schematic symbols for the P-channel and N-channel JFETs are shown in the figure

OPERATION OF N-CHANNEL JFET:-

The overall operation of the JFET is based on varying the width of the channel to control the drain current.

A piece of N type material referred to as the channel, has two smaller pieces of P type material attached to its sites, farming PN –Junctions. The channel's ends are designated the drain and the source. And the two pieces of P type material are connected together and their terminal is called the gate. With the gate terminal not connected and the potential applied positive at the drain negative at the source a drain current I_D flows.

When the gate is biased negative with respective to the source the PN junctions are reverse biased and depletion regions are formed. The channel is more lightly doped than the P type gate blocks, so the depletion regions penetrate deeply into the channel. Since depletion region is a region depleted of charge carriers it behaves as an Insulator. The result is that the channel is narrowed. Its resistance is increased and I_D is reduced. When the negative gate bias voltage is further increased, the depletion regions meet at the center and Id is cut off completely.

There are two ways to control the channel width

- 1. By varying the value of V_{GS}
- 2. And by Varying the value of $V_{DS}\,$ holding $V_{GS}\, constant$

1 By varying the value of V_{GS} :-

We can vary the width of the channel and in turn vary the amount of drain current. This can be done by varying the value of V_{GS} . This point is illustrated in the fig below. Here we are dealing with N channel FET. So channel is of N type and gate is of P type that constitutes a PN junction. This PN junction is always reverse biased in JFET operation .The reverse bias is applied by a battery voltage V_{GS} connected between the gate and the source terminal i.e positive terminal of the battery is connected to the source and negative terminal to gate.



- 1) When a PN junction is reverse biased the electrons and holes diffuse across junction by leaving immobile ions on the N and P sides , the region containing these immobile ions is known as depletion regions.
- 2) If both P and N regions are heavily doped then the depletion region extends symmetrically on both sides.
- 3) But in N channel FET P region is heavily doped than N type thus depletion region extends more in N region than P region.
- 4) So when no V_{DS} is applied the depletion region is symmetrical and the conductivity becomes Zero. Since there are no mobile carriers in the junction.
- 5) As the reverse bias voltage is increases the thickness of the depletion region also increases. i.e. the effective channel width decreases .
- 6) By varying the value of V_{GS} we can vary the width of the channel.

2 Varying the value of $V_{DS}\,$ holding V_{GS} constant :-

- 1) When no voltage is applied to the gate i.e. $V_{GS} = 0$, V_{DS} is applied between source and drain the electrons will flow from source to drain through the channel constituting drain current I_D .
- 2) With $V_{GS} = 0$ for $I_D = 0$ the channel between the gate junctions is entirely open .In response to a small applied voltage V_{DS} , the entire bar acts as a simple semi conductor resistor and the current I_D increases linearly with V_{DS} .
- 3) The channel resistances are represented as R_D and R_S as shown in the fig.



- 4) This increasing drain current I_D produces a voltage drop across rd which reverse biases the gate to source junction, $(R_D > R_S)$. Thus the depletion region is formed which is not symmetrical.
- 5) The depletion region i.e. developed penetrates deeper in to the channel near drain and less towards source because V $R_D >> V R_S$. So reverse bias is higher near drain than at source.
- 6) As a result growing depletion region reduces the effective width of the channel. Eventually a voltage V_{DS} is reached at which the channel is pinched off. This is the voltage where the current Id begins to level off and approach a constant value.
- 7) So, by varying the value of V_{DS} we can vary the width of the channel holding V_{GS} constant.

When both V_{GS} and V_{DS} is applied:-



It is of course in principle not possible for the channel to close Completely and there by reduce the current Id to Zero for, if such indeed, could be the case the gate voltage V_{GS} is applied in the direction to provide additional reverse bias

- 1) When voltage is applied between the drain and source with a battery V_{DD} , the electrons flow from source to drain through the narrow channel existing between the depletion regions. This constitutes the drain current I_D , its conventional direction is from drain to source.
- 2) The value of drain current is maximum when no external voltage is applied between gate and source and is designated by I_{DSS} .



- 3) When V_{GS} is increased beyond Zero the depletion regions are widened. This reduces the effective width of the channel and therefore controls the flow of drain current through the channel.
- 4) When V_{GS} is further increased a stage is reached at which to depletion regions touch each other that means the entire channel is closed with depletion region. This reduces the drain current to Zero.

CHARACTERISTICS OF N-CHANNEL JFET :-

The family of curves that shows the relation between current and voltage are known as characteristic curves.

There are two important characteristics of a JFET.

- 1) Drain or VI Characteristics
- 2) Transfer characteristics

1. Drain Characteristics:

 $\label{eq:VDS} Drain \ characteristics \ shows \ the \ relation \ between \ the \ drain \ to \ source \ voltage \ V_{DS} \ and \ drain \ current \ Id. \ In \ order \ to \ explain \ typical \ drain \ characteristics \ let \ us \ consider \ the \ curve \ with \ V_{GS} = 0 \ V.$

- 1) When V_{DS} is applied and it is increasing the drain current I_D also increases linearly up to knee point.
- 2) This shows that FET behaves like an ordinary resistor. This region is called as ohmic region.
- 3) I_D increases with increase in drain to source voltage. Here the drain current is increased slowly as compared to ohmic region.



4) It is because of the fact that there is an increase in $V_{\rm DS}$. This in turn increases the reverse bias voltage across the gate source junction .As a result of this depletion region grows in size thereby reducing the effective width of the channel.

5) All the drain to source voltage corresponding to point the channel width is reduced to a minimum value and is known as pinch off.

6) The drain to source voltage at which channel pinch off occurs is called pinch off voltage(V_P).

PINCH OFF Region:

- 1) This is the region shown by the curve as saturation region.
- 2) It is also called as saturation region or constant current region. Because of the channel is occupied with depletion region, the depletion region is more towards the drain and less towards the source, so the channel is limited, with this only limited number of carriers are only allowed to cross this channel from source drain causing a current that is constant in this region. To use FET as an amplifier it is operated in this saturation region.
- 3) In this drain current remains constant at its maximum value I_{DSS} .
- 4) The drain current in the pinch off region depends upon the gate to source voltage and is given by the relation

 $I_D = I_{DSS} [1 - V_{GS} / V_P]^2$

This is known as shokley's relation.

BREAKDOWN REGION:

- 1) The region is shown by the curve .In this region, the drain current increases rapidly as the drain to source voltage is increased.
- 2) It is because of the gate to source junction due to avalanche effect.
- 3) The avalanche break down occurs at progressively lower value of V_{DS} because the reverse bias gate voltage adds to the drain voltage thereby increasing effective voltage across the gate junction

This causes

- 1. The maximum saturation drain current is smaller
- 2. The ohmic region portion decreased.
- 4) It is important to note that the maximum voltage V_{DS} which can be applied to FET is the lowest voltage which causes available break down.

2. TRANSFER CHARACTERISTICS:

- 1) First adjust the drain to source voltage to some suitable value, then increase the gate to source voltage in small suitable value.
- 2) Plot the graph between gate to source voltage along the horizontal axis and current ID on the vertical axis. We shall obtain a curve like this.



- 3) As we know that if V_{GS} is more negative curves drain current to reduce . where V_{GS} is made sufficiently negative, I_D is reduced to zero. This is caused by the widening of the depletion region to a point where it is completely closes the channel. The value of V_{GS} at the cutoff point is designed as $V_{GS \text{ off}}$
- 4) The upper end of the curve as shown by the drain current value is equal to I_{DSS} that is when $V_{GS} = 0$ the drain current is maximum.
- 5) While the lower end is indicated by a voltage equal to $V_{GS \text{ off}}$
- 6) If V_{GS} continuously increasing , the channel width is reduced , then $I_D = 0$
- 7) It may be noted that curve is part of the parabola; it may be expressed as $I_D = I_{DSS} [1 V_{GS} / V_{GS \text{ off}}]^2$

DIFFERENCE BETWEEN V_P and $V_{GS\,off}$:

1) V_P is the value of V_{GS} that causes the JFET to become constant current component, It is measured at V_{GS} =0V and has a constant drain current of $I_D = I_{DSS}$. Where $V_{GS off}$ is the value of V_{GS} that reduces I_D to approximately zero.

Why the gate to source junction of a JFET be always reverse biased ?

The gate to source junction of a JFET is never allowed to become forward biased because the gate material is not designed to handle any significant amount of current. If the junction is allowed to become forward biased, current is generated through the gate material. This current may destroy the component.

There is one more important characteristic of JFET reverse biasing i.e. J FET 's have extremely high characteristic gate input impedance. This impedance is typically in the high mega ohm range. With the advantage of extremely high input impedance it draws no current from the source. The high input impedance of the JFET has led to its extensive use in integrated circuits. The low current requirements of the component makes it perfect for use in ICs. Where thousands of transistors must be etched on to a single piece of silicon. The low current draw helps the IC to remain relatively cool, thus allowing more components to be placed in a smaller physical area.

MOSFET:

➢ We now turn our attention to the Insulated Gate FET or Metal Oxide Semi Conductor FET which is having the greater commercial importance than the junction FET.

➢ Most MOSFETS however are triodes, with the substrate internally connected to the source. The circuit symbols used by several manufacturers are indicated in the Fig below.



(a) Depletion type MOSFET

(b) Enhancement type MOSFET

Both of them are P- channel

- ➢ Here are two basic types of MOSFETS
 - (1) Depletion type (2) Enhancement type MOSFET.
- > D-MOSFETS can be operated in both the depletion mode and the enhancement mode.
- E MOSFETS are restricted to operate in enhancement mode. The primary difference between them is their physical construction.
- > The construction difference between the two is shown in the fig given below.



As we can see the D MOSFET have physical channel between the source and drain terminals(Shaded area)



The E MOSFET on the other hand has no such channel physically. It depends on the gate voltage to form a channel between the source and the drain terminals.

Both MOSFETS have an insulating layer between the gate and the rest of the component. This insulating layer is made up of SIO_2 a glass like insulating material. The gate material is made up of metal conductor .Thus going from gate to substrate, we can have metal oxide semi conductor which is where the term MOSFET comes from.

Since the gate is insulated from the rest of the component, the MOSFET is sometimes referred to as an insulated gate FET or IGFET.

The foundation of the MOSFET is called the substrate. This material is represented in the schematic symbol by the center line that is connected to the source.

In the symbol for the MOSFET, the arrow is placed on the substrate. As with JFET an arrow pointing in represents an N-channel device, while an arrow pointing out represents p-channel device.

CONSTRUCTION OF AN N-CHANNEL MOSFET :

The N- channel MOSFET consists of a lightly doped p type substance into which two heavily doped n+ regions are diffused as shown in the Fig. These n+ sections, which will act as source and drain.

A thin layer of insulation silicon dioxide (SIO_2) is grown over the surface of the structure, and holes are cut into oxide layer, allowing contact with the source and drain. Then the gate metal area is overlaid on the oxide, covering the entire channel region.Metal contacts are made to drain and source and the contact to the metal over the channel area is the gate terminal.The metal area of the gate, in conjunction with the insulating dielectric oxide layer and the semiconductor channel, forms a parallel plate capacitor. The insulating layer of Sio2 Is the reason why this device is called the insulated gate field effect transistor. This layer results in an extremely high input resistance (10 10 to 10power 150hms) for MOSFET.

DEPLETION MOSFET

The basic structure of D –MOSFET is shown in the fig. An N-channel is diffused between source and drain with the device an appreciable drain current I_{DSS} flows foe zero gate to source voltage, $V_{GS}=0$.



Depletion mode operation:-

- 1) The above fig shows the D-MOSFET operating conditions with gate and source terminals shorted together ($V_{GS}=0V$)
- 2) At this stage $I_D = I_{DSS}$ where $V_{GS} = 0V$, with this voltage V_{DS} , an appreciable drain current I_{DSS} flows.
- 3) If the gate to source voltage is made negative i.e. V_{GS} is negative .Positive charges are induced in the channel through the SIO₂ of the gate capacitor.
- 4) Since the current in a FET is due to majority carriers(electrons for an N-type material), the induced positive charges make the channel less conductive and the drain current drops as V_{GS} is made more negative.
- 5) The re distribution of charge in the channel causes an effective depletion of majority carriers , which accounts for the designation depletion MOSFET.
- 6) That means biasing voltage V_{GS} depletes the channel of free carriers This effectively reduces the width of the channel , increasing its resistance.
- 7) Note that negative V_{GS} has the same effect on the MOSFET as it has on the JFET.



8) As shown in the fig above, the depletion layer generated by V_{GS} (represented by the white space between the insulating material and the channel) cuts into the channel, reducing its width. As a result , $I_{D} < I_{DSS}$. The actual value of I_{D} depends on the value of I_{DSS} , V_{GSOFF} and V_{GS}

Enhancement mode operation of the D-MOSFET:-

- 1) This operating mode is a result of applying a positive gate to source voltage V_{GS} to the device.
- 2) When V_{GS} is positive the channel is effectively widened. This reduces the resistance of the channel allowing I_D to exceed the value of I_{DSS}
- 3) When V_{GS} is given positive the majority carriers in the p-type are holes. The holes in the P type substrate are repelled by the +ve gate voltage.
- 4) At the same time, the conduction band electrons (minority carriers) in the P type material are attracted towards the channel by the +gate voltage.
- 5) With the build up of electrons near the channel, the area to the right of the physical channel effectively becomes an N type material.
- 6) The extended n type channel now allows more current, $I_D > I_{DSS}$



Characteristics of Depletion MOSFET:-

The fig. shows the drain characteristics for the N channel depletion type MOSFET

- 1) The curves are plotted for both V_{GS} positive and V_{GS} negative voltages
- 2) When $V_{GS} = 0$ and negative the MOSFET operates in depletion mode when V_{GS} is positive ,the MOSFET operates in the enhancement mode.
- 3) The difference between JFET and D MOSFET is that JFET does not operate for positive values of V_{GS} .
- 4) When $V_{DS}=0$, there is no conduction takes place between source to drain, if $V_{GS} < 0$ and $V_{DS} > 0$ then Id increases linearly.
- 5) But as V_{GS} ,0 induces positive charges holes in the channel, and controls the channel width. Thus the conduction between source to drain is maintained as constant, i.e. I_D is constant.
- 6) If $V_{GS} > 0$ the gate induces more electrons in channel side, it is added with the free electrons generated by source. again the potential applied to gate determines the channel width and maintains constant current flow through it as shown in Fig



TRANSFER CHARACTERISTICS:-

The combination of 3 operating states i.e. $V_{GS} = 0V$, $V_{GS} < 0V$, $V_{GS} > 0V$ is represented by the D MOSFET transconductance curve shown in Fig.



- 1) Here in this curve it may be noted that the region AB of the characteristics similar to that of JFET.
- 2) This curve extends for the positive values of V_{GS}
- 3) Note that $I_D = I_{DSS}$ for $V_{GS} = 0V$ when V_{GS} is negative, $I_D < I_{DSS}$ when $V_{GS} = V_{GS}$ (off), I_D is reduced to approximately 0mA. Where V_{GS} is positive $I_D > I_{DSS}$. So obviously Idss is not the maximum possible value of I_D for a MOSFET.
- 4) The curves are similar to JFET so that the D MOSFET have the same transconductance equation.

E-MOSFETS

The E MOSFET is capable of operating only in the enhancement mode. The gate potential must be positive w.r.t to source.



- 1) when the value of $V_{GS} = 0V$, there is no channel connecting the source and drain materials.
- 2) As aresult, there can be no significant amount of drain current.
- 3) When $V_{GS} = 0$, the Vdd supply tries to force free electrons from source to drain but the presence of p-region does not permit the electrons to pass through it. Thus there is no drain current at $V_{GS} = 0$,
- 4) If V_{GS} is positive, it induces a negative charge in the p type substrate just adjacent to the SIO₂ layer.

- 5) As the holes are repelled by the positive gate voltage, the minority carrier electrons attracted toward this voltage. This forms an effective N type bridge between source and drain providing a path for drain current.
- 6) This +ve gate voltage forma a channel between the source and drain.
- 7) This produces a thin layer of N type channel in the P type substarate. This layer of free electrons is called N type inversion layer.



- 8) The minimum V_{GS} which produces this inversion layer is called threshold voltage and is designated by V_{GS} (th). This is the point at which the device turns on is called the threshold voltage V_{GS} (th)
- 9) When the voltage V_{GS} is $< V_{GS}$ (th) no current flows from drain to source.
- 10) How ever when the voltage $V_{GS} > V_{GS}$ (th) the inversion layer connects the drain to source and we get significant values of current.

CHARACTERISTICS OF E MOSFET: 1. DRAIN CHARACTERISTICS:

The volt ampere drain characteristics of an N-channel enhancement mode MOSFET are given in.



2. TRANSFER CHARACTERISTICS:

- 1) The current I_{DSS} at $V_{GS} \le 0$ is very small beinf of the order of a few nano amps.
- 2) As V_{GS} is made +ve, the current I_D increases slowly at forst, and then much more rapidly with an increase in V_{GS} .
- 3) The standard transconductance formula will not work for the E MOSFET.
- 4) To determine the value of I_D at a given value of VGs we must use the following relation

$$I_D = K[V_{GS} - V_{GS(Th)}]^2$$

Where K is constant for the MOSFET . found as

$$K = \frac{Id(on)}{[vgs(on) - Vgs(Th)]2}$$

From the data specification sheets, the 2N7000 has the following ratings.

 $I_D(on) = 75 \text{mA}(\text{minimum}).$

And V_{GS} (th)=0.8(minimum)



APPLICATION OF MOSFET

One of the primary contributions to electronics made by MOSFETs can be found in the area of digital (computer electronics). The signals in digital circuits are made up of rapidly switching dc levels. This signal is called as a rectangular wave ,made up of two dc levels (or logic levels). These logic levels are 0V and +5V.

A group of circuits with similar circuitry and operating characteristics is referred to as a logic family. All the circuits in a given logic family respond to the same logic levels, have similar speed and power-handling capabilities, and can be directly connected together. One such logic family is complementary MOS (or CMOS) logic. This logic family is made up entirely of MOSFETs.

COMPARISON OF MOSFET WITH JFET

- a. In enhancement and depletion types of MOSFET, the transverse electric field induced across an insulating layer deposited on the semiconductor material controls the conductivity of the channel.
- b. In the JFET the transverse electric field across the reverse biased PN junction controls the conductivity of the channel.
- c. The gate leakage current in a MOSFET is of the order of 10^{-12} A. Hence the input resistance of a MOSFET is very high in the order of 10^{10} to $10^{15} \Omega$. The gate leakage current of a JFET is of the order of 10^{-9} A., and its input resistance is of the order of $10^{8}\Omega$.

- d. The output characteristics of the JFET are flatter than those of the MOSFET, and hence the drain resistance of a JFET (0.1 to $1M\Omega$) is much higher than that of a MOSFET (1 to $50k\Omega$).
- e. JFETs are operated only in the depletion mode. The depletion type MOSFET may be operated in both depletion and enhancement mode.
- f. Comparing to JFET, MOSFETs are easier to fabricate.
- g. Special digital CMOS circuits are available which involve near zero power dissipation and very low voltage and current requirements. This makes them suitable for portable systems.