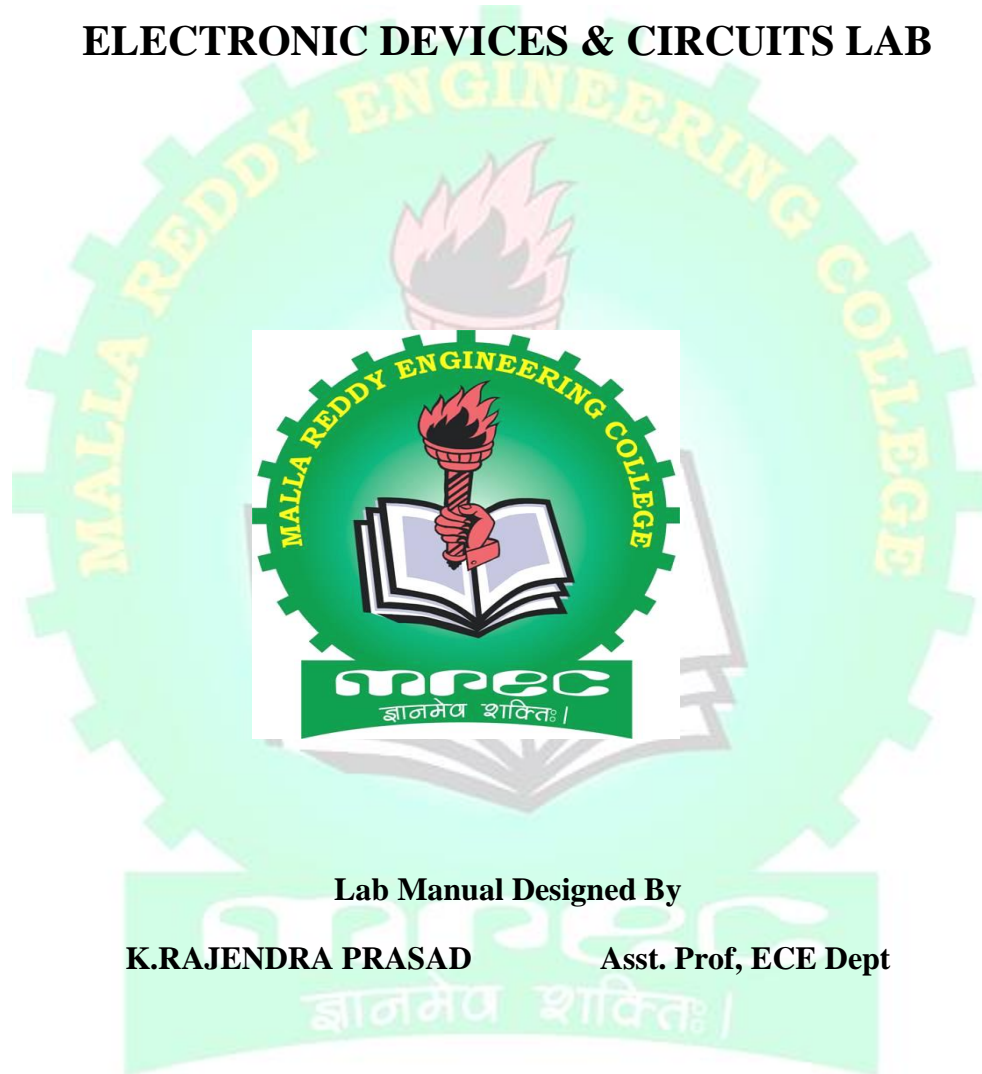


**DEPARTMENT OF ELECTRONICS AND COMMUNICATION
ENGINEERING**

LAB MANUAL

FOR

ELECTRONIC DEVICES & CIRCUITS LAB



Lab Manual Designed By

K.RAJENDRA PRASAD

Asst. Prof, ECE Dept

**MALLA REDDY ENGINEERING COLLEGE
(AUTONOMOUS)**

**NAAC accredited with 'A' Grade
Maisammaguda, Dhulapally, (post via Kompally)
Secunderabad -500100.AP.**

IMPORTANCE OF EDC LAB

“A practical approach is probably the best approach to mastering a subject and gaining a clear insight.”

Electronic Devices and Circuits lab covers those practical oriented Electronic circuits that are very essential for the students to solidify their theoretical concepts. This provides a communication bridge between the theory and practical world of the electronic circuits. The knowledge of these practical are very essential for the engineering students. All of these practical are arranged on the modern electronic trainer boards.

The lab section consists of Diode circuits. Some of the very useful diode based circuits. Labs concerning over this part provides the elementary knowledge of the subject. It also provides some sort of introduction to the lab equipments. This lab also describes the Bipolar Junction Transistor based circuits. Different configurations of BJT amplifier are discussed in this part of the book .Each and every practical provides a great in depth practical concepts of BJT. It also covers some other useful features such as biasing concepts, different type of biasing technique and load line concept, Oscillators and Feedback amplifiers etc. And this lab consists of Field Effect Transistor (FET); one of the leading technologies in electronics is discussed. It gives the introduction to the FET based electronic circuits.



ELECTRONIC DEVICES AND CIRCUITS LAB

S.No	LIST OF EXPERIMENTS	Page No
1	Forward & Reverse Bias Characteristics of PN Junction Diode	1 - 4
2	Zener Diode Characteristics and Zener as Voltage Regulator	5 - 9
3	Rectifiers Without Filters (Full Wave & Half wave)	10 - 13
4	Rectifiers With Filters (Full Wave & Half wave)	14 – 16
5	Input & Output Characteristics of Transistor in CB Configuration	17 - 20
6	Input & Output Characteristics of Transistor in CE Configuration	21 - 24
7	Input & Output Characteristics of Transistor in CC Configuration	25 - 28
8	Field Effect Transistor Characteristics (Using any Simulation Software)	29 – 32
9	SCR Characteristics (Using any Simulation Software)	33 - 36
10	UJT Characteristics (Using any Simulation Software)	37 - 40
ADD ON EXPERIMENTS		
11	Frequency Response of Common Emitter Amplifier	41 - 44

1. FORWARD & REVERSE BIAS CHARACTERISTICS OF PN JUNCTION DIODE

AIM:- 1. To Plot the Volt -Ampere Characteristics of PN Junction diode under Forward and Reverse bias Conditions.


2. To find the static and dynamic forward bias resistance and reverse bias resistance.

APPARATUS REQUIRED:-


- | | |
|----------------------------------|-------|
| 1. IN 4007 Diode (Silicon) | 1.No. |
| 2. OA79(Ge) | 1.No. |
| 3. Resistor $1K\Omega$ | 1.No. |
| 4. 0-20 mA DC Ammeter | 1.No. |
| 5. 0-200 μ A DC Ammeter | 1.No. |
| 6. 0-20 V DC Voltmeter. | 1.No. |
| 7. 0-30 V Regulated Power Supply | 1.No. |
| 8. Bread Board | 1.No. |
| 9. Connecting wires | set |

CIRCUIT DIAGRAMS:-

FORWARD BIAS

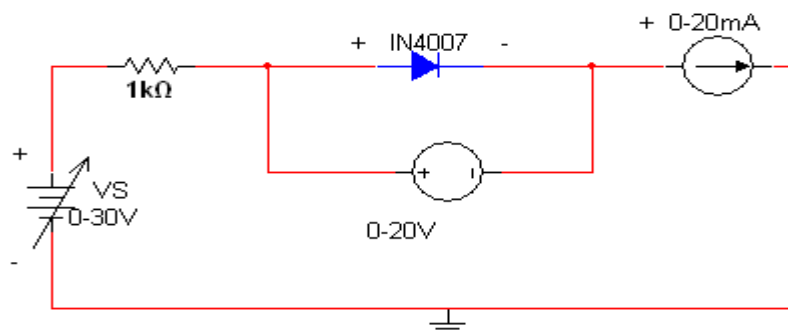

REVERSE BIAS

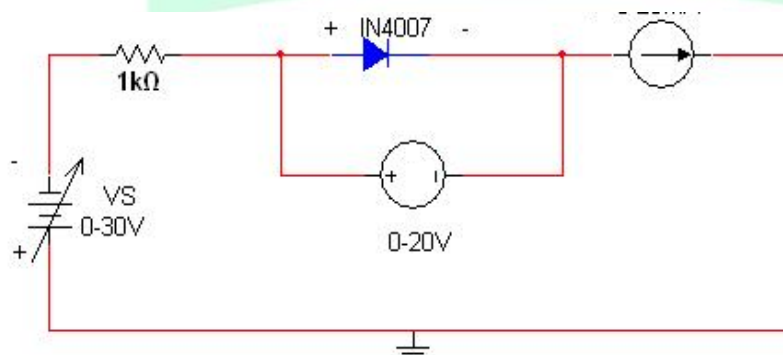

THEORY:

A P-N Junction diode is also called as Semiconductor diode (Ge or Si). When a semiconductor is doped with p type impurity on one half and with N type impurity on the other half and heated to a temperature of 1200⁰C then a P-N Junction diode is formed. Junction diode can work in two types of biases.

FORWARD BIAS:

When P-type (Anode) is connected to +ve terminal and n- type (cathode) is connected to -ve terminal of the supply voltage, is known as forward bias. The potential barrier is reduced when diode is in the forward biased condition. At some forward voltage, the potential barrier altogether eliminated and current starts flowing through the diode and also in the circuit. The diode is said to be in ON state. The current increases with increasing forward voltage due to majority carriers take part in conduction of current.

REVERSE BIAS:

When N-type (cathode) is connected to +ve terminal and P-type (Anode) is connected -ve terminal of the supply voltage is known as reverse bias and the potential barrier across the junction increases. Therefore, the junction resistance becomes very high and a very small current (reverse saturation current) flows in the circuit. The diode is said to be in OFF state. The reverse bias current is due to minority charge carriers.

CUT IN VOLTAGE:

The Forward Voltage at which the current starts to rise abruptly is known as Cut -In voltage of the diode. For Ge is 0.3V, For Si is 0.7V.

PROCEDURE:**FORWARD BIAS CHARACTERISTICS:**

1. Make the Circuit connection as per the Circuit Diagram on the bread board
2. The regulated Power supply is switched ON and the source voltage is slowly increased and the voltage across the PN Junction diode insteps of 0.1Volt is noted down and the Corresponding diode currents are noted down under forward bias Condition in table given below.
3. The graph V_f versus I_f is plotted on the graph Sheet to the scale.
4. The dynamic forward bias resistance of the diode is calculated from the graph

$$r = \frac{\Delta V}{\Delta I}$$

5. The cut in Voltage of the diode is observed and noted down.

TABLE:**FORWARD BIAS CHARACTERISTICS:**

S.No	Forward Bias Voltage (V _f) in volts		Forward Bias Current (I _f) in mA	
	Ge	Si	Ge	Si
1				
2				
3.				
4.				
5.				
6.				
7.				


REVESE BIAS CHARACTERISTICS:

1. The Circuit is connected as per the Circuit Diagram on the bread board.
2. The regulated Power supply is switched on and the source voltage is slowly increased and the voltage across the PN Junction diode insteps of 1Volt is noted down and the Corresponding diode currents are noted down under reverse bias Condition in the table given below.
3. The graph V_r versus I_r is plotted on the graph Sheet to the scale.
4. the dynamic reverse bias resistance of the diode is calculated from the graph.

$$r = \frac{\Delta V}{\Delta I}$$

REVERSE BIAS CHARACTERISTICS:

S.No	Reverse Bias Voltage (V _r) in Volts		Reverse Bias Current (I _r) in μ A	
	Ge	Si	Ge	Si
1				
2				
3.				
4.				
5.				
6.				
7.				
8.				
9.				
10.				

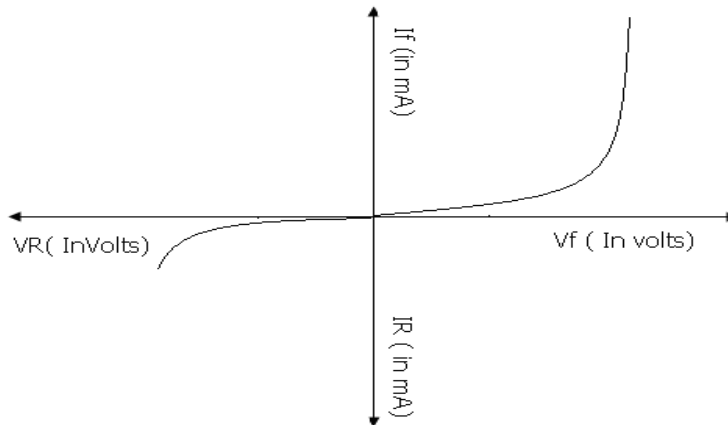MODEL GRAPH:**RESULT :**

The V-I Characteristics of the PN Junction diode are plotted for the Both forward and reverse bias conditions and Calculated the dynamic forward and reverse bias resistance.

QUESTIONS:

1. Define forward resistance and Reverse Resistance, What are the approximate values from the graph?
2. Define Cut in voltage of a diode, mention the cut in voltage for Ge & Si?
3. Explain the working of PN Junction in Forward and Reverse Bias conditions?
4. Define depletion region of a diode?
5. What is meant by transition & space charge capacitance of a diode?
6. Is the V-I relationship of a diode Linear or Exponential?
7. Define cut-in voltage of a diode and specify the values for Si and Ge diodes?
8. What are the applications of a p-n diode?

2. ZENER DIODE CHARACTERISTICS AND ZENER AS VOLTAGE REGULATOR


AIM:- To Obtain the Voltage – Current characteristics of a Zener diode and find out the Zener Break down Voltage from the Characteristics.

APPARATUS REQUIRED:-

- | | |
|-------------------------------------|------|
| 1. D.C Regulated Power Supply 0-30V | 1No. |
| 2. Zener Diodes -3.9V,-8.2V Each | 1No. |
| 3. Resistor 1 KΩ & 680 Ω | 1No. |
| 4. DC Ammeter 0-20mA | 1No. |
| 5. DC Voltmeters 0-1V,0-10V Each | 1No. |
| 6. Decade Resistance Box | 1No. |
| 7. Bread Board. | 1No. |

CIRCUIT DIAGRAMS:-

REVERSE BIAS CHARACTERISTICS:-

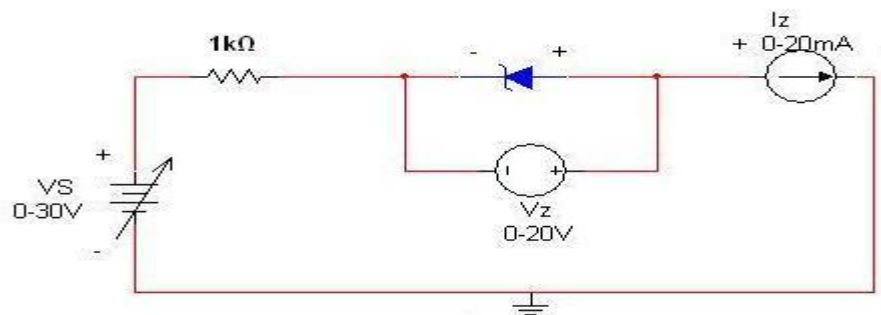


TABULAR FORMS:-

CASE I. REVERSE BIAS CHARACTERISTICS:-

S.No	Source voltage(Vs) in volts	Zener diode voltage (Vz) in volts	Zener diode current (Iz) in mA
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			
11			

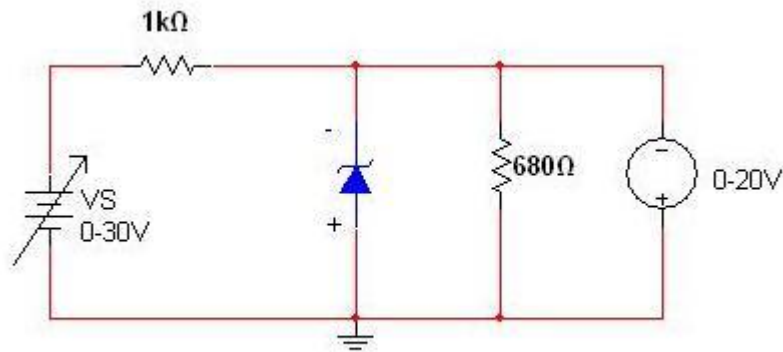
CASE II. REGULATION WITH VARYING INPUT VOLTAGE :



TABULAR COLUMN:

S. No	Source Voltage(Vs) in Volts	Load voltage (VL) in volts	Load Current (IL) in mA $I_L = V_L / R_L$
1			
2			
3			
4			
5			
6			
7			
8			

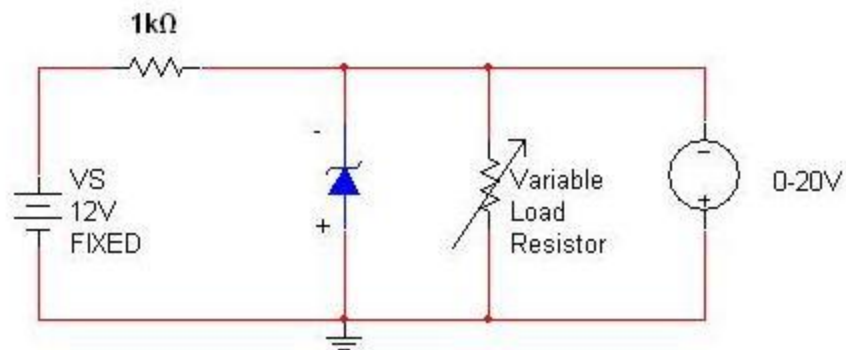CASE III. REGULATION WITH VARYING LOAD RESISTANCE :



TABULAR COLUMN:

S.No	Load Resistance (R_L) in $K\Omega$	Load Voltage(V_L) in Volts	Load Current in mA $I_L = V_L / R_L$
1			
2			
3			
4			
5			
6			
7			
8			

THEORY :**CASE (I) :**

The Diodes which are designed with adequate power dissipation to operate in the break down region are known as Break Down (or) Zener diodes. These diodes are employed as constant voltage sources.

CASE (II) :

- As the input voltage increases, the input current also increases. This increase the current through the Zener Diode with out affecting the load current.
- The increase in the input current will also increases the voltage drop across the series resistance (R_L), thereby keeping the load voltage (V_L) as constant.

CASE (III) :

- When the load resistance decreases the load current increases.
- This causes the Zener current to decrease. As a result of this the input current and voltage drop across series resistance remains constant. Thus the load voltage is kept constant.

PROCEDURE:-**CASE(I) : Reverse bias characteristics**

- Make the connections as per the circuit diagram.
- Switch the DC Regulated power supply and slowly increase the source Voltage and note down the Voltage across Zener diode insteps of the 1Volt and note the Corresponding diode current as per table given below.
- Repeat the above procedure for the 9.1V Zener diode.
- Plot the graph between Voltage across the Zener diode (V_r) Vs current (I_r) through the diode on graph sheet for the both zener Diodes.

CASE (II): REGULATION WITH VARYING INPUT VOLTAGE

1. Make the connections as per the circuit diagram.
2. Keep the input voltage from 0 – 10V in steps of 1 V and note down the readings of source voltage (V_s), Load voltage (V_L), Load current (I_L). c) Plot the graph between I_L Versus V_L .

CASE(III) : REGULATION WITH VARYING LOAD RESISTANCE


1. Make the connections as per the circuit diagram
2. Keep the input voltage constant at 12V and note down the current without load resistance. Note this as No load voltage.
3. Slowly vary the load resistance in steps of $1K\Omega$ to up to $10K\Omega$ and note down the corresponding meter readings. Calculate the regulation by using the formula.

$$\frac{(V_{NL} - V_{FL})}{V_{FL}}$$
4. Plot the graph between I_L Versus V_L .

ZENER BREAK DOWN VOLTAGE:-

Draw the tangent on the reverse bias Characteristics of the Zener Diode starting from the Knee and touching most of the points of the Curve.


The point where the Tangent intersects the X-axis is the Zener Break down Voltage.

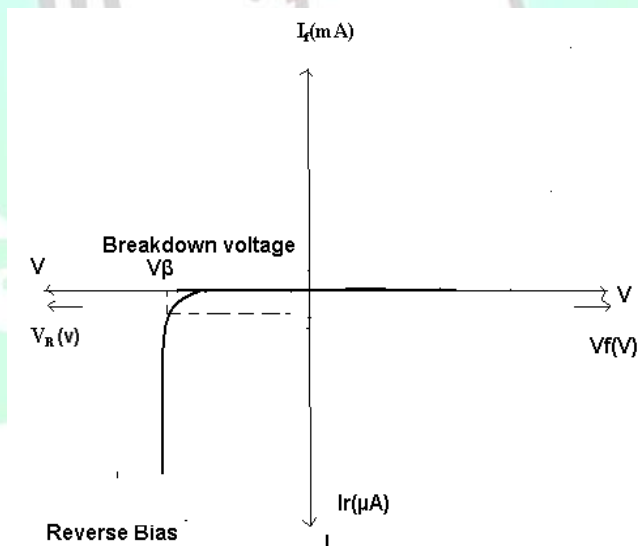MODEL GRAPH:-

RESULT:- The V- I Characteristics of the Zener Diode and the Zener Break Down Voltage from the Characteristics are Observed.

QUESTIONS:

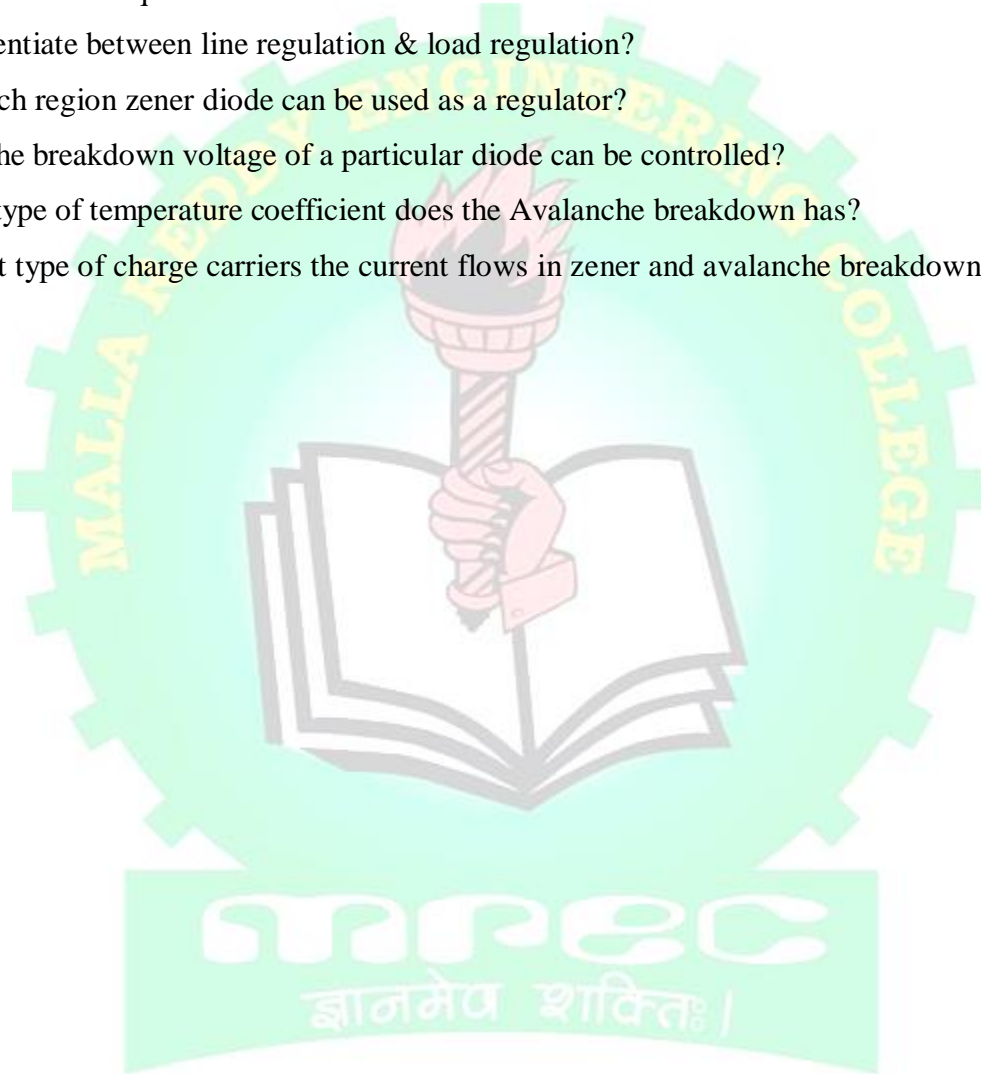1. What type of temp? Coefficient does the zener diode have?
2. If the impurity concentration is increased, how the depletion width effected?
3. Does the dynamic impedance of a zener diode vary?
4. Explain briefly about avalanche and zener breakdowns?
5. Draw the zener equivalent circuit?
6. Differentiate between line regulation & load regulation?
7. In which region zener diode can be used as a regulator?
8. How the breakdown voltage of a particular diode can be controlled?
9. What type of temperature coefficient does the Avalanche breakdown has?
10. By what type of charge carriers the current flows in zener and avalanche breakdown diodes?



3. RECTIFIER WITHOUT FILTERS (HALFWAVE & FULLWAVE)


AIM: To rectify the signal and then to find ripple factor, efficiency and percentage of regulation in full wave and half wave rectifier without filters.

APPARATUS:


1. Transformer 230v / 6v – 0 – 6v
2. Diodes IN4007 2 No
3. Resistance 10k
4. Multimeter
5. Bread Board
6. 20MHz Dual Trace CRO
7. Connecting wires

CIRCUIT DIAGRAM:

HALFWAVE RECTIFIER:

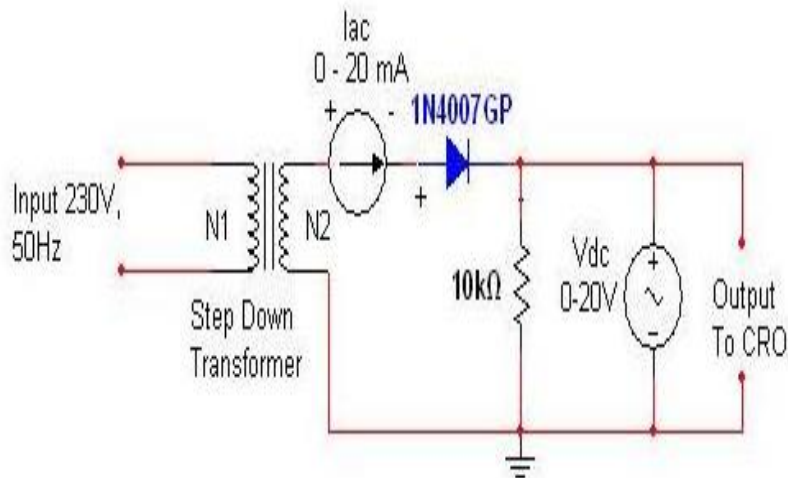

FULLWAVE RECTIFIER:

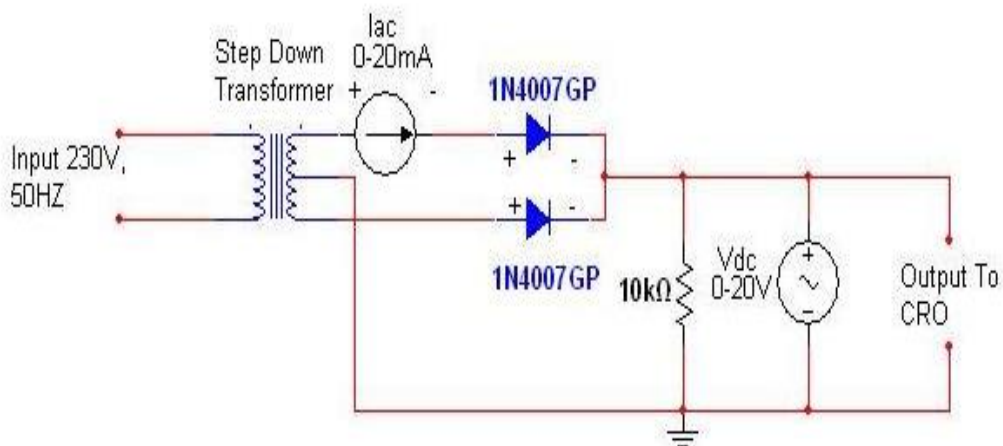

THEORY:

A Half wave Rectifier is one which converts the ac voltage in to a pulsating dc voltage using only one half cycle of the applied voltage. Rectifier conducts during one half cycle only. During positive half-cycle of the input voltage, the diode D1 is in forward bias and conducts through the load resistor R1. Hence the current produces an output voltage across the load resistor R1, which has the same shape as the +ve half cycle of the input voltage.

During the negative half-cycle of the input voltage, the diode is reverse biased and there is no current through the circuit. i.e, the voltage across R1 is zero. The net result is that only the +ve half cycle of the input voltage appears across the load. The average value of the half wave rectified o/p voltage is the value measured on dc voltmeter.

For practical circuits, transformer coupling is usually provided for two reasons.



1. The voltage can be stepped-up or stepped-down, as needed.
2. The ac source is electrically isolated from the rectifier. Thus preventing shock hazards in the secondary circuit.

PROCEDURE:**COMMON TO HALFWAVE RECTIFIER & FULLWAVE RECTIFIER:**

1. Connecting the circuit on bread board as per the circuit diagram
2. Connect the primary of the transformer to main supply i.e. 230V, 50Hz
3. Connect the Multimeter at output terminals and note down the V_{rms} and V_{dc} as per given tabular form.
4. Disconnect load resistance and note down No load voltage V_{dc} .
5. Connect Channel – II of CRO at output terminals and CH – I of CRO at Secondary Input terminals observe and note down the Input and Output Wave form on Graph Sheet

CALCULATIONS:


1. Calculate Ripple Factor $\gamma = \frac{V_{rms}}{V_{dc}}$
2. Calculate Percentage of regulation = $\frac{V_{no\ load} - V_{full\ load}}{V_{full\ load}} \times 100\%$
3. Calculate efficiency $\eta = P_{dc} / P_{ac}$
 $P_{dc} = V_{dc} \times I_{dc} = V_{dc}^2 / R_L$
 $P_{ac} = V_{ac} \times I_{ac}$

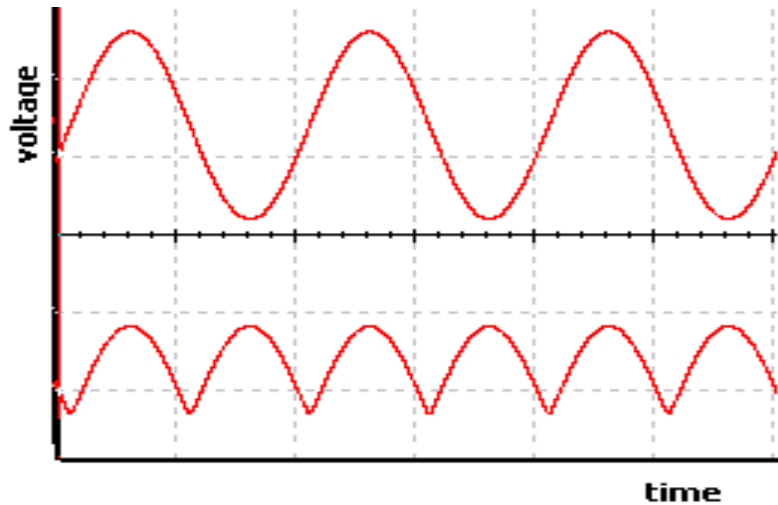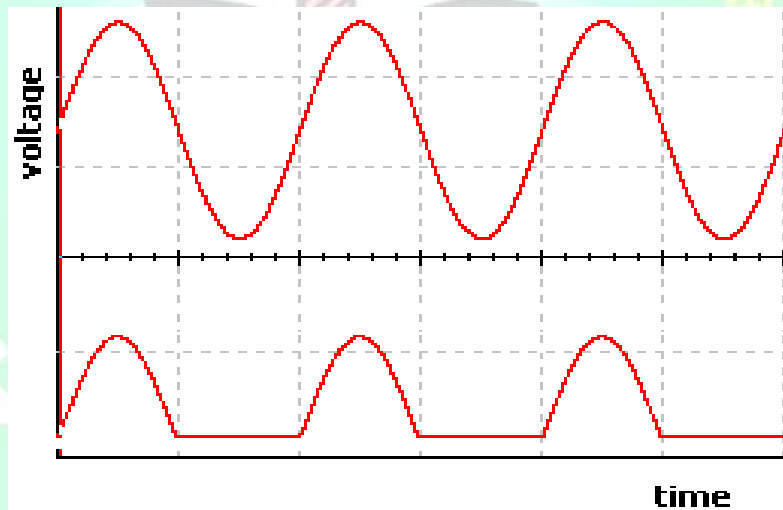WAVE SHAPES:**FULL WAVE WITHOUT FILTER****HALF WAVE WITHOUT FILTER****RESULT:**

Observe Input and Output Wave forms and Calculate ripple factor and percentage of regulation in Full wave and half wave rectifiers without filter.

QUESTIONS:

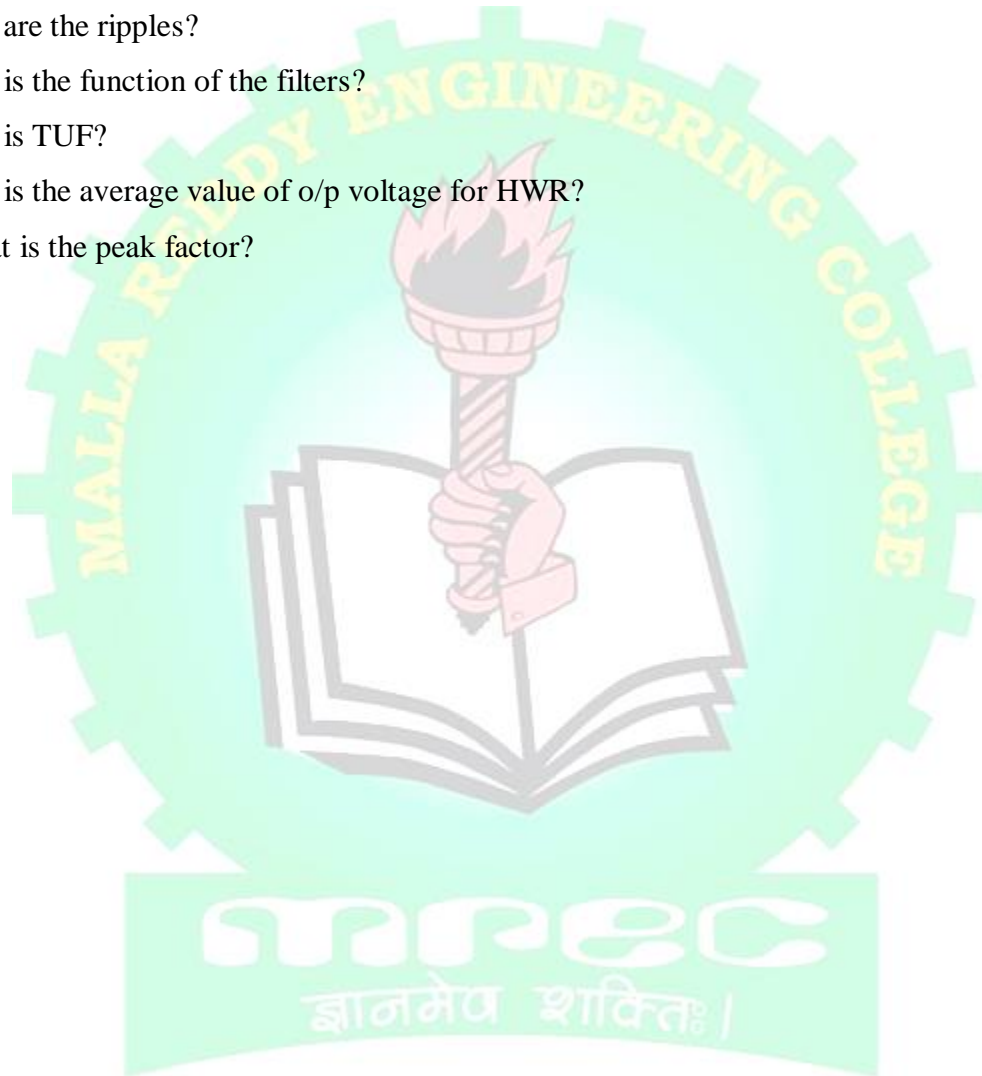1. What is the PIV of Half wave rectifier?
2. What is the Ripple factor, efficiency, % of Regulation of Rectifier?
3. What is the rectifier?
4. What is the difference between the half wave rectifier and full wave Rectifier?
5. What is the o/p frequency of Bridge Rectifier?
6. What are the ripples?
7. What is the function of the filters?
8. What is TUF?
9. What is the average value of o/p voltage for HWR?
10. What is the peak factor?



4. RECTIFIER WITH FILTERS (HALFWAVE & FULLWAVE)


AIM: To rectify the signal and then to find ripple factor in full wave and half wave rectifier with filters.

APPARATUS:


1. Transformer 230v/6v – 0 – 6v
2. Diodes IN4007 - 2 no's
3. Capacitor 470 μ f/35v - 1 no.
4. Decade Inductance Box
5. Resistance 1K
6. Multi meter
7. Bread Board
8. 20MHz Dual Trace CRO
9. Connecting wires




CIRCUIT DIAGRAM:

HALFWAVE RECTIFIER:

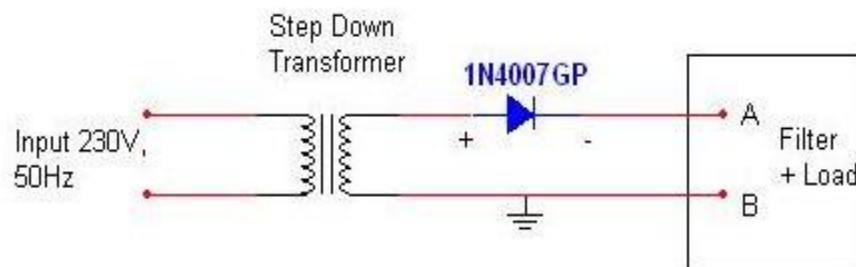

FULLWAVE RECTIFIER :


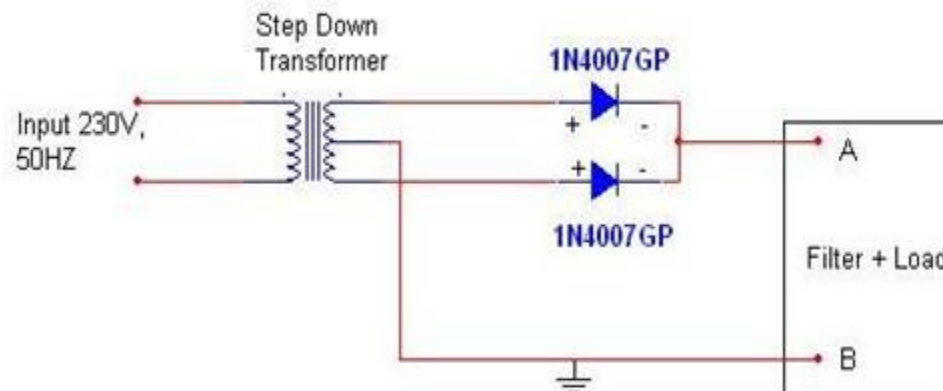


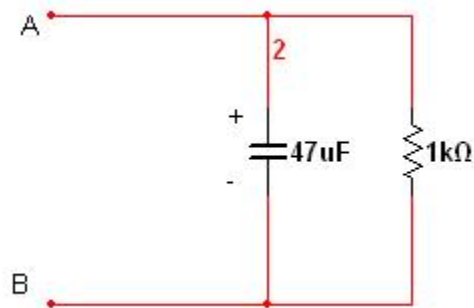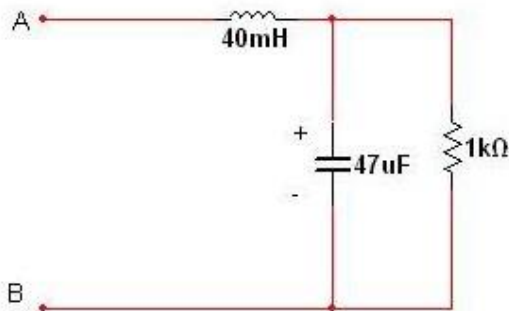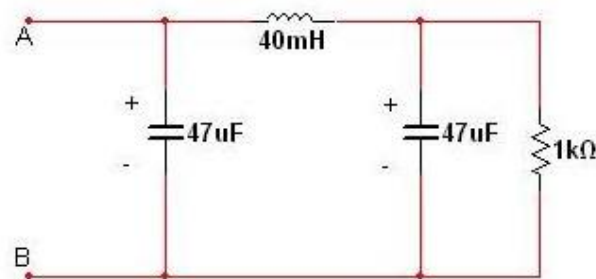C – FILTER:**L-C FILTER:****CLC – FILTER:****PROCEDURE:****FULLWAVE RECTIFIER:**

1. Make the connections as per the circuit diagram
2. Make the connection of primary transformer to main supply i.e. 230V, 50Hz
3. Make the connection of decade resistance box and set the R_L value to 100Ω
4. Make the connection of multimeter at output terminals and vary the load resistance (DRB) from 100Ω to $5K\Omega$ and note down the V_{ac} and V_{dc} as per given tabular form
5. Disconnect load resistance (DRB) and note down No load voltage V_{dc}
6. Make the connection of load resistance at $100K\Omega$ and connect CH – I of Dual Trace CRO at Secondary (Input) terminals, Channel – II of Dual Trace CRO at output terminals and observe and note down the Input and Output Wave form on Graph Sheet

HALFWAVE RECTIFIER:

7. Make the connections as per the circuit diagram and repeat the above procedure from steps 2 to 6 Calculate Ripple Factor $\gamma = V_{rms} / V_{dc}$

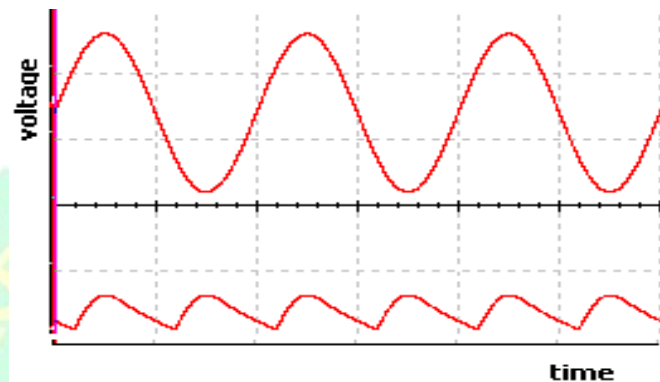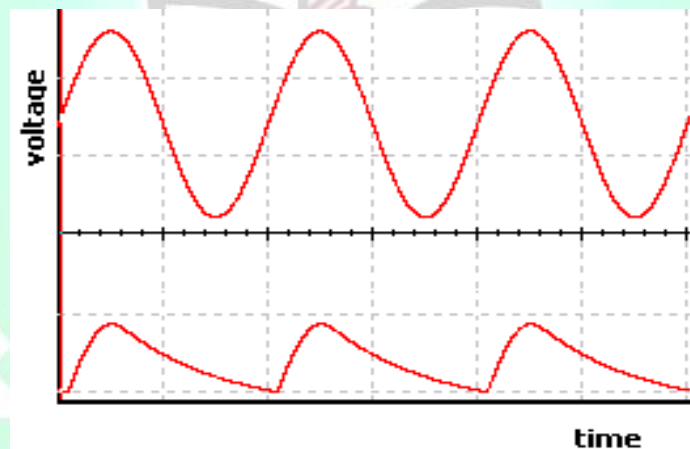WAVE SHAPES:**FULL WAVE WITH FILTER****HALF WAVE WITH FILTER**

RESULT: Observe Input and Output Wave forms and Calculate ripple factor and percentage of regulation in Full wave and Half wave rectifiers with capacitor filter

QUESTIONS:

1. What is the need of filter?
2. Why we are using L & C components in the filter?
3. What are the types of filters?
4. Which is the best among the different types of filters?


5. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR IN CB CONFIGURATION

AIM: To plot the family of input and output characteristics of a transistor connected in Common Base Configuration.

APPARATUS:

1. Transistor BC 107	1No.
2. Resistor $1K\Omega$	1No.
3. Ammeter 0-20mA	2No.
4. Voltmeter 0-20V	2No.
5. Multimeter	1No.
6. 0-30V, 1A Dual Channel powers supply	1No.
7. Bread Board	1No.
8. Connecting wires	set

CIRCUIT DIAGRAM:

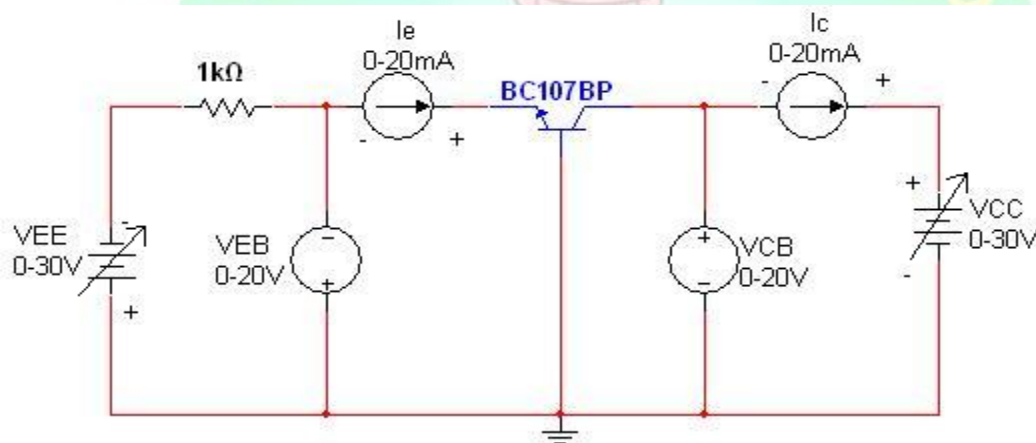

THEORY :

In the common Base configuration input is applied between emitter and base, similarly output is taken from collector and base. Here base of the transistor is common to both input and output circuits and hence the name common base configuration.

Input characteristics are similar to forward bias characteristics of a P-N junction diode. The curve shift left with increase in VCB value. Output characteristics can be obtained by varying the output voltage and noting the output current. The characteristics have been divided into three regions namely active, saturation and cut off region. But BJT has low input resistance and high output resistance in Common Base configuration.

PROCEDURE:

INPUT CHARACTERISTICS:

1. Make the connections as per the circuit diagram.
2. Make VCB open and vary the Power Supply (Channel-1) and note the Values of I_E and V_{BE}

by increasing the I_E in steps of 0.5mA

3. Adjust $V_{CB} = 1V$ (Channel -2) Power supply.

4. Vary the 0-30V (Channel -1) power Supply and note down the Values of I_E and V_{EB} .

5. Repeat the steps 3 & 4 For $V_{CB} = 2V, 3V, 4V$.

TABULAR FORM:-

S.No	$V_{CB} = 0V$		$V_{CB} = 3V$		$V_{CB} = 6V$	
	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$
1	0.1		0.1		0.1	
2	0.2		0.2		0.2	
3	0.3		0.3		0.3	
4	0.4		0.4		0.4	
5.	0.5		0.5		0.5	
6.	0.6		0.6		0.6	
7.	0.7		0.7		0.7	
8.	0.8		0.8		0.8	
9.	0.9		0.9		0.9	

OUTPUT CHARACTERISTICS:-

1. Make the connections as per the circuit diagram

2. Adjust the 0 – 30V (Channel – 1) power supply and fix the value of $I_E = 2mA$

3. Vary the 0 – 30 V (Channel – 2) power supply and note the value of V_{CB} and I_C .

4. Vary the V_{CB} in steps of 1v

5. Repeat steps 2 to 4 for $I_E = 1mA, 1.5mA, 2mA, 2.5mA$

TABULAR FORM:-

S.No	$I_E = 2mA$		$I_E = 4mA$		$I_E = 6mA$	
	$V_{CB}(v)$	$I_C(mA)$	$V_{CB}(v)$	$I_C(mA)$	$V_{CB}(v)$	$I_C(mA)$
1	1		1		1	
2	2		2		2	
3	3		3		3	
4	4		4		4	
5	5		5		5	
6	6		6		6	
7	7		7		7	
8	8		8		8	


Input Impedance $h_{ib} = \Delta V_{BE} / \Delta I_E$ at V_{CB} constant

Output impedance $h_{ob} = \Delta V_{CB} / \Delta I_C$ at I_E constant


Reverse Transfer Voltage Gain $h_{rb} = \Delta V_{BE} / \Delta V_{CB}$ at I_E constant

Forward Transfer Current Gain $h_{fb} = \Delta I_C / \Delta I_E$ at constant V_{CB}

GRAPH:- INPUT CHARACTERISTICS

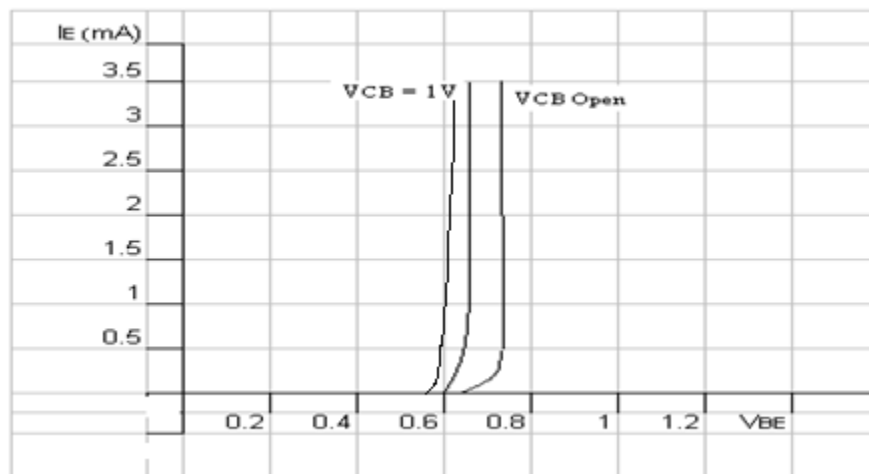

OUTPUT CHARACTERISTICS :

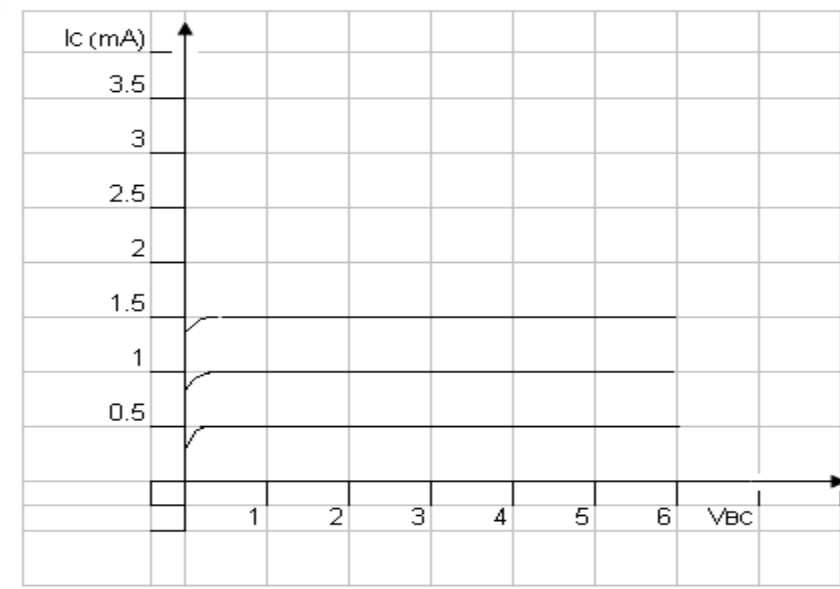

1. Plot the input characteristics by taking I_E on y – axis and V_{EB} on X – axis
2. Plot the output characteristics by taking I_C on y – axis and V_{CB} on X – axis

RESULT: - Input and Output characteristics are plotted

QUESTIONS:

1. Define transistor and mention types of transistors. Draw their symbolic diagram and indicate terminals?
2. What are the three configurations of Transistor?
3. In which region transistor acts as an Amplifier?
4. In which region transistor acts as an Switch?
5. Why transistor is called current controlled device?
6. What is meant by Base width modulation?
7. What is the range of α for the transistor?
8. Draw the input and output characteristics of the transistor in CB configuration?
9. Identify various regions in output characteristics?
10. What are the applications of CB configuration?
11. What are the input and output impedances of CB configuration?
12. Define α (alpha)? What is the relation between α and β ?
13. What is EARLY effect?
14. Draw diagram of CB configuration for PNP transistor?
15. What is the power gain of CB configuration?
16. Which biasing techniques are used for both input and output?


6. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR IN CE CONFIGURATION

AIM: To Plot the Family of input and output Characteristics of a Transistor connected in Common Emitter Configuration.

APPARATUS REQUIRED:

1. Transistor BC 107	1No.
2. Resistor 1K Ω	1.No.
3. Connecting Wires	1 Set
4. Ammeter 0-20mA, 0-500 μ A	1 Each
5. Multimeter	1No.
6. 0-30,1A Dual Channel power supply.	1.No.
7. Bread Board	1No.

CIRCUIT DIAGRAM:

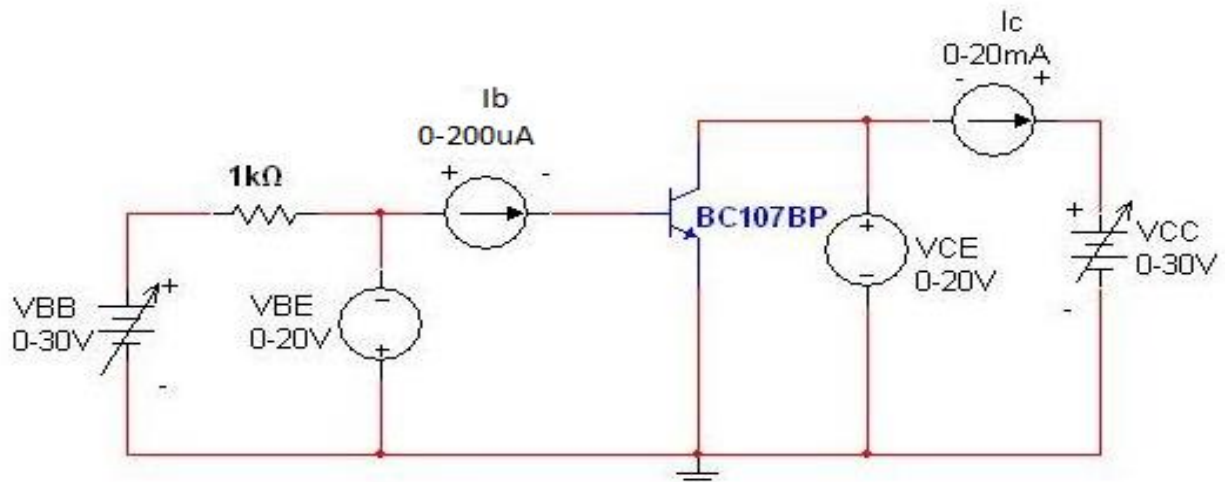

THEORY:

A transistor is a three terminal device. The terminals are emitter, base, collector. In common emitter configuration, input voltage is applied between base and emitter terminals and output is taken across the collector and emitter terminals. Therefore the emitter terminal is common to both input and output. The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement I_B increases less rapidly with V_{BE} . Therefore input resistance of CE circuit is higher than that of CB circuit.

The output characteristics are drawn between I_C and V_{CE} at constant I_B . The collector current varies with V_{CE} upto few volts only. After this the collector current becomes almost constant, and independent of V_{CE} . The value of V_{CE} up to which the collector current changes with V_{CE} is known as Knee voltage. The transistor always operated in the region above Knee voltage, I_C is always constant and is approximately equal to I_B .

PROCEDURE:**INPUT CHARACTERISTICS**

1. Make the connections as per the circuit diagram.
2. Make V_{CE} Open and Vary the 5 V Supply (Channel 1) and note the Values of I_B and V_{BE} , by increasing the I_B in Steps of .5mA.
3. Adjust $V_{CE} = 1V$ in Channel 2 Power supply.
4. Vary the 0-5V (Channel 1) power Supply and note the Values of I_B and V_{BE}
5. Repeat the Steps 3 and 4 for $V_{CE} = 2V, 3V, 4V$.
6. Need not connect 0-2mA (I_C Measurement), Ammeter while taking the input Characteristics.

TABULAR FORM:

S.No	VCE = 0V		VCE = 3V		VCE = 6V	
	VBE(V)	IB(uA)	VBE(V)	IB(uA)	VBE(V)	IB(uA)
1	0.1		0.1		0.1	
2	0.2		0.2		0.2	
3	0.3		0.3		0.3	
4	0.4		0.4		0.4	
5	0.5		0.5		0.5	
6	0.6		0.6		0.6	
7	0.7		0.7		0.7	
8	0.8		0.8		0.8	

OUTPUT CHARACTERISTICS:

1. Make the connections as per the circuit diagram.
2. Connect 0-500 μ A Ammeter in place of 0-20mA.
3. Adjust 0-5V (Channel -1) power Supply and fix the Values of $I_B = 10 \mu$ A
4. Vary the V_{CE} 0-20V (Channel -2) power supply and note down the Values of the I_C and V_{CE} . Vary in the Steps of 1V.
5. Repeat the steps 3 & 4 for $I_B = 30 \mu$ A, 40μ A, 50μ A .

TABULAR FORM: _

1. Plot the input characteristics by taking I_B on Y-Axis and V_{BE} on X-Axis.
2. Plot the output characteristics by taking I_C on the Y-Axis and V_{CE} on X -Axis

S.No	$I_B = 10 \mu A$		$I_B = 20 \mu A$		$I_B = 30 \mu A$	
	$V_{CE}(mA)$	$I_c(mA)$	$V_{CE}(mA)$	$I_c(mA)$	$V_{CE}(mA)$	$I_c(mA)$
1	1		1		1	
2	2		2		2	
3	3		3		3	
4	4		4		4	
5	5		5		5	
6	6		6		6	
7	7		7		7	
8	8		8		8	
9	9		9		9	
10	10		10		10	


Input Impedance $h_{ie} = \Delta V_{BE} / \Delta I_B$ at V_{CE} constant


Output impedance $h_{oe} = \Delta V_{CE} / \Delta I_C$ at I_B constant

Reverse Transfer Voltage Gain $h_{re} = \Delta V_{BE} / \Delta V_{CE}$ at I_B constant

Forward Transfer Current Gain $h_{fe} = \Delta I_C / \Delta I_B$ at constant V_{CE}

GRAPH: INPUT CHARACTERISTICS

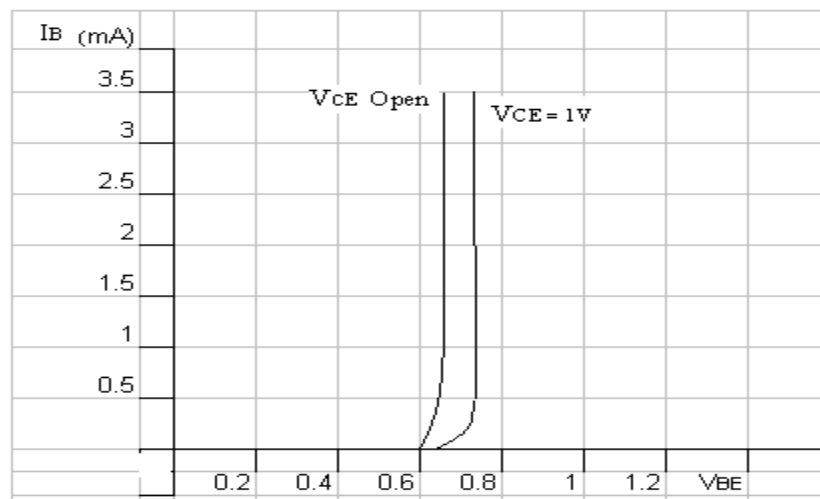

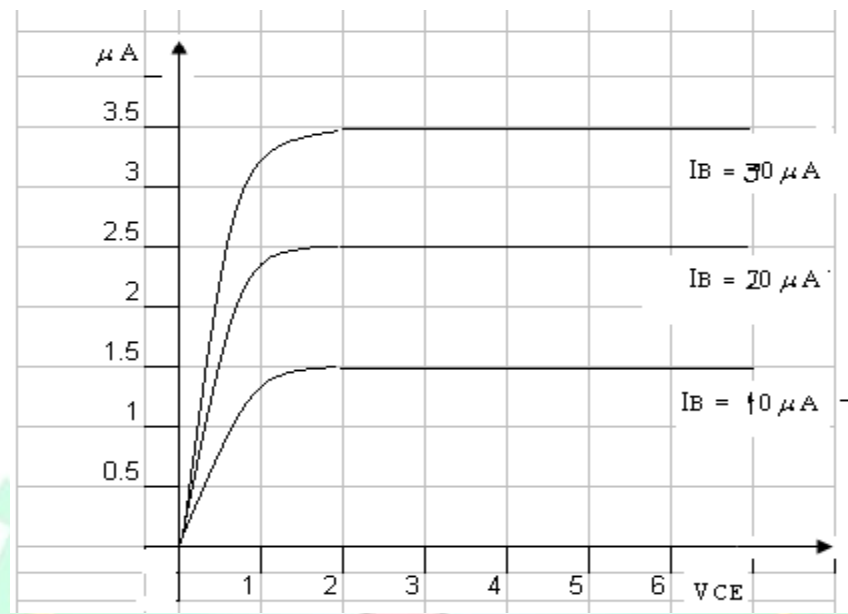OUTPUT CHARACTERISTICS:**RESULT:**

Input and output characteristics of CE are plotted.

QUESTIONS:

1. What is meant by α and β in a CE transistor Characteristics?
2. What are the input and output impedances of CE configuration?
3. Identify various regions in the output characteristics?
4. what is the relation between α and β ?
5. Define current gain in CE configuration?
6. Why CE configuration is preferred for amplification?
7. What is the phase relation between input and output?
8. Draw diagram of CE configuration for PNP transistor?
9. What is the power gain of CE configuration?
10. What are the applications of CE configuration?


7. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR IN CC CONFIGURATION

AIM: To Plot the Family of input and output Characteristics of a Transistor connected in Common Collector Configuration.

APPARATUS REQUIRED:

- | | |
|---------------------------------------|--------|
| 1. Transistor BC 107 | 1No. |
| 2. Resistor $1K\Omega$ | 1.No. |
| 3. Connecting Wires | 1 Set |
| 4. Ammeter 0-20mA, 0-500 μA | 1 Each |
| 5. Multimeter | 1No. |
| 6. 0-30,1A Dual Channel power supply. | 1.No. |
| 7. Bread Board | 1No. |

CIRCUIT DIAGRAM:

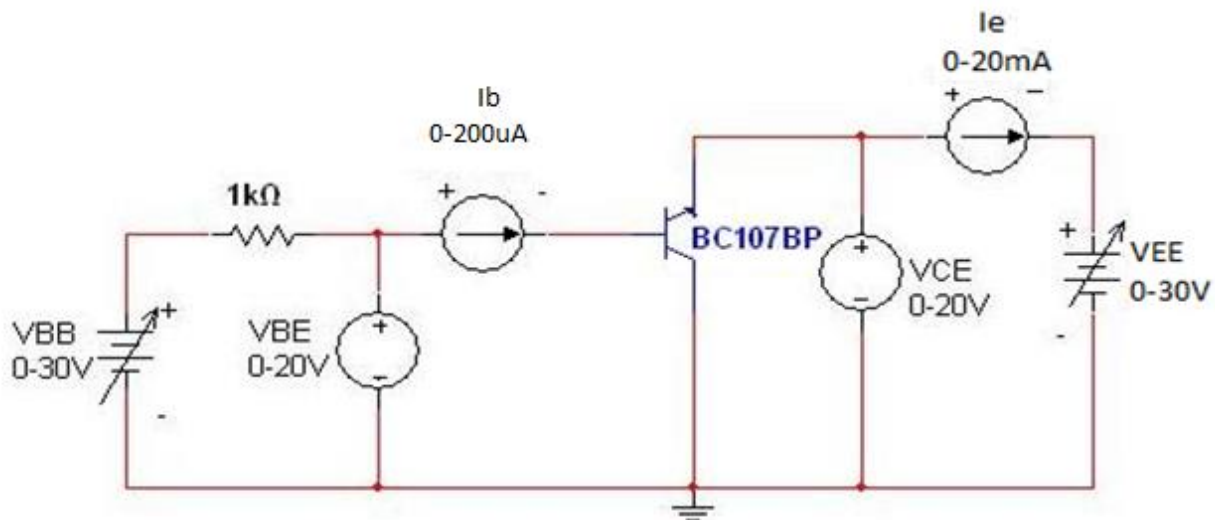

THEORY:

A transistor is a three terminal device. The terminals are emitter, base, collector. In common collector configuration, input voltage is applied between base and collector terminals and output is taken across the collector and emitter terminals. Therefore the collector terminal is common to both input and output. The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-collector junction of the transistor is forward biased. As compared to CB arrangement I_B decreases rapidly with V_{BE} .

The output characteristics are drawn between I_E and V_{CE} at constant I_B . The emitter current varies with V_{CE} upto few volts only. After this the emitter current becomes almost constant, and independent of V_{CE} . The value of V_{CE} up to which the emitter current changes with V_{CE} is known as Knee voltage. The transistor always operated in the region above Knee voltage, I_E is always constant and is approximately equal to I_B .

PROCEDURE:**INPUT CHARACTERISTICS**

1. Make the connections as per the circuit diagram.
2. Make V_{CE} Open and Vary the 5 V Supply (Channel 1) and note the Values of I_B and V_{CB} , by increasing the I_B in Steps of .5mA.
3. Adjust $V_{CE} = 1V$ in Channel 2 Power supply.
4. Vary the 0-5V (Channel 1) power Supply and note the Values of I_B and V_{BE}
5. Repeat the Steps 3 and 4 for $V_{CE} = 2V, 3V, 4V$.
6. Need not connect 0-2mA (I_C Measurement), Ammeter while taking the input Characteristics.

TABULAR FORM:

S.No	VCE = 2V		VCE = 4V		VCE = 6V	
	VBC(V)	IB(uA)	VBC(V)	IB(uA)	VBC(V)	IB(uA)
1	0.1		0.1		0.1	
2	0.2		0.2		0.2	
3	0.3		0.3		0.3	
4	0.4		0.4		0.4	
5	0.5		0.5		0.5	
6	0.6		0.6		0.6	
7	0.7		0.7		0.7	
8	0.8		0.8		0.8	

OUTPUT CHARACTERISTICS:

1. Make the connections as per the circuit diagram.
2. Connect 0-500 μ A Ammeter in place of 0-20mA.
3. Adjust 0-5V (Channel -1) power Supply and fix the Values of $I_B = 20 \mu$ A
4. Vary the V_{CE} 0-20V (Channel -2) power supply and note down the Values of the I_E and V_{CE} . Vary in the Steps of 1V.
5. Repeat the steps 3 & 4 for $I_B = 40 \mu$ A, 60μ A, 80μ A .

TABULAR FORM: .

3. Plot the input characteristics by taking I_B on Y-Axis and V_{BE} on X-Axis.
4. Plot the output characteristics by taking I_E on the Y-Axis and V_{CE} on X -Axis

S.No	$I_B = 20 \mu A$		$I_B = 40 \mu A$		$I_B = 60 \mu A$	
	$V_{CE}(mA)$	$I_E(mA)$	$V_{CE}(mA)$	$I_E(mA)$	$V_{CE}(mA)$	$I_E(mA)$
1	1		1		1	
2	2		2		2	
3	3		3		3	
4	4		4		4	
5	5		5		5	
6	6		6		6	
7	7		7		7	
8	8		8		8	
9	9		9		9	
10	10		10		10	


Input Impedance $h_{ie} = \Delta V_{BC} / \Delta I_B$ at V_{CE} constant


Output impedance $h_{oe} = \Delta V_{CE} / \Delta I_E$ at I_B constant

Reverse Transfer Voltage Gain $h_{re} = \Delta V_{BC} / \Delta V_{CE}$ at I_B constant

Forward Transfer Current Gain $h_{fe} = \Delta I_E / \Delta I_B$ at constant V_{CE}

GRAPH: INPUT CHARACTERISTICS

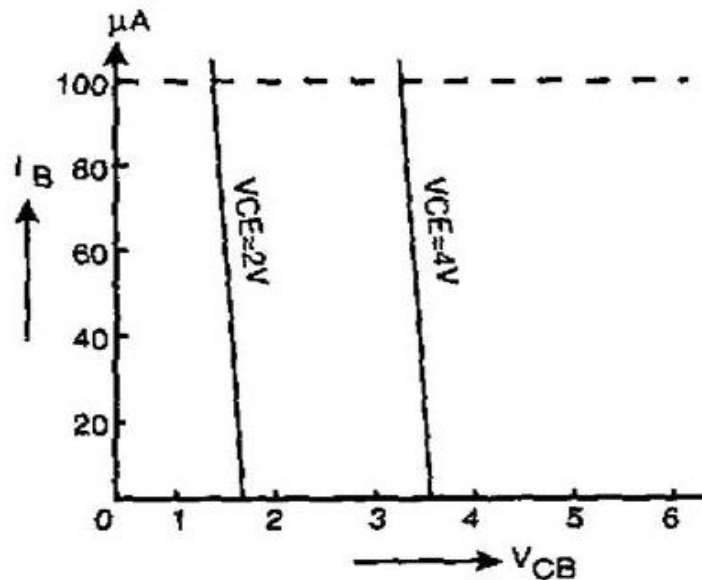

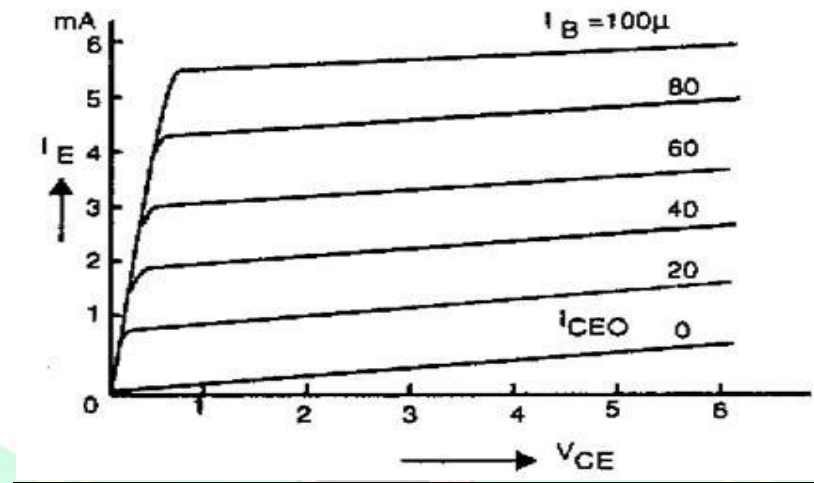OUTPUT CHARACTERISTICS:**RESULT:**

Input and output characteristics of CC are plotted.

QUESTIONS:

11. What is meant by α and β in a CC transistor Characteristics?
12. What are the input and output impedances of CC configuration?
13. Identify various regions in the output characteristics?
14. what is the relation between α and β ?
15. Define current gain in CC configuration?
16. What is the phase relation between input and output?
17. Draw diagram of CC configuration for PNP transistor?
18. What is the power gain of CC configuration?
19. What are the applications of CC configuration?


8. FET CHARACTERISTICS

AIM: To study the drain and transfer characteristics of JFET and find the Drain resistance, transconductance and amplification factor of a JFET using MULTISIM.

SOFTWARE REQUIRED:

1. PC WITH WINDOWS XP
2. MULTISIM 10.1

CIRCUIT DIAGRAM:

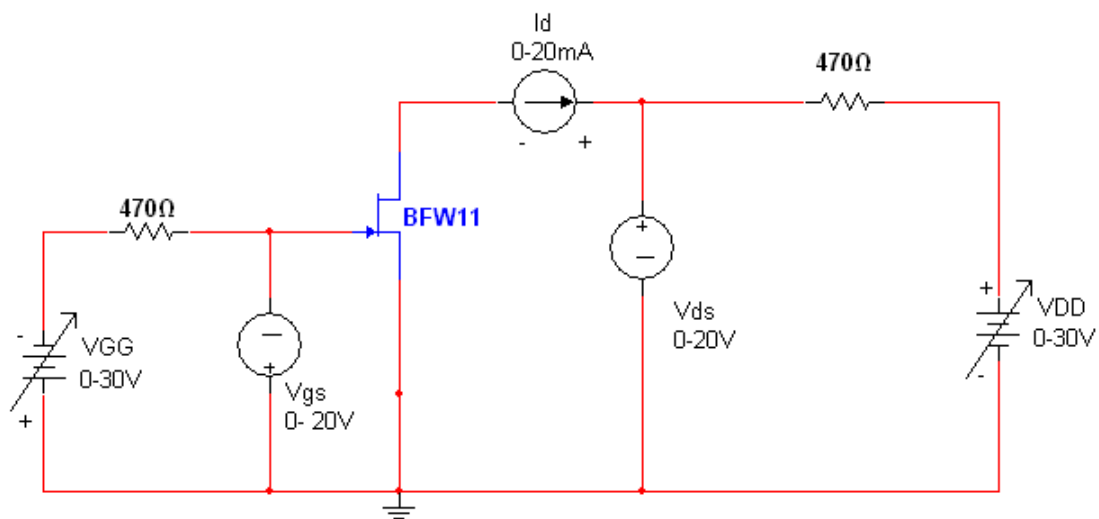

THEORY:

A FET is a three terminal device, having the characteristics of high input impedance and less noise, the Gate to Source junction of the FET is always reverse biased. In response to small applied voltage from drain to source, the n-type bar acts as sample resistor, and the drain current increases linearly with V_{DS} . With increase in I_D the ohmic voltage drop between the source and the channel region reverse biases the junction and the conducting position of the channel begins to remain constant. The V_{DS} at this instant is called “pinch of voltage”.

If the gate to source voltage (V_{GS}) is applied in the direction to provide additional reverse bias, the pinch off voltage will be decreased.

In amplifier application, the FET is always used in the region beyond the pinch-off.

$$I_{DS} = I_{DSS}(1 - V_{GS}/V_P)^2$$

PROCEDURE:**TRANSFER CHARACTERISTICS**

1. Connect the circuit as shown in figure.
2. Select **Simulate >>Analysis>>DC Sweep**.The **DC Sweep Analysis** window opens.
3. Configure the **Analysis Parametr**s with first sweep variables as V_{GG} and do not use source 2.
4. Select the output tab and make sure that **$-I(V_{DD})$ is listed under Selected variables for analysis.**
5. Click Simulate and transfer characteristics will be displayed in the **Grapher View**.

DRAIN CHARACTERISTICS

1. Connect the circuit as shown in figure
2. Select **Simulate >>Analysis>>DC Sweep**.The **DC Sweep Analysis** window opens.
3. Configure the **Analysis Parametr**s with first sweep variables as V_{DD} and second sweep variable as V_{GG} .
4. Select the output tab and make sure that **$-I(V_{DD})$ is listed under Selected variables for analysis.**
5. Click Simulate and transfer characteristics will be displayed in the **Grapher View**.

TABULAR FORM:**DRAIN CHARACTERISTICS:**


$V_{GS}=0v$		$V_{GS}=-0.5v$		$V_{GS}=-1v$	
$V_{DS}(v)$	$I_D(mA)$	$V_{DS}(v)$	$I_D(mA)$	$V_{DS}(v)$	$I_D(mA)$
0		0		0	
1		1		1	
2		2		2	
3		3		3	
4		4		4	
5		5		5	
6		6		6	
7		7		7	
8		8		8	
9		9		9	
10		10		10	

TRANSFER CHARACTERISTICS:


$V_{DS} = 1V$		$V_{DS} = 2V$		$V_{DS} = 3V$	
$V_{GS} (V)$	$I_D (mA)$	$V_{GS} (V)$	$I_D (mA)$	$V_{GS} (V)$	$I_D (mA)$
0		0		0	
0.5		0.5		0.5	
1.0		1.0		1.0	
1.5		1.5		1.5	
2.0		2.0		2.0	
2.5		2.5		2.5	
3.0		3.0		3.0	
3.5		3.5		3.5	
4.0		4.0		4.0	
4.5		4.5		4.5	
5.0		5.0		5.0	
5.5		5.5		5.5	
6.0		6.0		6.0	

GRAPH:

1. Plot the Output Characteristics by taking I_D on Y-axis and V_{DS} on X-axis for constant values of V_{GS}
2. Plot the Transfer Characteristics by taking I_D on Y-axis and V_{GS} on X-axis for constant values of V_{DS}

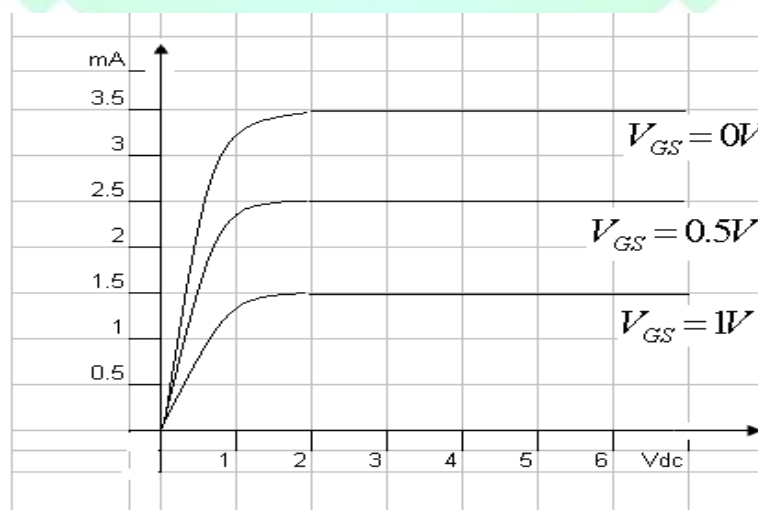DRAIN CHARACTERISTICS:

TRANSFER CHARACTERISTICS:

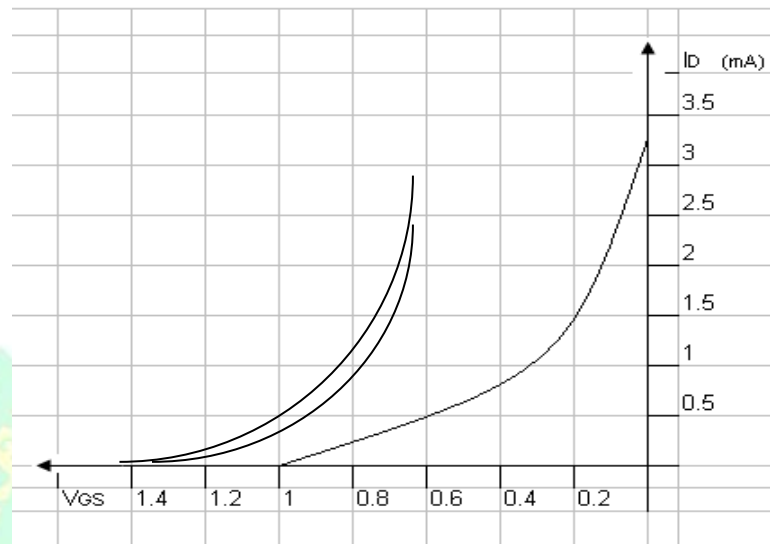

RESULT:

Output Characteristics and Transfer Characteristics of FET are plotted

QUESTIONS:

1. What are the advantages of FET?
2. Different between FET and BJT?
3. Explain different regions of V-I characteristics of FET?
4. What are the applications of FET?
5. What are the types of FET?
6. Draw the symbol of FET.
7. What are the disadvantages of FET?
8. What are the parameters of FET?


9. SCR CHARACTERISTICS

AIM: To plot the V-I characteristics of Silicon-Controlled Rectifier(SCR) using MULTISIM.

APPARATUS REQUIRED:


1. PC with Windows XP
2. MULTISIM 10.1

CIRCUIT DIAGRAM:

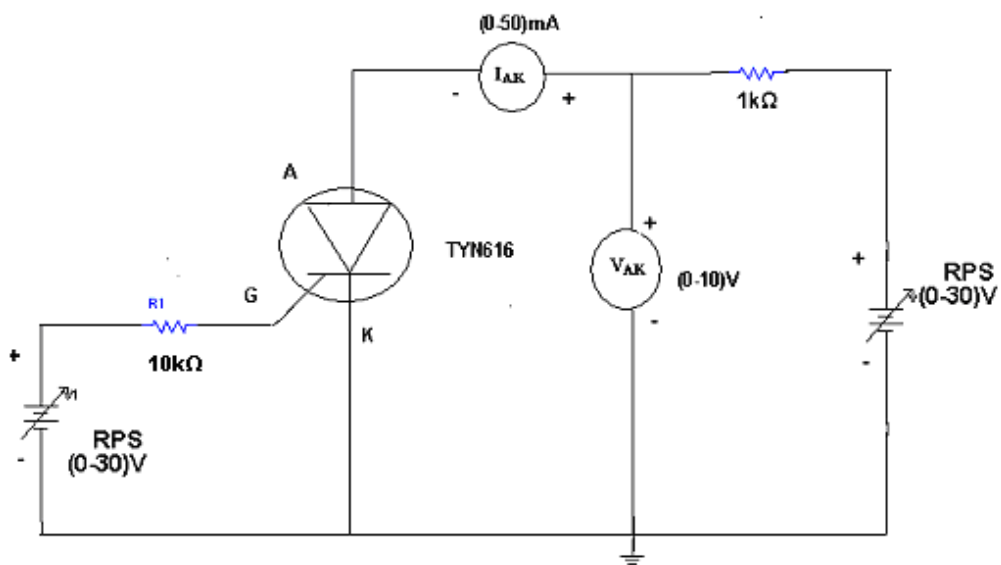

THEORY:

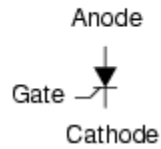It is a four layer semiconductor device being alternate of P-type and N-type silicon. It consists of 3 junctions J_1 , J_2 , J_3 the J_1 and J_3 operate in forward direction and J_2 operates in reverse direction and three terminals called anode A, cathode K, and a gate G. The operation of SCR can be studied when the gate is open and when the gate is positive with respect to cathode.



Schematic symbol

When gate is open, no voltage is applied at the gate due to reverse bias of the junction J_2 no current flows through R_2 and hence SCR is at cut off. When anode voltage is increased J_2 tends to breakdown.

When the gate positive, with respect to cathode J_3 junction is forward biased and J_2 is reverse biased. Electrons from N-type material move across junction J_3 towards gate while holes from P-type material moves across junction J_3 towards cathode. So gate current starts flowing, anode current increase is in extremely small current junction J_2 break down and SCR conducts heavily.

When gate is open the break over voltage is determined on the minimum forward voltage at which SCR conducts heavily. Now most of the supply voltage appears across the load resistance. The holding current is the maximum anode current gate being open, when break over occurs.

PROCEDURE:


1. Connect the circuit as shown in figure.
2. Select **Simulate >>Analysis>>DC Sweep**.The **DC Sweep Analysis** window opens.
3. Configure the **Analysis Parameters** with first sweep variables as V_{AK} and do not use source 2.
4. Select the output tab and make sure that **$-I(V_{AK})$ is listed under Selected variables for analysis.**
5. Click Simulate and transfer characteristics will be displayed in the **Grapher View**.

TABULAR FORM :

Firing Current

$$I_G =$$

Sl. No	V_{AK} (Volts)	I_A (mA)
1		
2		
3		
4		
5		
6		
7		
8		
9		
10		

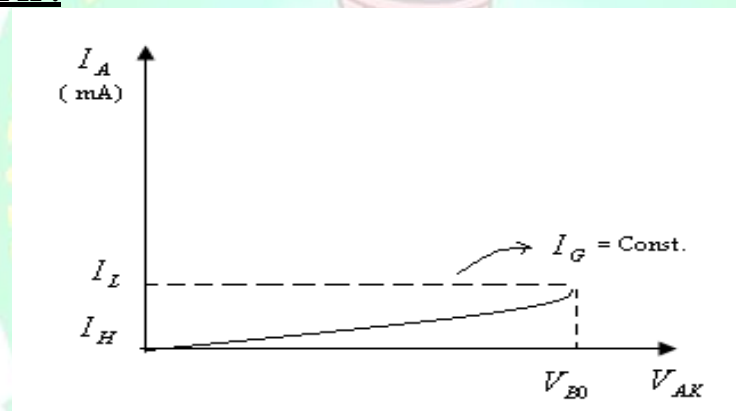
MODEL GRAPH :**RESULT:**

V-I characteristics of SCR is plotted and Values are obtained as

Parameter	Practical
Break over voltage(V_{B0})	
Latching Current (I_L)	
Holding Current (I_H)	
Maximum Current	

VIVA QUESTIONS

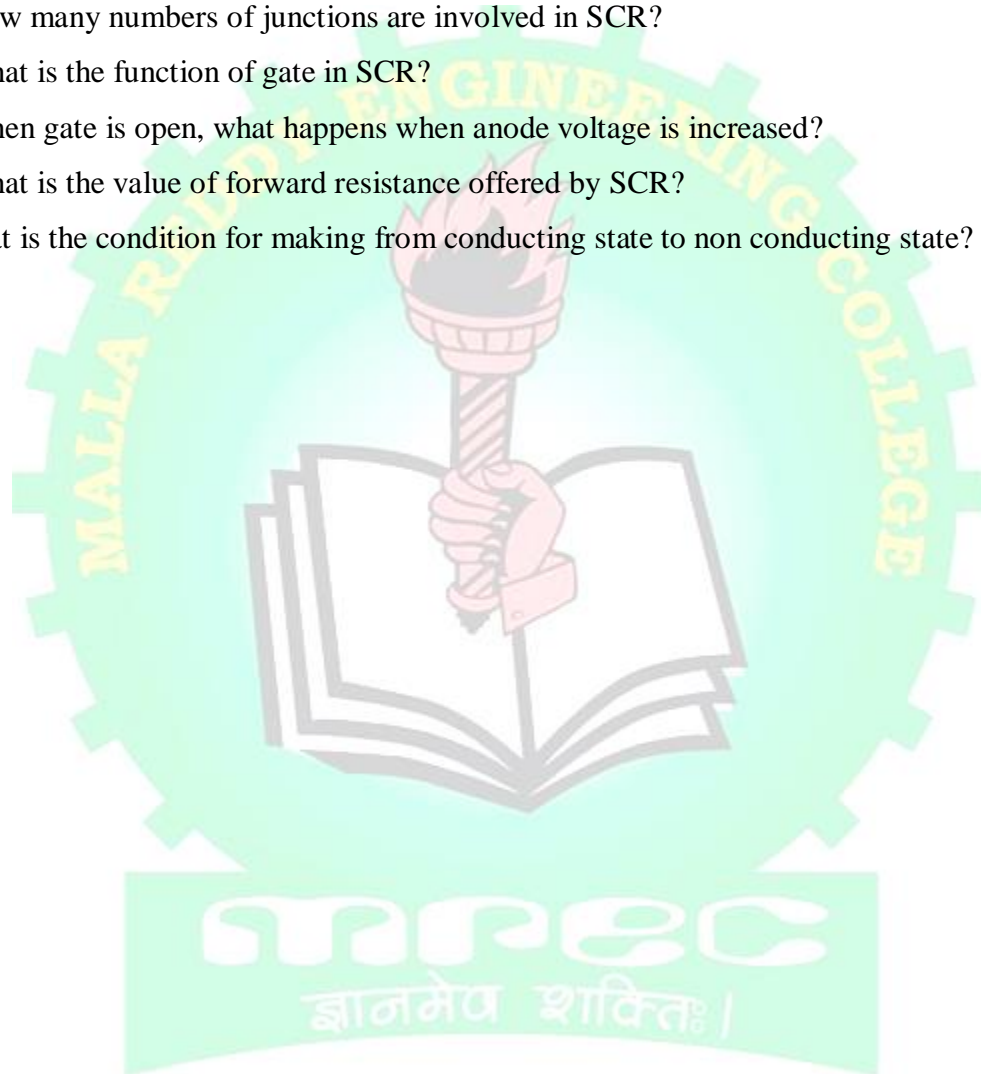1. What the symbol of SCR?
2. IN which state SCR turns of conducting state to blocking state?
3. What are the applications of SCR?
4. What is holding current?
5. What are the important type's thyristors?
6. How many numbers of junctions are involved in SCR?
7. What is the function of gate in SCR?
8. When gate is open, what happens when anode voltage is increased?
9. What is the value of forward resistance offered by SCR?
10. What is the condition for making from conducting state to non conducting state?




10. UJT CHARACTERISTICS

AIM: To plot the V-I characteristics of Unijunction Transistor (UJT) using MULTISIM.

APPARATUS:


- 1.PC with Windows XP
- 2.MULTISIM 10.1

CIRCUIT DIAGRAM:

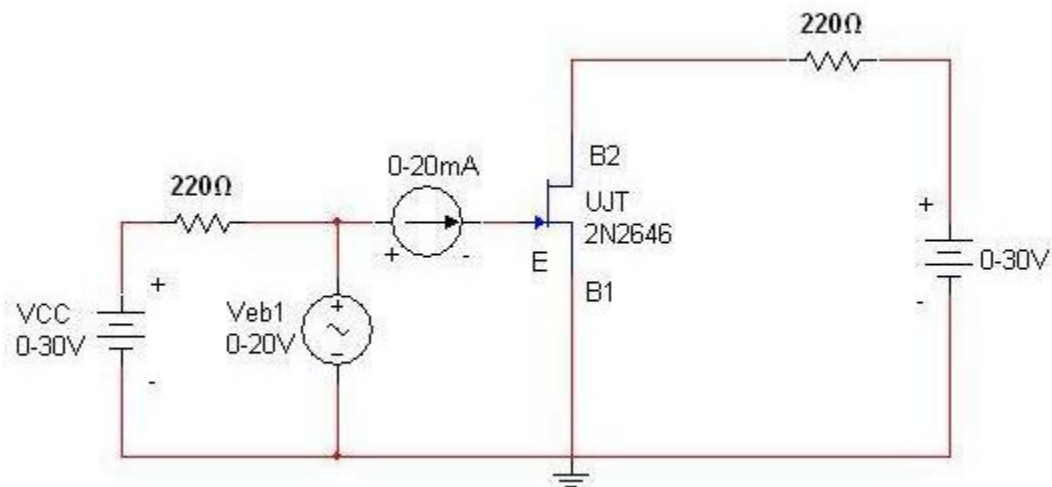

THEORY:

A Uni junction Transistor (UJT) is an electronic semiconductor device that has only one junction. The UJT Uni junction Transistor (UJT) has three terminals an emitter (E) and two bases (B1 and B2). The base is formed by lightly doped n-type bar of silicon. Two ohmic contacts B1 and B2 are attached at its ends. The emitter is of p-type and it is heavily doped. The resistance between B1 and B2, when the emitter is Open-circuit is called inter base resistance. The original uni junction transistor, or UJT, is simple device that is essentially a bar of N type semiconductor material into which P type material has been diffused somewhere along its length. The 2N2646 is the most commonly used version of the UJT.

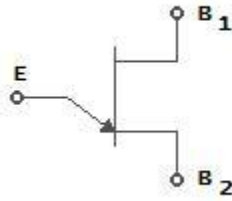


Circuit symbol

The UJT is biased with a positive voltage between the two bases. This causes a potential drop along the length of the device. When the emitter voltage is driven approximately one diode voltage above the voltage at the point where the P diffusion (emitter) is, current will begin to flow from the emitter into the base region. Because the base region is very lightly doped, the additional current (actually charges in the base region) causes (conductivity modulation) which reduces the resistance of the portion of the base between the emitter junction and the B2 terminal. This reduction in resistance means that the emitter junction is more forward biased, and so even more current is injected. Overall, the effect is a negative resistance at the emitter terminal. This is what makes the UJT useful, especially in simple oscillator circuits. When the emitter voltage reaches V_p , the current starts to increase and the emitter voltage starts to decrease. This is represented by negative slope of the characteristics which is referred to as the negative resistance region, beyond the valley point, R_{B1} reaches minimum value and this region, V_{EB} proportional to I_E .

PROCEDURE:

1. Connect the circuit as shown in figure.
2. Select **Simulate >> Analysis >> DC Sweep**. The **DC Sweep Analysis** window opens.
3. Configure the **Analysis Parameters** with first sweep variables as V_{AK} and do not use source 2.
4. Select the output tab and make sure that **V_{EB} is listed under Selected variables for analysis.**
5. Click Simulate and transfer characteristics will be displayed in the **Grapher View**.

MODEL GRAPH:

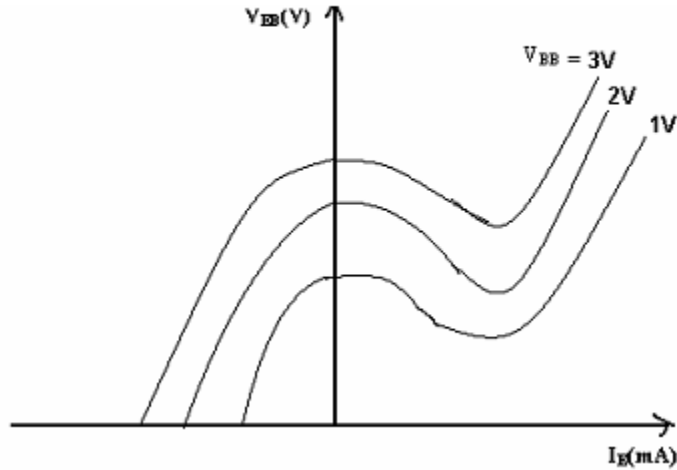

OBSERVATIONS:

$V_{BB}=1V$		$V_{BB}=2V$		$V_{BB}=3V$	
$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$

CALCULATIONS:

$$V_P = \eta V_{BB} + V_D$$


$$\eta = (V_P - V_D) / V_{BB}$$

$$\eta = (\eta_1 + \eta_2 + \eta_3) / 3$$

RESULT: The characteristics of UJT are observed and the values of Intrinsic Stand-Off ratio is calculated.

VIVA QUESTIONS

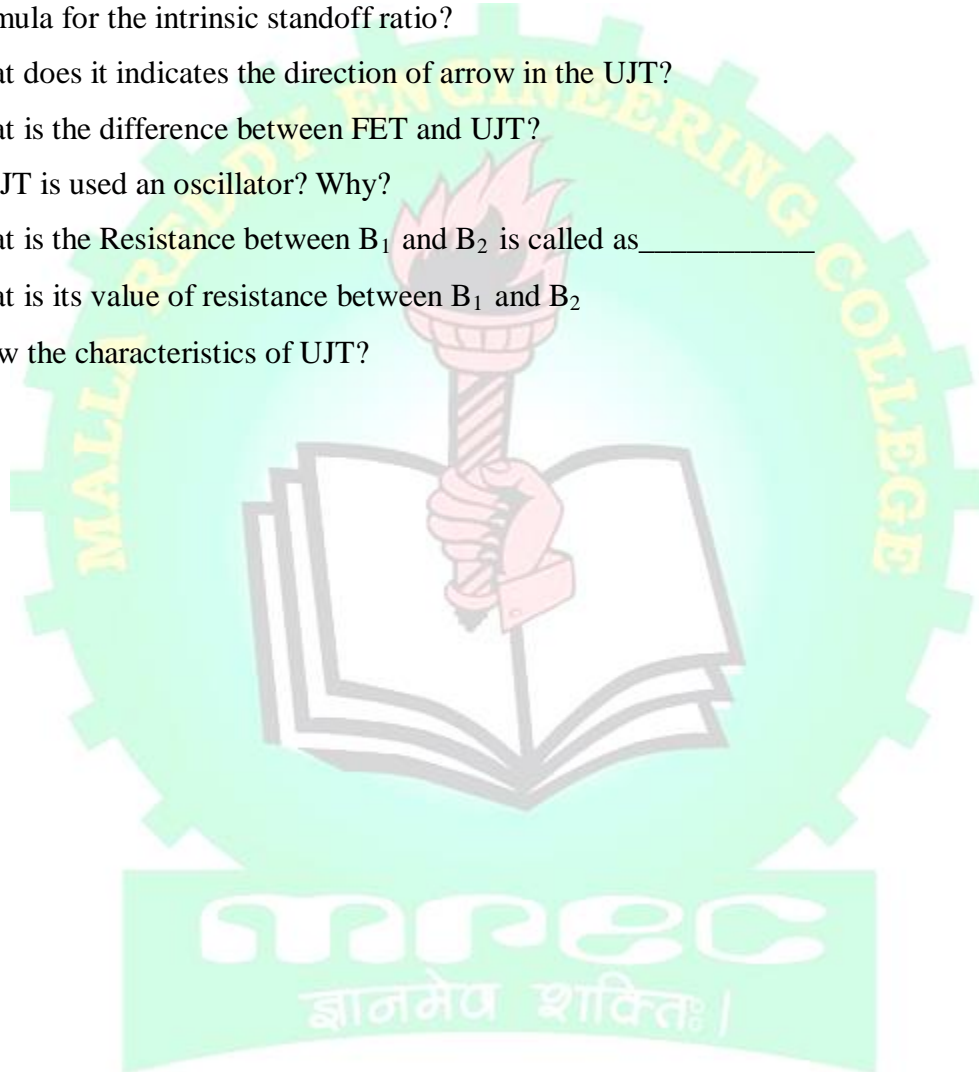1. What is the symbol of UJT?
2. Draw the equivalent circuit of UJT?
3. What are the applications of UJT?
4. Formula for the intrinsic standoff ratio?
5. What does it indicate the direction of arrow in the UJT?
6. What is the difference between FET and UJT?
7. Is UJT used as an oscillator? Why?
8. What is the Resistance between B_1 and B_2 is called as _____
9. What is its value of resistance between B_1 and B_2
10. Draw the characteristics of UJT?




11. FREQUENCY RESPONSE OF COMMON EMITTER AMPLIFIER

AIM: To measure the voltage gain and plot the frequency response of CE amplifier

APPARATUS:

1. Transistor BC 107-1 1 no
2. Capacitor 10 μ f / 25v 2 no's
3. Resistors 1K Ω , 3.3K Ω , 4.7K Ω , 470 Ω , 33K Ω – each 1no.
4. Function Generator
5. Dual trace oscilloscope
6. Bread board trainer
7. D.C power supply 0-30V

CIRCUIT DIAGRAM:

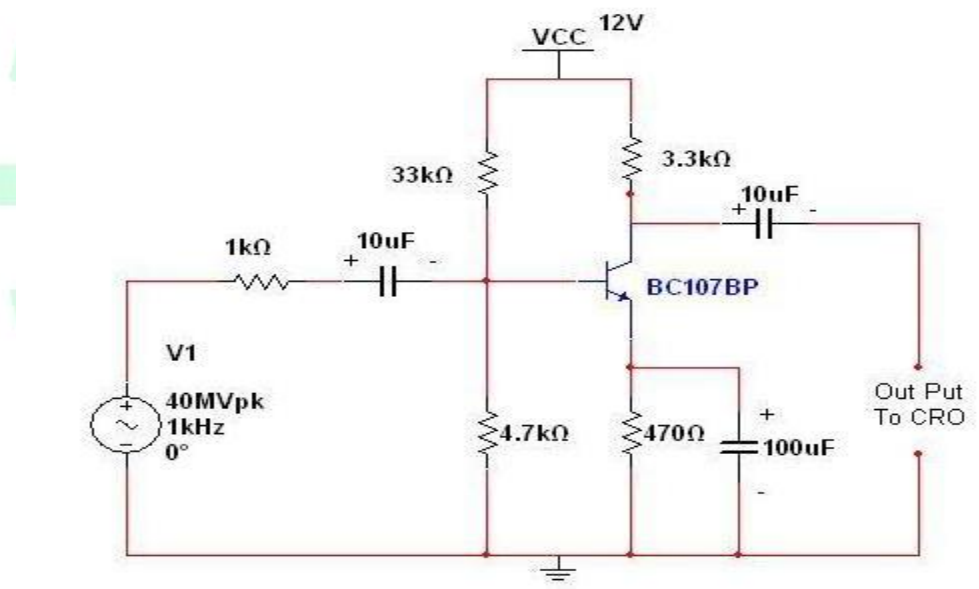

THEORY:

The CE amplifier provides high gain & wide frequency response. The emitter lead is common to both input & output circuits and is grounded. The emitter-base circuit is forward biased. The collector current is controlled by the base current rather than emitter current. The input signal is applied to base terminal of the transistor and amplifier output is taken across collector terminal. A very small change in base current produces a much larger change in collector current. When +VE half-cycle is fed to the input circuit, it opposes the forward bias of the circuit which causes the collector current to decrease, it decreases the voltage more -VE. Thus when input cycle varies through a -VE half-cycle, increases the forward bias of the circuit, which causes the collector current to increase thus the output signal is common emitter amplifier is in out of phase with the input signal.




PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Make the Connection of signal generator output to input terminals of the circuit and channel –1 of dual trace CRO
3. Make the Connection of output terminal of the circuit to channel – 2 of the dual trace CRO
4. Set the signal generator output at 10mv constant to the circuit
5. Set the signal generator output at 10mv constant, sine wave at 100 Hz
6. Vary the signal generator frequency from 100 Hz to 500 kHz as per the table given and note the corresponding output voltage
7. Calculate the gain $A_v = V_o/V_i$

TABULAR FORM:

Input Voltage= 40 mV

S.NO	INPUT FREQUENCY (HZ)	OUTPUT VOLTAGE (Vo)	GAIN $A_v = V_o/V_i$	GAIN in db $20 \log (A_v)$
1	100			
2	200			
3	300			
4	400			
5	500			
6	600			
7	700			
8	800			
9	900			
10	1K			
11	2K			
12	3K			
13	4K			
14	5K			
15	6K			
16	7K			
17	8K			
18	9K			
19	10K			
20	20K			
21	30K			
22	40K			
23	50K			
24	100K			
25	200K			
26	300K			
27	400K			
28	500K			

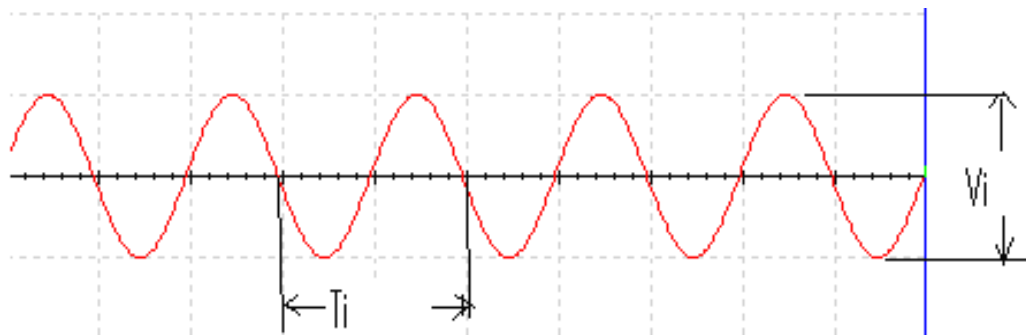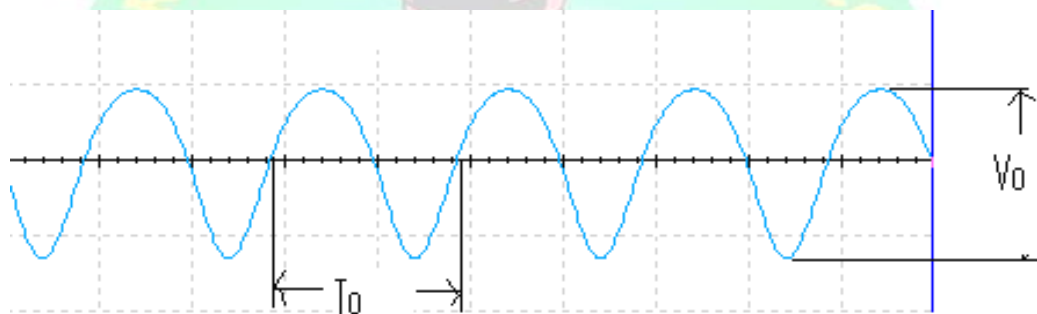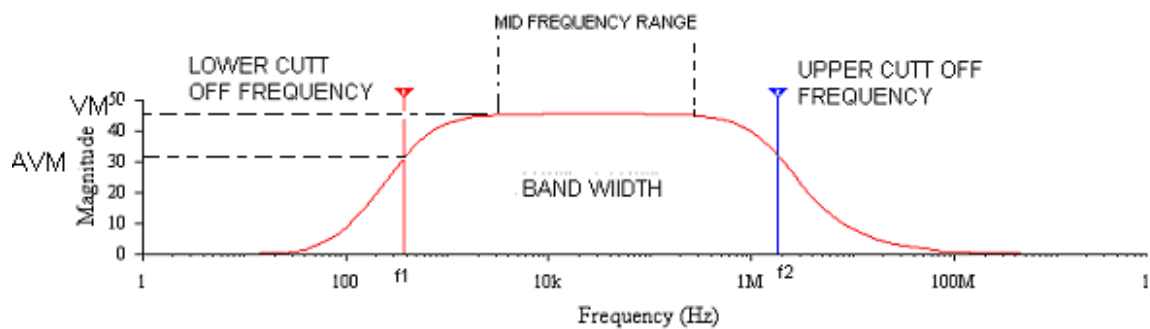INPUT WAVE FORM:**OUTPUT WAVE FORM****FREQUENCY RESPONSE****GRAPH:**

Plot the graph frequency verses gain (db) on a semi log sheet

RESULT:

Verified the voltage gain and frequency response of CE amplifier.

QUESTIONS:

1. What is phase difference between input and output waveforms of CE amplifier?
2. What type of biasing is used in the given circuit?
3. If the given transistor is replaced by a p-n-p, can we get output or not?
4. What is effect of emitter-bypass capacitor on frequency response?
5. What is the effect of coupling capacitor?
6. What is region of the transistor so that it is operated as an amplifier?
7. How does transistor acts as an amplifier?
8. Draw the h-parameter model of CE amplifier?
9. What type of transistor configuration is used in intermediate stages of a multistage amplifier?
10. What is Early effect?

