

MALLA REDDY ENGINEERING COLLEGE (AUTONOMOUS)


(Affiliated to JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD)
Gundlapochampally (H), Maisammaguda (V), Medchal (M), Medchal-Malkajgiri (Dist), Hyderabad

III B.TECH I SEMESTER SUPPLEMENTARY EXAMINATIONS, MAY-2019Subject: Integrated Circuits & ApplicationsBranch: **EEE****Time: 3 hours****Max. Marks: 75**Answer any **FIVE** Questions of the following**5x15 Marks= 75 Marks**

1. a) Explain about CMRR and SVRR of an op-amp.
b) What are the features of IC 741? [5M]
2. a) Draw the circuit diagram for Schmitt trigger and explain its working with waveforms. [5M]
b) Explain the characteristics of comparator and how they are used in limiter circuits with neat circuit diagram and waveforms. [7M]
c) Design op-amp differentiator for I/P signal $f_{max}=100$ Hz, (square wave) amplitude of IV peak to peak. Draw the O/P wave forms. [3M]
3. a) Explain the Wein bridge oscillator circuit using OP-AMP. [8]
b) Design a wide band pass filter with $f_l=200$ Hz, $f_h=1$ KHz and a pass band gain is 4. Calculate the 'Q' factor for a filter. [7]
4. a) Draw the Block schematic of PLL and explain about each block separately. [8M]
b) If $R_A=6.8$ K Ω , $R_B=3.3$ K Ω , $C=0.1$ μ F values of 555 IC A stable Multivibrator. Calculate i) t_{high} ii) t_{low} iii) free Running frequency (f_o) iv) duty cycle. [7M]
5. a) Explain successive approximation type ADC with neat sketches
b) Explain about the specifications of DAC.
6. a) Explain the characteristics & parameters of 74TTL IC's & compare the parameters with respect to TTL, ECL & CMOS. [8]
b) Explain about CMOS NAND and CMOS Tristate Inverter. [7]
7. a) List out the different 74 IC numbers for Data selectors. Explain about IC 74157 with one application. [8]
b) Draw the Pin diagram, Logic diagram & Truth table for 1C74138 & Design 4 to 16 Decoder by using 74138. [7]
8. a) Convert a T-flip flop into a D-flip flop and explain its operation. 8M
b) Convert a D-flip flop into a T-flip flop and explain its operation. 7M

MALLA REDDY ENGINEERING COLLEGE (AUTONOMOUS)(Affiliated to JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD)
Gundlapochampally (H), Maisammaguda (V), Medchal (M), Medchal-Malkajgiri (Dist), Hyderabad**III B.TECH I SEMESTER SUPPLEMENTARY EXAMINATIONS, MAY - 2019**Subject: Control SystemsBranch: **Common to EEE & ECE****Time: 3 hours****Max. Marks: 75**Answer any **FIVE** Questions of the following**5x15 Marks= 75 Marks**

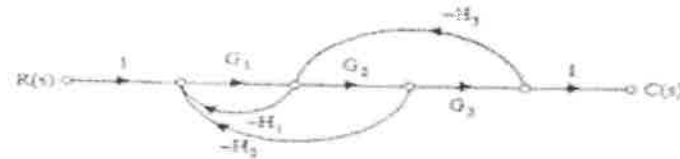1. a) Define Transfer function and write its limitations? [7M]
b) What is closed loop control systems and explain the characteristics of feedback? [8M]
2. a) Explain the rules in Block diagram reduction technique. [8M]
b) Obtain the transfer function for the following signal flow graph [7M]



3. Evaluate static error constants for unity feedback system having a forward path T.F $G(s) = \frac{50}{s(s+10)}$.
Estimate steady state errors for input given by $r(t) = 1 + 2t + t^2$.
4. A unity feedback control system is characterized by $G(s) = \frac{K}{s^2(s+2)}$
 - a. Show that the system is always unstable
 - b. Show that the system is always stable if a zero $(s+a)$ is added to above T.F where $0 < a < 2$.
5. a) What is frequency response analysis
b) Determine phase margin and gain margin using bode plot for T.F of

$$G(s) = \frac{40(s+1)}{(s^2+2s+4)(1+5s)}$$
6. Using Nyquist stability criterion, find range of 'K' for closed loops system stability for

$$G(s)H(s) = \frac{K(4s+1)}{s(s-1)}, K > 0$$
7. a) What is compensation
b) Explain different types of compensation networks clearly.
8. a) What is diagonalisation
b) Obtain the state transition matrix $\phi(t)$ for the following system

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$