

**MALLA REDDY ENGINEERING COLLEGE**  
**(Autonomous)**

**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**LAB MANUAL**  
**AC MACHINES LAB**

**Prepared by**  
**Mr. P.GANESH**  
**Assistant Professor**

**Approved by**  
**Dr.N.Rajeswaran**  
**Prof. & HOD/EEE**



**CLASS : III YEAR EEE**

**SEMESTER : I SEM**

**SUBJECT CODE : 80216**

**REGULATION : MR18**


**SUBJECT : AC Machines Lab**

## **SYLLABUS**

1. OC & SC Tests on Single phase Transformer.
2. Sumpner's test on a pair of single phase transformers.
3. Scott connection of transformers.
4. No-load & Blocked rotor tests on three phase Induction motor.
5. Regulation of a three –phase alternator by synchronous impedance & m.m.f. methods.
6. V and Inverted V curves of a three-phase synchronous motor.
7. Equivalent Circuit of a single phase induction motor.
8. Determination of  $X_d$  and  $X_q$  of a salient pole synchronous machine.
9. Parallel operation of Single phase Transformers.
10. Brake test on three phase Induction Motor.
11. Regulation of three-phase alternator by Z.P.F. and A.S.A methods.
12. Load test of a three-phase alternator.

**EXPERIMENT-1**  
**OC & SC TESTS ON SINGLE PHASE**  
**TRANSFORMER**

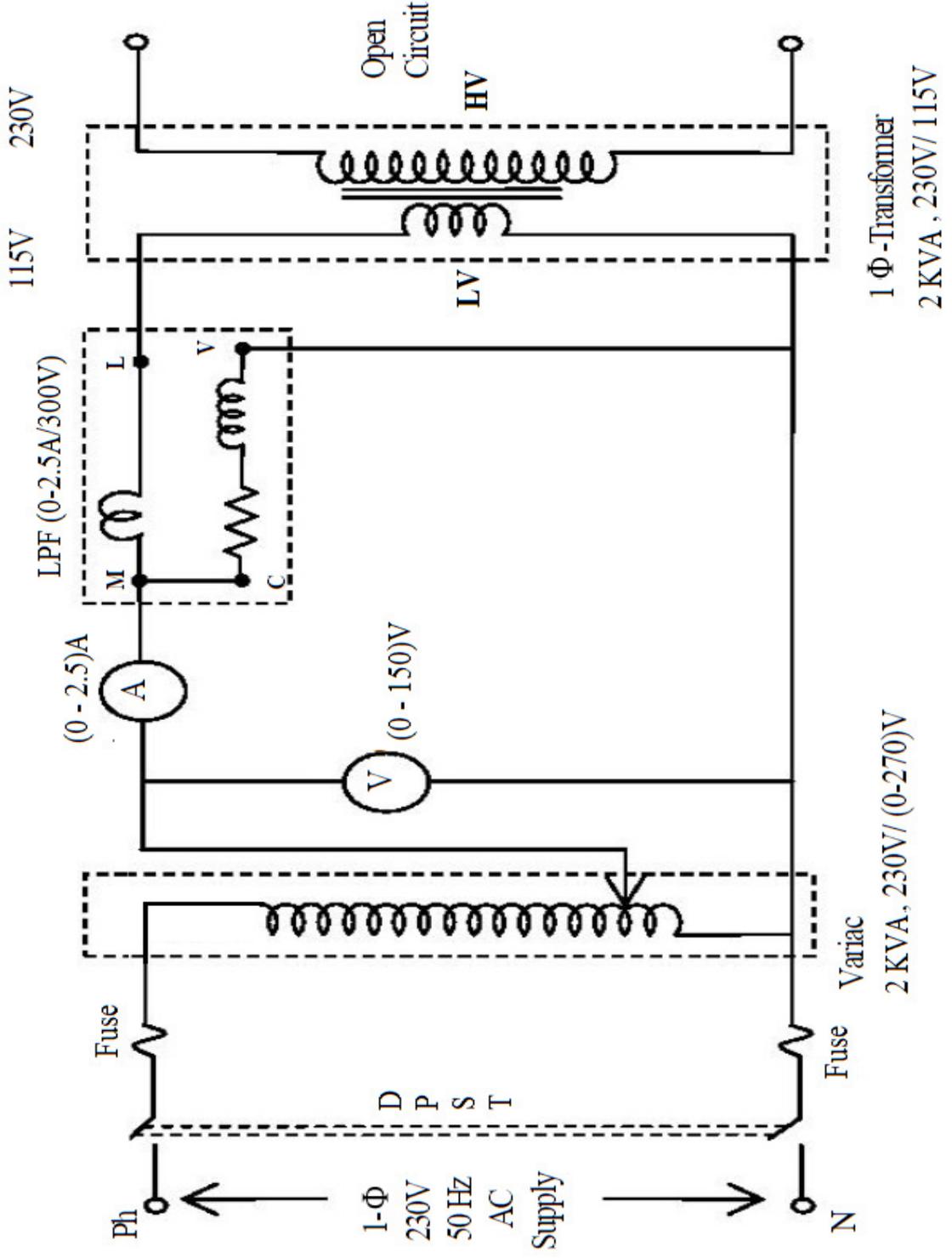**CIRCUIT DIAGRAM FOR OPEN CIRCUIT TEST ON 1-PHASE**



T/F:

## O.C & S.C TESTS ON SINGLE PHASE TRANSFORMER

**AIM:** a) To predetermine the efficiency and regulation of Single Phase Transformer by conducting no-load test and short circuit test.

b) To draw the equivalent circuit of single phase transformer referred to LV side as well as HV side.


### APPARATUS:

S.NO.	NAME OF THE EQUIPMENT	TYPE	RANGE	QUANTITY
1.	Single phase Variac		2KVA,0-270V	1
2.	Ammeter	MI	0-2.5A and 0-10A	1,1
3.	Voltmeter	MI	0-300 V, 0-30V	1,1
4.	Wattmeter	Dynamometer	(0-2.5A/300V) LPF	1
5.	Wattmeter	Dynamometer	(0-10A/300V) UPF	1

### NAME PLATE DETAILS:

S.No.	1- $\Phi$ TRANSFORMER	
	PARAMETER	RATING
1	Capacity	
2	I/P voltage	
3	I/P Current	
4	O/P Voltage	
5	O/P Current	
6	Frequency	
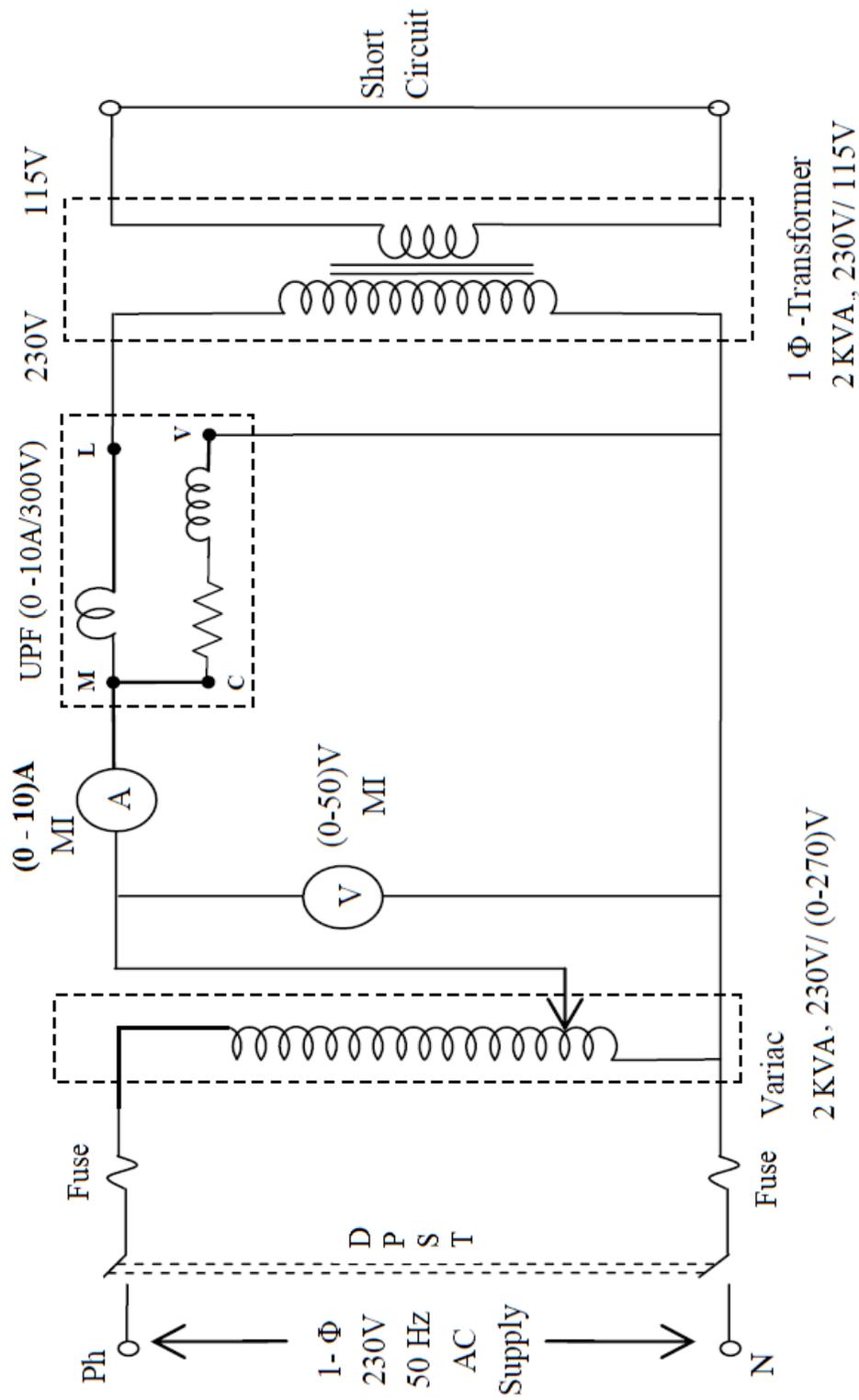
# CIRCUIT DIAGRAM FOR SHORT CIRCUIT TEST ON 1-PHASE T/F:



**PROCEDURE:**

- (1) Connect the circuit for no-load test as per the circuit diagram. Shown in fig(1).
- (2) Keep the variac in minimum output position and switch on the supply.
- (3) Apply the rated voltage to the transformer by properly adjusting the variac.
- (4) Note down the readings of various meters and switch off the supply.
- (5) Connect the circuit for SC test as per the circuit diagram, shown in fig (2) with appropriate ranges of meters.
- (6) Keep the variac in minimum output position and switch on the supply.
- (7) Apply proper voltage (low voltage) to the transformer by adjusting the variac such that rated current flows through the transformer.
- (8) Note down the readings of various meters and switch off the supply.

**PRECAUTIONS:**

- (i) Connections must be made tight
- (ii) Before making or breaking the circuit, supply must be switched off.

**OBSERVATIONS:****O.C TEST**



S.NO.	$V_o$ (V)	$I_o$ (A)	$W_o$ (W)

**S. C TEST:**

S.NO.	$V_{sc}$ (V)	$I_{sc}$ (A)	$W_{sc}$ (W)

**MODEL GRAPHS: PLOTS DRAWN BETWEEN**

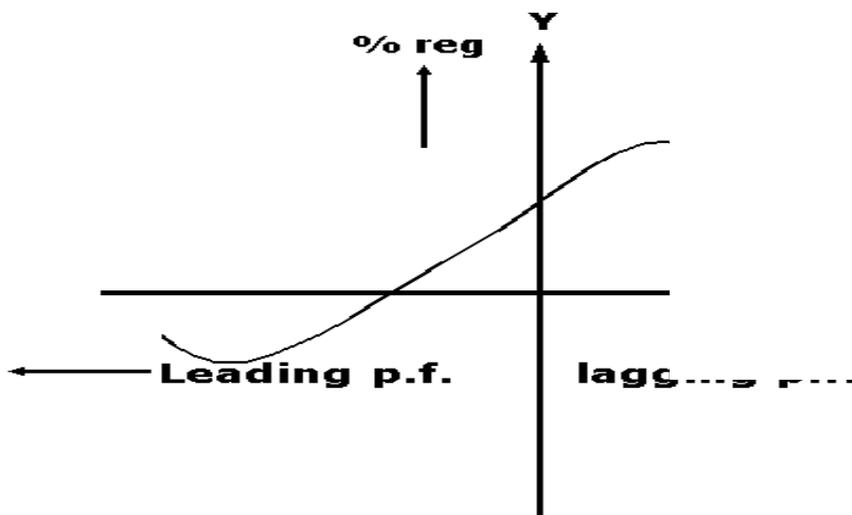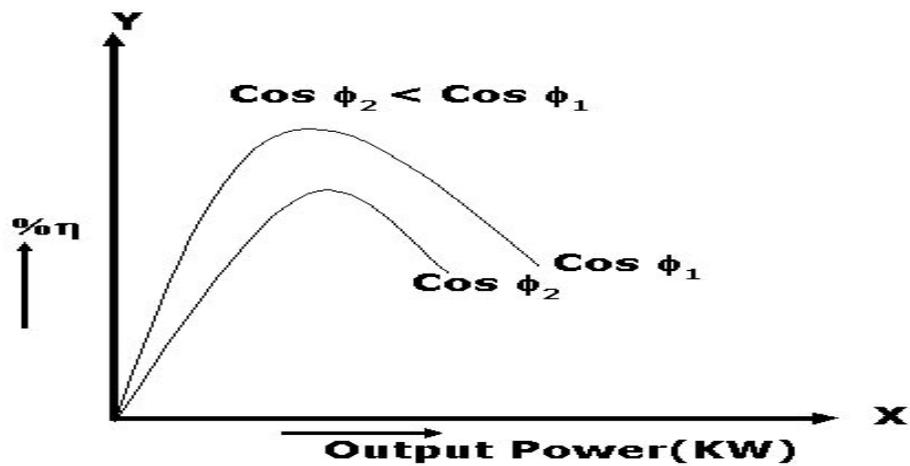- (i) % Efficiency Vs Output
- (ii) % Regulation Vs Power Factor



**MODEL CALCULATIONS:**

Find the equivalent circuit parameters  $R_0, X_0, R_{01}, R_{02}, X_{01}$  and  $X_{02}$  from the O. C. and S. C. test results and draw the equivalent circuit referred to L. V. side as well as H. V. side.

Let the transformer be the step-down transformer  
 Primary is H. V. side.

Secondary is L. V. side

$$\cos \phi_0 = \frac{W_0}{V_0 I_0} =$$

$$\sin \phi_0 =$$

$$R_0 = \frac{V_0}{I_w} =$$

$$\text{Where } I_w = I_0 \cos \phi_0$$

$$X_0 = \frac{V_0}{I_m} =$$

$$\text{Where } I_m = I_0 \sin \phi_0$$

$$R_{02} = \frac{W_{sc}}{I_{sc}^2} =$$

$$Z_{02} = \frac{V_{sc}}{I_{sc}}$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} =$$

$$X_{01} = K^2 X_{02} =$$

$$\text{Where } K = \frac{V_2}{V_1} = 1 \text{ Transformation ratio.}$$

$$R_{01} = K^2 R_{02} =$$

## CALCULATIONS OF EFFICIENCY AND REGULATION

For example at  $\frac{1}{2}$  full load

Copper losses =  $W_{sc} \times (1/2)^2$  watts, where  $W_{sc}$  = full – load copper losses

Constant losses =  $W_i$  watts

Output =  $\frac{1}{2}$  KVA  $\times \cos \phi$  [ $\cos \phi$  may be assumed]

Input = output + Cu. Loss + constant loss

$$\% \text{ efficiency} = \frac{\text{Output}}{\text{Input}} \times 100$$

$$\text{Efficiency at any load} = \frac{S \times \cos \phi}{S \times \cos \phi + W_i + W_{sc}} \times 100$$

### Regulation:

#### From open circuit

$$\% \text{ Regulation} = \frac{I_1 R_{01} \cos \phi \pm I_1 X_{01} \sin \phi}{V_1} \times 100$$

‘+’ for lagging power factors


‘-’ for leading power factors

#### FOR S.C. TEST:

Regulation: From Short circuit test

$$\% \text{ Regulation} = \frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \times 100$$

### EQUIVALENT CIRCUIT:

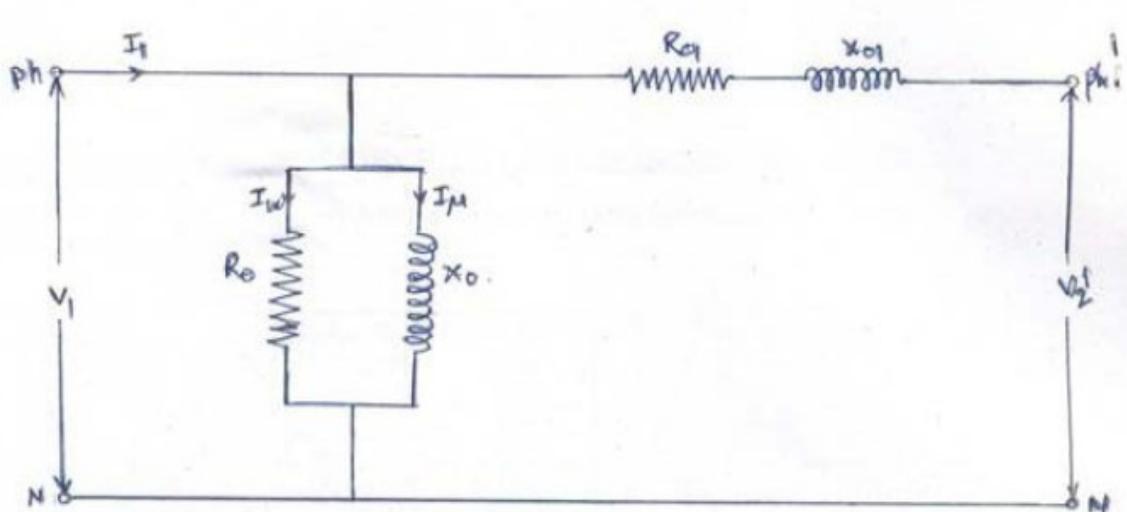


## TABULAR FORM

S.No.	Load	Cu.loss (W)	Output (W)	Input (W)	% $\eta$		S.N.	Load	Cu.loss (W)	Output (W)	Input (W)	% $\eta$
1.	1/4F.L.							1/4F.L.				
2.	1/2F.L.							1/2F.L.				
3.	3/4F.L.							3/4F.L.				
4.	F.L.							F.L.				

Lagging Pf			Leading Pf		
S.N.	P.F.	% Reg.	S. N.	P. F.	% Reg.
1.	0.3		1.	0.	
2.	0.4		2.	0.4	
3.	0.5		3.	0.5	
4.	0.6		4.	0.6	
5.	0.7		5.	0.7	
6.	0.8		6.	0.8	
7.	Unity		7.	Unity	

**REGULATION MODEL GRAPH:**

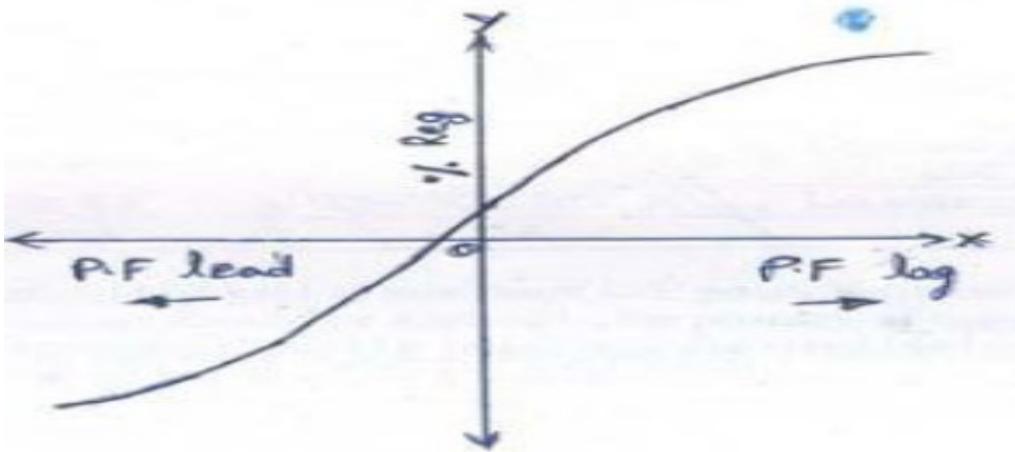


**RESULT:**

## **EXPERIMENT-2**
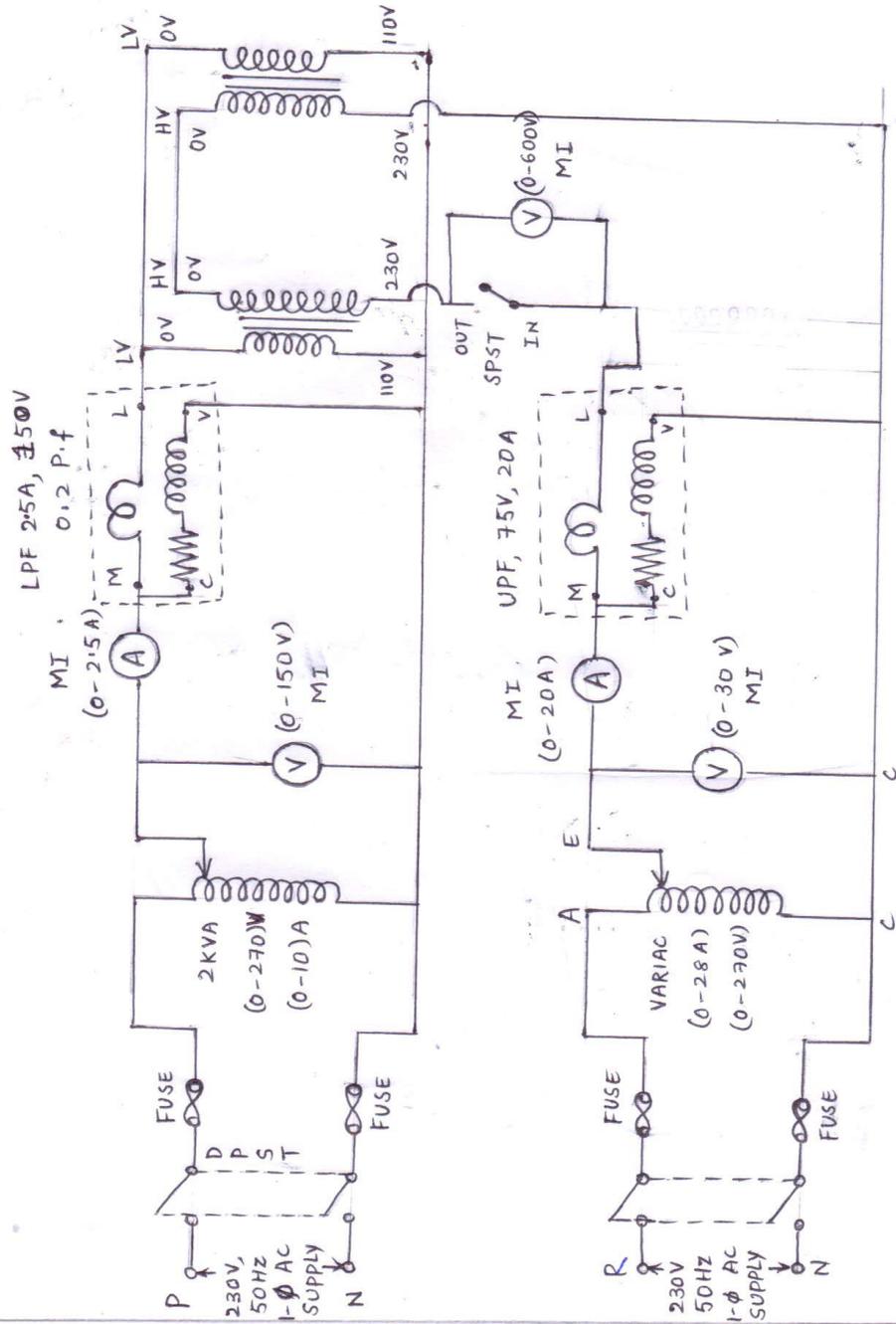
# **SUMPNER'S TEST ON A PAIR OF SINGLE PHASE TRANSFORMERS**

CIRCUIT DIAGRAM FOR SUMPNER'S TEST ON 1- $\phi$  TRANSFORMER



## SUMPNER'S TEST ON 1-PHASE TRANSFORMER

**AIM:** (i) To conduct sumpner's test on two identical single phase transformers.

(ii) To find out the iron loss, copper loss and the efficiency of each transformer.

### NAME PLATE DETAILS:

1-PHASE TRANSFORMER		
S.No.	NAME	RATING
1	Power	
2	Voltage	
3	Frequency	
4	Taps On H.V	

### APPARATUS REQUIRED:

S.No.	NAME	TYPE	RANGE	QUANTITY
1	Voltmeter	MI	(0-30)V	1
			(0-300)V	1
2	Ammeter	MI	(0-2.5)A	1
			(0-20)A	1
3	Variac	-	(0-20)A	1
4	Wattmeter	Dynamometer type	300V,5A,LPF	1
			75V,10A,UPF	1

**PROCEDURE:****OC TEST:**

1. Connect the circuit as per the circuit diagram.
2. Set the autotransformer at low voltage position.
3. Switch on the low voltage side auto transformer.
4. Apply rated voltage by adjusting the auto transformer.
5. Note the values of applied voltage, current and power readings is given by wattmeter.
6. The readings of wattmeter will give the iron losses.

**SC TEST:**

1. Close the DPST switch
2. Switch ON the supply 1-phase,50hz,230v on secondary side of the transformer
3. By slowly varying the 1-phase auto t/f till the rated current is reached
4. Now take the voltage voltmeter(v1&v2),ammeter(A1&A2),W1&W2 respectively
5. Switch OFF the supply

**PRECAUTIONS:**

- (iii) Connections must be made tight
- (iv) Before making or breaking the circuit, supply must be switched off.

**OBSERVATIONS:****O.C TEST**



S.NO.	$V_o$ (V)	$I_o$ (A)	$W_o$ (W)

**S. C TEST:**

S.NO.	$V_{sc}$ (V)	$I_{sc}$ (A)	$W_{sc}$ (W)

## MODEL GRAPHS: PLOTS DRAWN BETWEEN

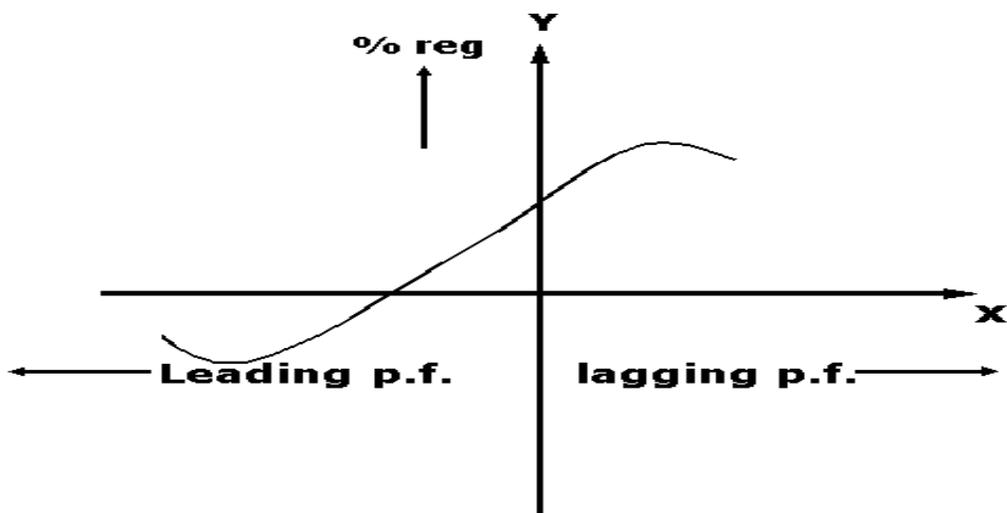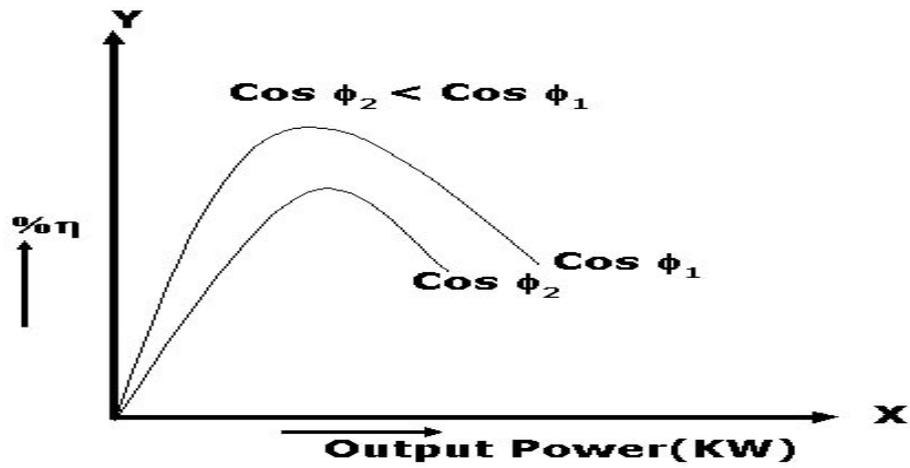- (iii) % Efficiency Vs Output
- (iv) % Regulation Vs Power Factor



## MODEL CALCULATIONS:

Find the equivalent circuit parameters  $R_0$ ,  $X_0$ ,  $R_{01}$ ,  $R_{02}$ ,  $X_{01}$  and  $X_{02}$  from the O. C. and S. C. test results and draw the equivalent circuit referred to L. V. side as well as H. V. side.

Let the transformer be the step-down transformer

Primary is H. V. side.

Secondary is L. V. side

$$\cos \phi_0 = \frac{W_0}{V_0 I_0} =$$

$$\sin \phi_0 =$$

$$R_0 = \frac{V_0}{I_w} =$$

$$\text{Where } I_w = I_0 \cos \phi_0$$

$$X_0 = \frac{V_0}{I_m} =$$

$$\text{Where } I_m = I_0 \sin \phi_0$$

$$R_{02} = \frac{W_{SC}}{I_{sc}^2} =$$

$$Z_{02} = \frac{V_{SC}}{I_{SC}}$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} =$$

$$X_{01} = K^2 X_{02} =$$

$$\text{Where } K = \frac{V_2}{V_1} = 1 \text{ Transformation ratio.}$$

$$R_{01} = K^2 R_{02} =$$

## CALCULATIONS OF EFFICIENCY AND REGULATION

For example at  $\frac{1}{2}$  full load

Copper losses =  $W_{sc} \times (1/2)^2$  watts, where  $W_{sc}$  = full – load copper losses

Constant losses =  $W_i$  watts

Output =  $\frac{1}{2}$  KVA  $\times \cos \phi$  [ $\cos \phi$  may be assumed]

Input = output + Cu. Loss + constant loss

$$\% \text{ efficiency} = \frac{\text{Output}}{\text{Input}} \times 100$$

$$\text{Efficiency at any load} = \frac{S \times \mathcal{K} \times \cos \phi}{S \times \mathcal{K} \times \cos \phi + W_i + W_{sc} \mathcal{K}^2} \times 100$$

### Regulation:

#### From open circuit

$$\% \text{ Regulation} = \frac{I_1 R_{01} \cos \phi \pm I_1 X_{01} \sin \phi}{V_1} \times 100$$

‘+’ for lagging power factors


‘-’ for leading power factors

#### FOR S.C. TEST:


Regulation: From Short circuit test

$$\% \text{ Regulation} = \frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \times 100$$

### EQUIVALENT CIRCUIT:

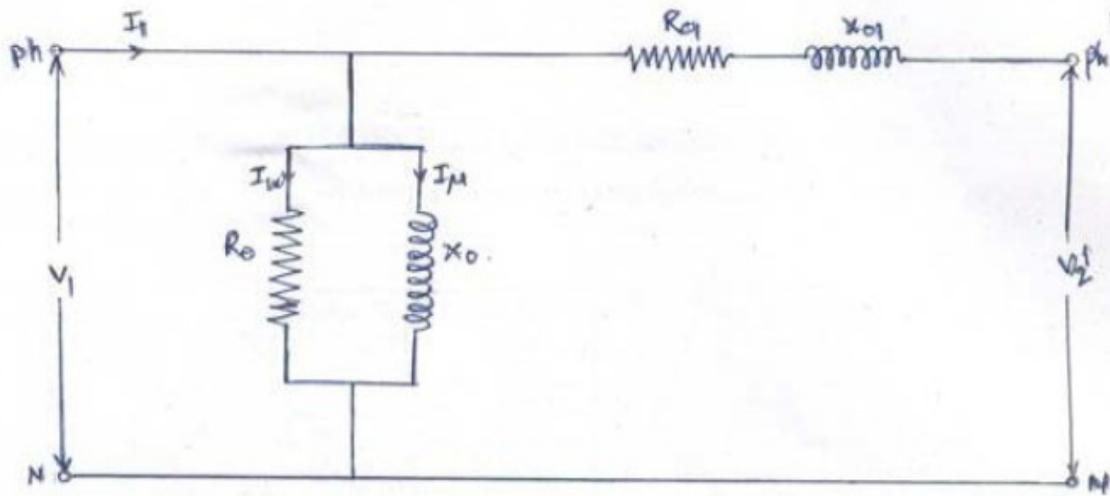

### REGULATION MODEL GRAPH:

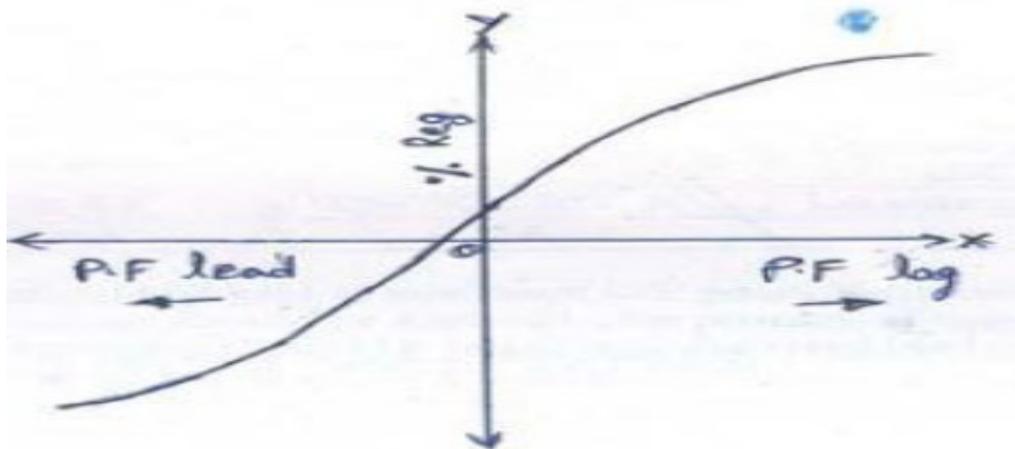

### TABULAR FORM

S.No.	Load	Cu.loss (W)	Output (W)	Input (W)	% $\eta$		S.N.	Load	Cu.loss (W)	Output (W)	Input (W)	% $\eta$
1.	1/4F.L.							1/4F.L.				
2.	1/2F.L.							1/2F.L.				
3.	3/4F.L.							3/4F.L.				
4.	F.L.							F.L.				


Lagging Pf			Leading Pf		
S.N.	P.F.	% Reg.	S. N.	P. F.	% Reg.
1.	0.3		1.	0.	
2.	0.4		2.	0.4	
3.	0.5		3.	0.5	
4.	0.6		4.	0.6	
5.	0.7		5.	0.7	
6.	0.8		6.	0.8	
7.	Unity		7.	Unity	

**RESULT:**

## **EXPERIMENT-3**
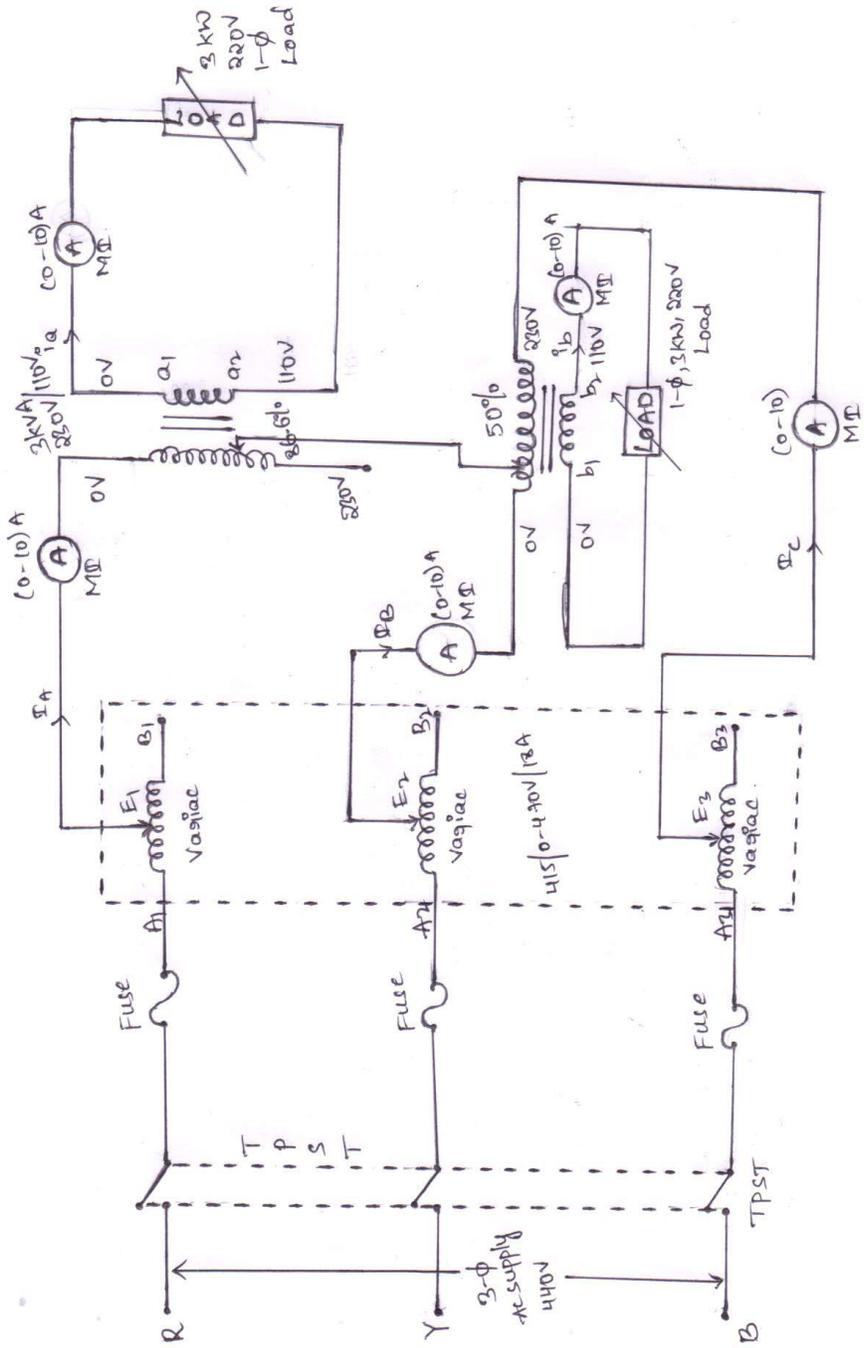
# **SCOTT CONNECTION OF TRANSFORMERS**

Circuit diagram for Scott connection of Transformers:



## SCOTT CONNECTION OF TRANSFORMERS

**AIM:** To verify the conversion of 3-phase to 2 1-phase of 90 degrees apart supplies and also verify the primary current from the 1-phase side.

### NAME PLATE DETAILS:


SCOTT TRANSFORMERS	
Transformer rating	
Rated Voltage	
Taps on HV	

### APPARATUS REQUIRED:


Sl. No.	Name of the Equipment	Range	Type	Quantity
1	Transformer	-	1-phase ,50%86.6%	2
2	Variac	(0-470)V	3-phase	1
3	Transformer	230/110V	1-phase	1
4	Ammeter	(0-10)A		5
5	VOLtmeter			


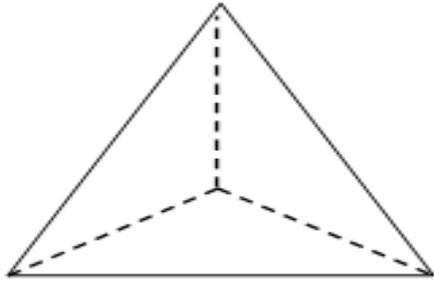
## MODEL PHASOR DIAGRAMS FOR SCOTT CONNECTION:



Primary Voltage

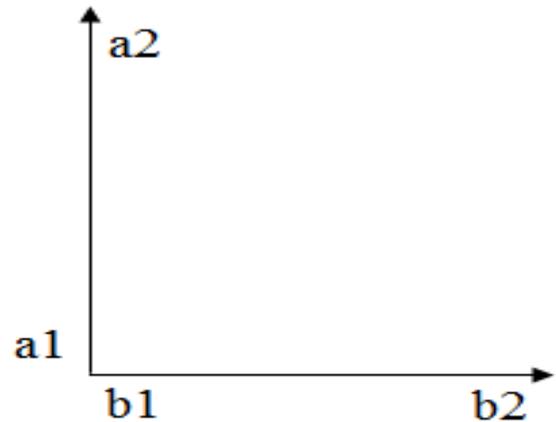

Secondary Voltage

## PROCEDURE:

1. Give all connections as per the circuit diagram.
2. Ensure the 3-phase variac and switch ON main supply
3. Increase the variac voltage or output voltage to 200V line to line.
4. Measure the 1-phase voltage on L.V side.
5. By shorting  $a_1, b_1$  to be shorted, measure the voltage across  $a_2, b_2$  and verify the scott connection tapping.
6. Reduce the variac voltage to zero and connect the loads to each 1-phase as shown in figure.
7. Apply rated voltage in each winding through 3-phase variac to 3-phase side.
8. Note down the voltage and currents on 3-phase side and 1-phase side.
9. Vary the values of V & I at each step.
10. Take around a half of a dozen readings.
11. Verify the 3-phase and measure the values of voltage and currents and represent in tabular column.
12. Draw the vector diagram for any particular load.


**PRECAUTIONS:**

- 1) The Dimmerstat should be kept at minimum O/P position initially.
- 2) The Dimmerstat should be varied slowly & uniformly.
- 3) Rated voltage should be applied to the primary of the Transformer.


**RESULT:**

**EXPERIMENT NO 4**  
**NO-LOAD AND BLOCKED ROTOR TEST ON 3-PHASE**  
**INDUCTION MOTOR**

**CIRCUIT DIAGRAM FOR NO LOAD TEST:**

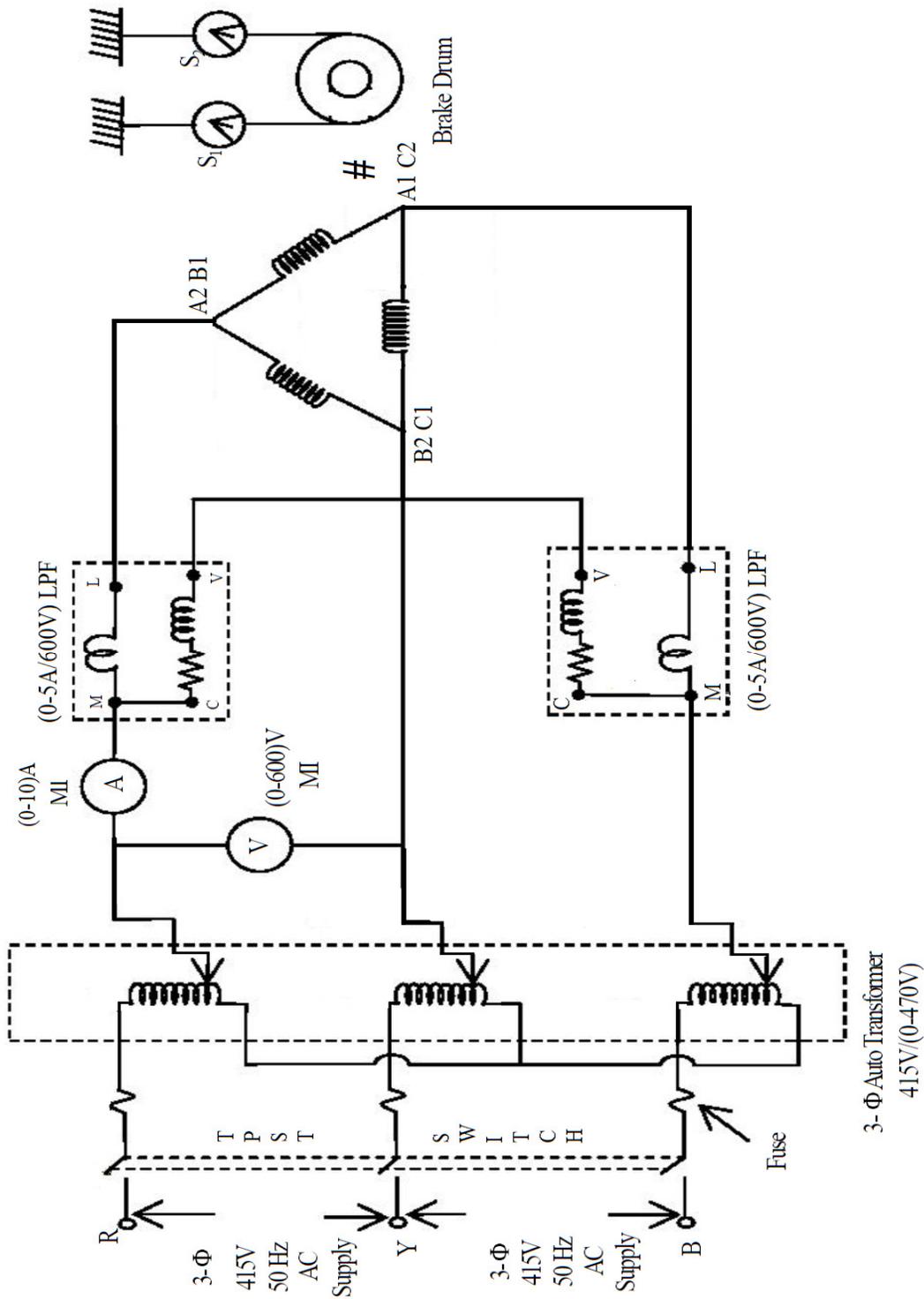

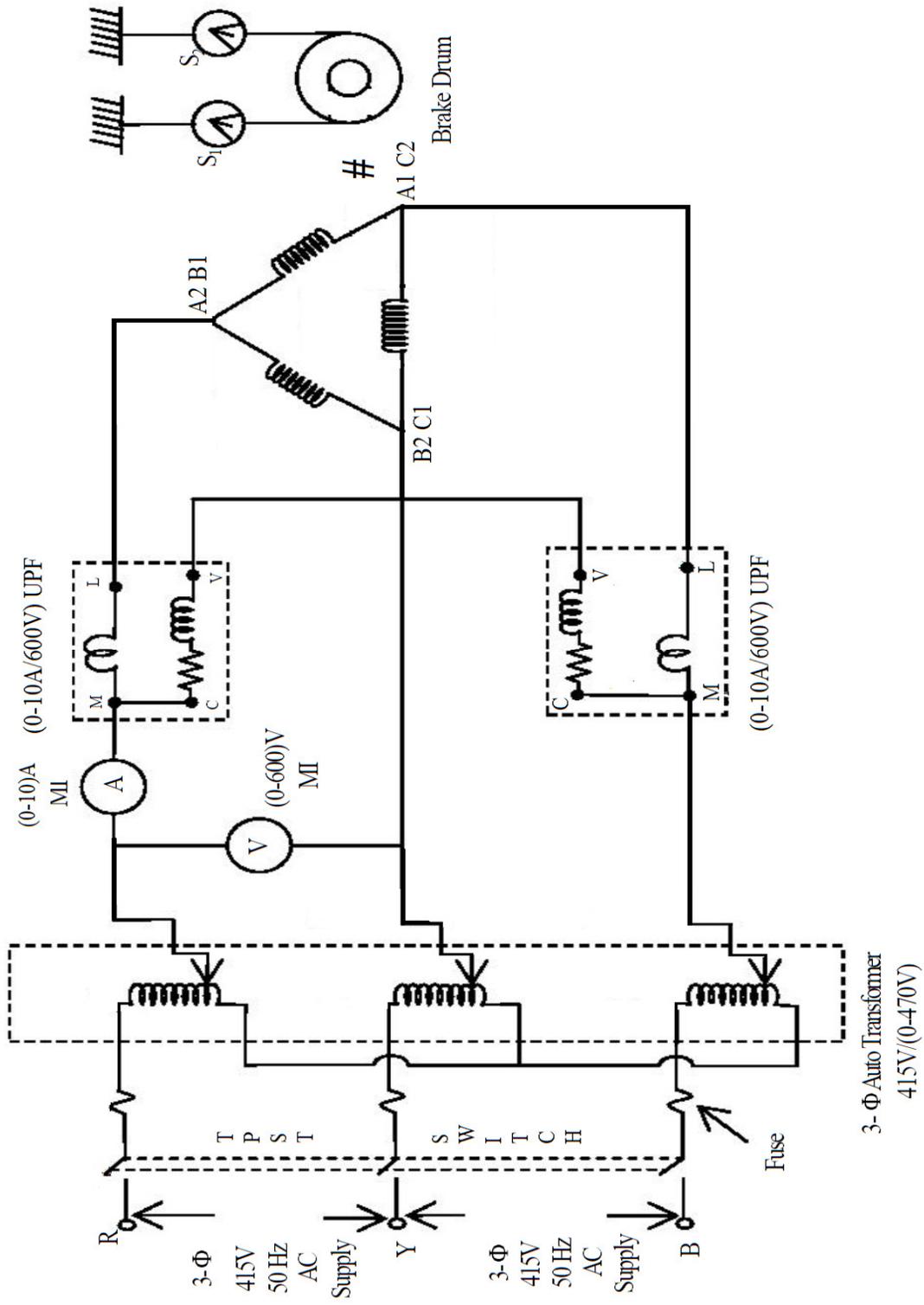**CIRCUIT DIAGRAM FOR BLOCKED ROTOR TEST:**



# NO-LOAD AND BLOCKED ROTOR TEST ON 3-PHASE INDUCTION MOTOR

**AIM:** To draw the equivalent circuit of a 3 phase induction motor and construct the circle diagram by conducting No-load and blocked rotor tests.

## NAME PLATE DETAILS:

3-PHASE INDUCTION MOTOR		
S.No.	NAME	RATINGS
1	Power	
2	Voltage	
3	Current	
4	Phase	
5	Frequency	
6	Speed	

## APPARATUS:

S.No.	NAME OF THE EQUIPMENT	TYPE	RANGE	QUANTITY
1	Voltmeter	MI	0-150V	1
			0-600V	1
2	Ammeter	MI	0-5A	1
3	Wattmeter	-	600V/5A,LPF	2
			150V/10A,UPF	2
4	Tachometer	-	-	1

## **PROCEDURE:**

### **NO LOAD TEST:**

1. Connect the no load circuit as per the circuit diagram.
2. Close the DPST and start the motor with the help of DOL starter.
3. Note the voltage ,no load current, power in wattmeter.
4. Switch off the starter and open the DPST.

### **BLOKED ROTOR TEST:**

1. Connect the blocked rotor circuit as per the circuit diagram.
2. Keep the autotransformer at minimum position and blocked the rotor by lightening the belt over the pulley.
3. Close the DPST and apply the rated current by increasing voltage with the help of autotransformer.
4. Note down the voltage, load current, power in wattmeter.
5. Minimize the auto transformer and open the DPST.

### **MEASUREMENT OF STATOR RESISTANCE**

1. Connect the circuit as per the circuit diagram shown in fig (2).
2. Keeping rheostat in maximum resistance position switch on the 220 V Dc supply.
3. Using volt-ammeter method measure the resistance of the stator winding.
4. After finding the stator resistance,  $R_{dc}$  must be multiplied with 1.6 so as to account for skin effect i.e.  $R_{ac} = 1.6 R_{dc}$ .

## OBSERVATION:

### No load test

S.No.	Voltage(v)	Current( $I_0$ )	POWER( $W_1$ )	POWER( $W_2$ )	Total power $W_0=W_1+W_2$

### Blocked rotor test

S.No.	Voltage( $V_{sc}$ )	Current( $I_{sc}$ )	Power( $W_1$ )	POWER( $W_2$ )	Total power $W_{sc}=W_1+W_2$

## CONSTRUCTION OF CIRCLE DIAGRAM:

1. Draw a line representing the applied voltage per phase  $V_1$ .
2. Draw the no load current  $I_0$  at the no load power factor angle  $(\phi)_0$  with the reference phasor  $V_1$  current scale may be suitably chosen, keeping in mind the short-circuit current at rated voltage.
3. Draw short-circuit or blocked rotor current corresponding to the rated phase voltage at power factor angle  $(\phi)_b$  with the reference phasor  $V_1$ .
4. Join AB, which represents the output line of the rotor.
5. Draw the horizontal line AF and erect a perpendicular bisector on the output line, so  $O^1$  as center and  $AO^1$  as the radius, draw the semi circle ABF.
6. Draw the vertical line from the point B, so as to meet the line AF at the point D. Divide the line BD in the ratio of rotor copper losses to stator copper losses at point E.  
i.e,  $BE/DE = \text{rotor copper losses} / \text{stator copper losses}$

## **CALCULATIONS:**

1.No load power factor= $P_{NL}/\text{square root of } [3V_{BL}I_{NL}]$

2.Blocked rotor power factor= $P_{BL}/\text{square root of } [3V_{BL}I_{BL}]$

### **From no load test**

1.  $G_0=W_0/3V_0^2$

2.  $Y_0=I_0/V_0$

3.  $B_0=\text{square root}[Y_0^2-G_0^2]$

### **From blocked rotor test**

1.  $Z_{01}=V_{SC}/I_{SC}$

2.  $R_{01}=W_{SC}/3I_{SC}^2$

3.  $X_{01}=\text{square root}[Z_{01}^2-R_{01}^2]$

### **For circle diagram**

1.  $\cos(\theta_0)=W_0/\text{square root}[3]V_0I_0=W_{SC}/\text{square root}[3]V_{SC}I_{SC}$

2.  $I_{SN}=I_{SC}*(V_0/V_{SC})$

3.  $W_{SN}=W_{SC}*(V_0/V_{SC})^2$

## **PRECAUTIONS:**

1. Loose connections should be avoided.
2. Operate the instruments carefully.
3. Load currents should not be exceeding beyond their rating.

## **RESULT:**


## QUESTIONS:

1. Explain why the locus of the induction motor current is a circle.
2. What is the difference between the transformer equivalent circuit and induction motor equivalent circuit?
3. What are the reasons in conducting no-load test with rated voltage and blocked-rotor test with rated current?
4. Why do you choose LPF wattmeter in load test and hpf wattmeter in blocked rotor test?
5. How do you reverse the direction of rotation of induction motor?
6. What are the various applications of this motor?
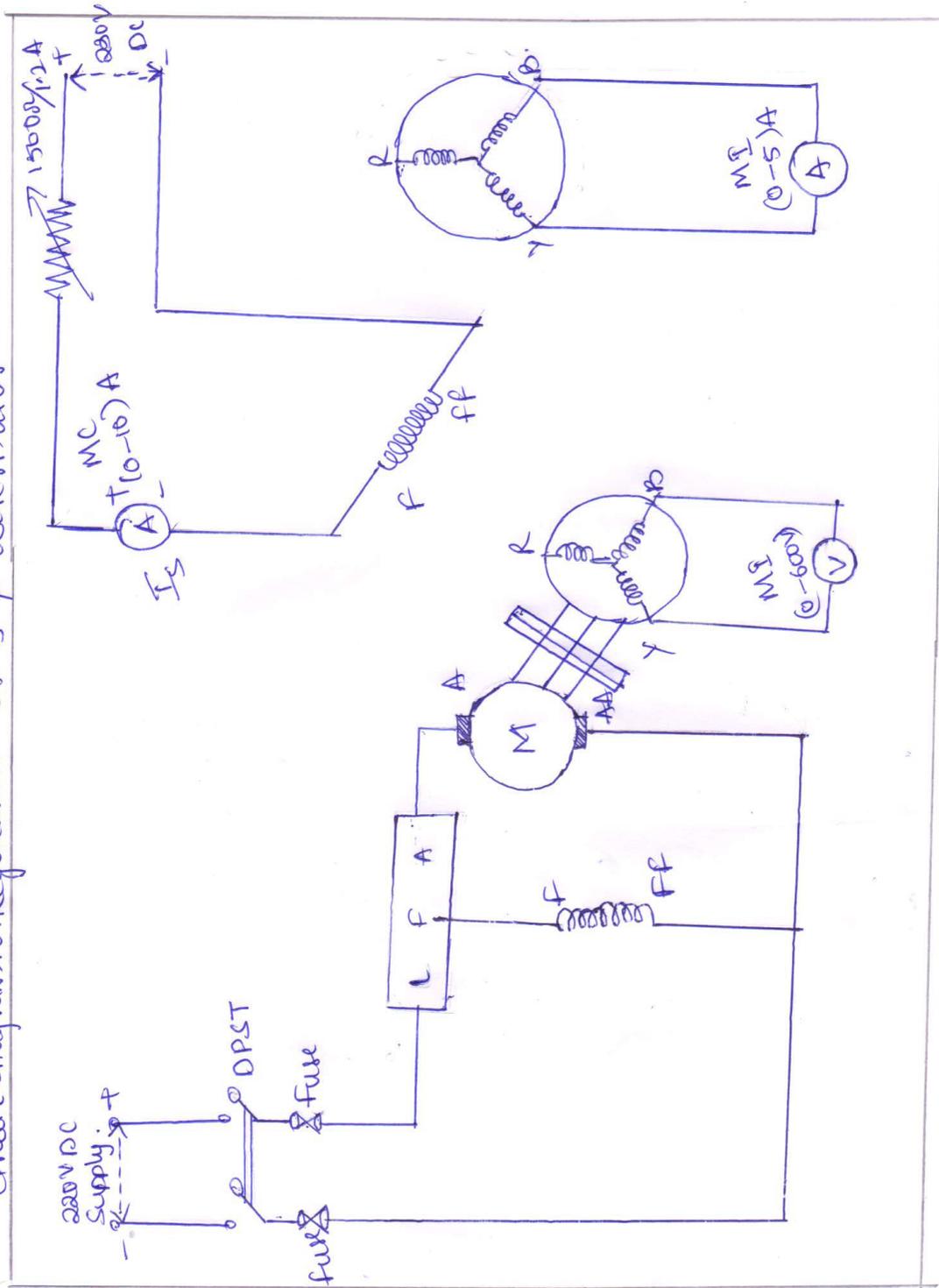
# **EXPERIMENT NO 5**

**REGULATION OF 3-PHASE ALTERNATOR BY SYNCHRONOUS  
IMPEDENCE AND MMF METHOD**

Circuit diagram for Regulation of 3- $\phi$  alternator



## REGULATION OF 3-PHASE ALTERNATOR BY SYNCHRONOUS IMPEDENCE AND MMF METHOD

**AIM:** To predetermine the regulation of an alternator by

- a) Synchronous impedance method and
- b) MMF method

**NAME PLATE DETAILS:**

S.NO.	DC SHUNT MOTOR		3 PHASE ALTERNATOR	
	PARAMETER	UNITS	PARAMETER	UNITS
1				
2				
3				
4				

**APPARATUS REQUIRED:**

S.NO	EQUIPMENT	TYPE	RANGE	QUANTITY
1	Ammeter	MC	(0-25)A	1
2	Ammeter	MI	(0-5)A	1
3	Voltmeter	MI	(0-600)V	1
4	Rheostat	-	-	1
5	Tachometer	Digital	-	1



**PROCEDURE:**

1. Make the connections as per the circuit diagram, start the alternator with the help of prime mover (DC shunt motor) and adjust speed to the synchronous speed. The speed of the alternator is to be kept constant throughout the experiment.
2. Excite the field winding alternator keeping armature open .
3. Note down the terminals voltage at different value of field currents.



## CALCULATIONS:


## MODEL GRAPH:

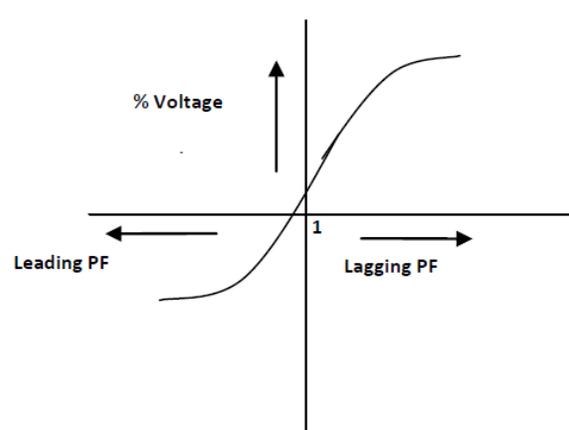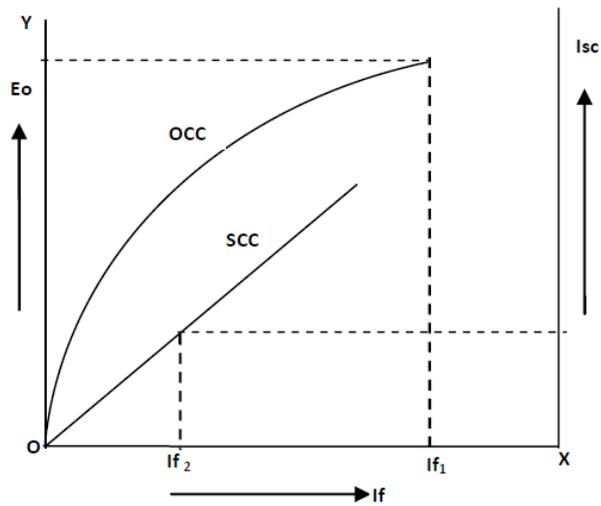
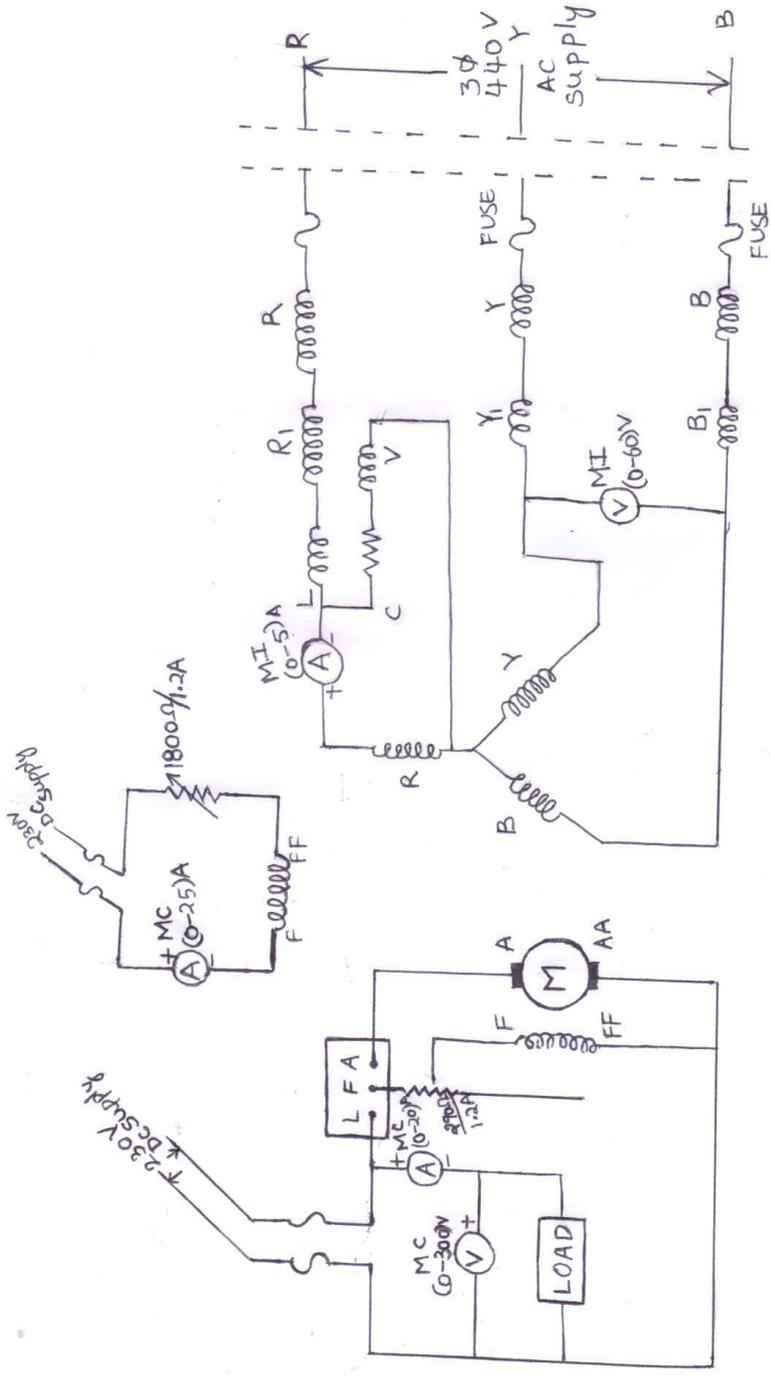
## RESULT:

**EXPERIMENT NO 6**  
**V AND INVERTED V CURVES OF 3-PHASE**  
**SYNCHRONOUS MOTOR**

Circuit diagram for 'V' and Inverted V curves of 3- $\phi$  Synchronous motor.



V AND INVERTED V CURVES OF 3- $\phi$  SYNCHRONOUS MOTOR

## V AND INVERTED V CURVES OF 3-PHASE SYNCHRONOUS MOTOR

**AIM:** To draw the V and inverted V-curves of synchronous motor

### APPARATUS:

S.NO	NAME	RANGE	TYPE	QUANTITY
1	Ammeter	(0-25)A	MI	1
2	Ammeter	(0-20A)/3A	MI	2
3	Voltmeter	(0-600)/300V	MI	3
4	Wattmeter	(0-300)W	MC	1
5	Rheostat	(290 $\Omega$ /12A)	-	1
6	Tachometer	-	Digital	1

### PROCEDURE:

1. Connection are made as per diagram.
2. Ensuring minimum resistance in  $I_f$  of DC supply is switch ON.
3. Using 3-point starter , the rotor is started and brought to rated speed.
4. The alternator is brought to rated voltage.
5. Keeping the synchronous open 3-phase supply to alternator is ON and following observation are made on the synchronous board.
6. The voltage of alternator is adjusted. to supply voltage
7. Speed of alternator is adjusted such that bulbs glow and become dark slow.
8. At constant ,when bulbs has no glow,switch is closed.
9. The supply is supplied to alternator and DC motor this condition is floating condition.
10. DC motor supply is switched OFF ,so that it acts as generator and alternator as motor.
11. The excitation increases then it has leading P.F and if excitation decreases then it has lagging.
12. Without load on generator of value for both lag and lead PF is verified.
13. A graph is plotted between  $I_f/I_a$  and  $P_f$  Vs  $I_f$ .

### PRECAUTIONS:

1. There should not be any load on the motor.
2. Initially the field current should be adjusted to rated value.

3. The direction of the rotation of the rotor should be in proper direction only.
4. If  $I_a$  value is increased more than rated value, then it should be brought to rated value by adjusting the field current.
5. The I/P voltage should be kept constant through out the experiment.
6. After completion of the experiment only 3-phase supply should be disconnected first and then DC supply.

**TABULAR FORM:**  
**FULL LOAD**

$I_f(A)$	$I_a(A)$	POWER(W)	Cos( $\phi$ )



**NO LOAD**

$I_f(A)$	$I_a(A)$	POWER(W)	Cos( $\phi$ )

**FORMULA:**

$$\text{COS}\phi_1 = W_0 / \sqrt{3} V_a I_a$$

**MODEL GRAPH:**

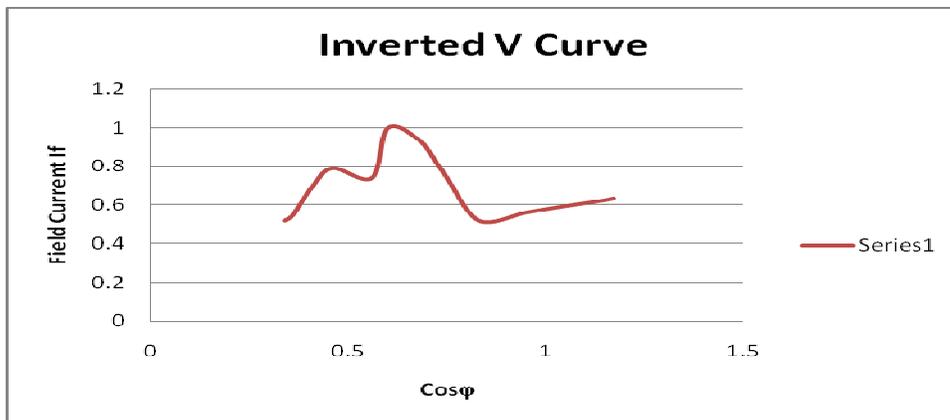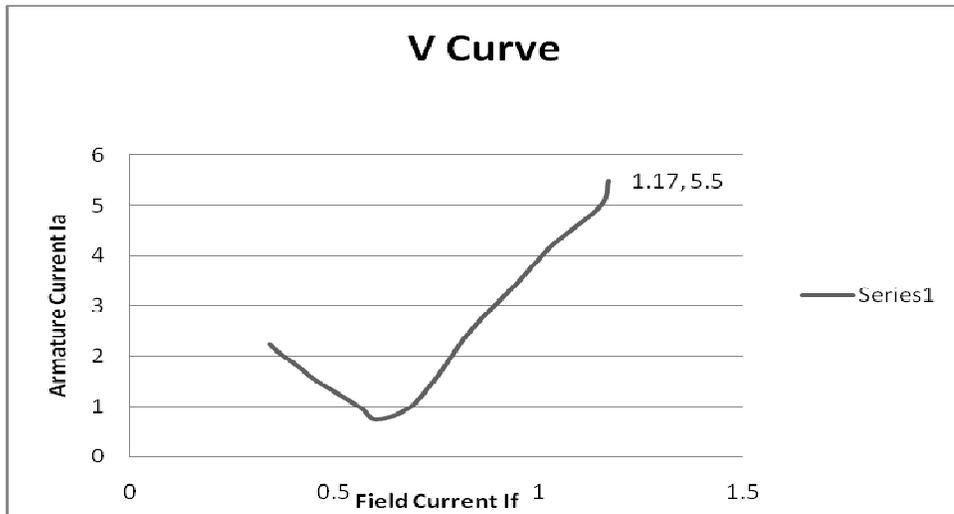


**RESULT:**

## **EXPERIMENT NO 7**

### **EQUIVALENT OF A SINGLE PHASE INDUCTION MOTOR**


# CIRCUIT DIAGRAM FOR NO-LOAD TEST:

## No-Load Test

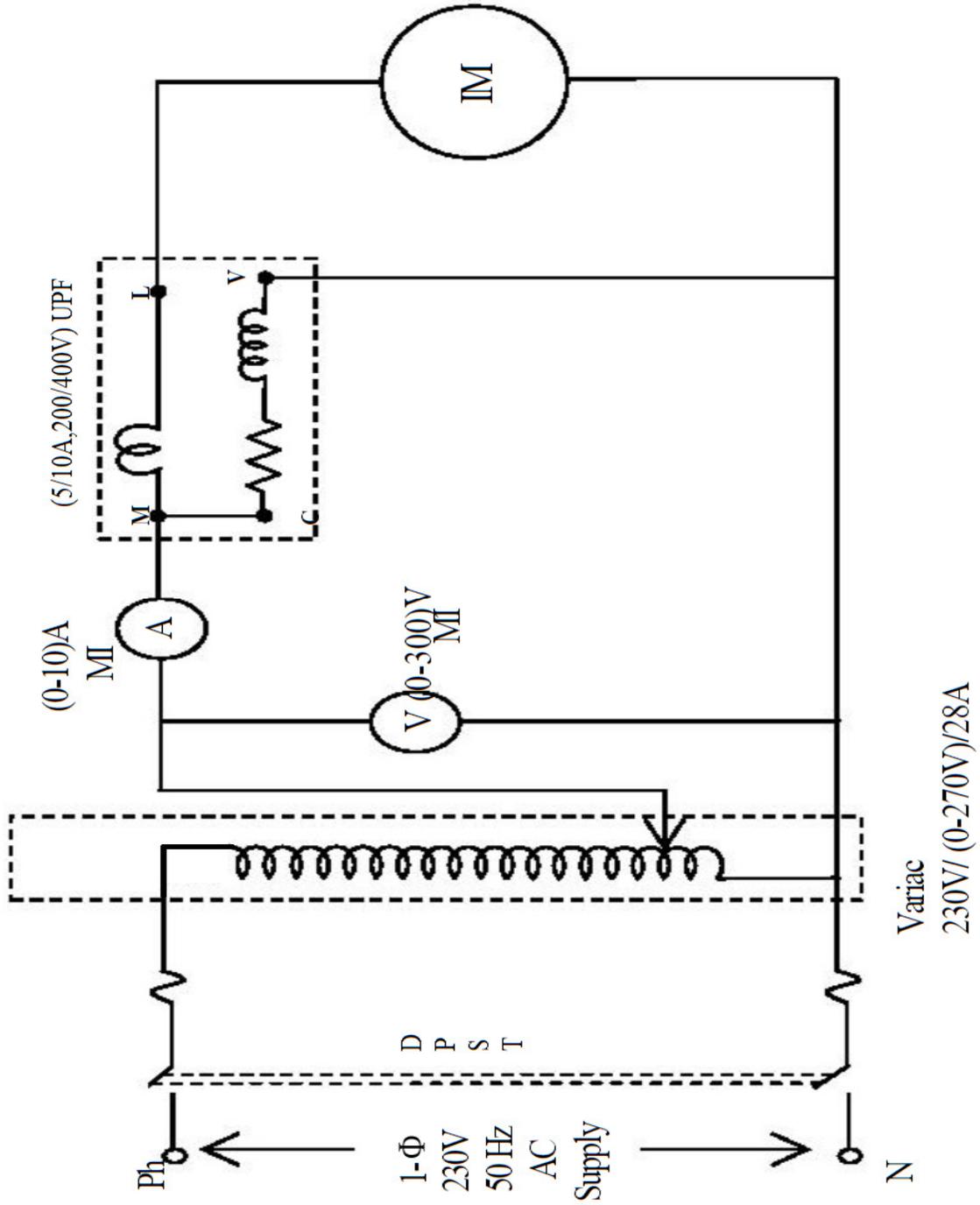

# CIRCUIT DIAGRAM FOR BLOCKED ROTOR TEST:

## Blocked Rotor Test

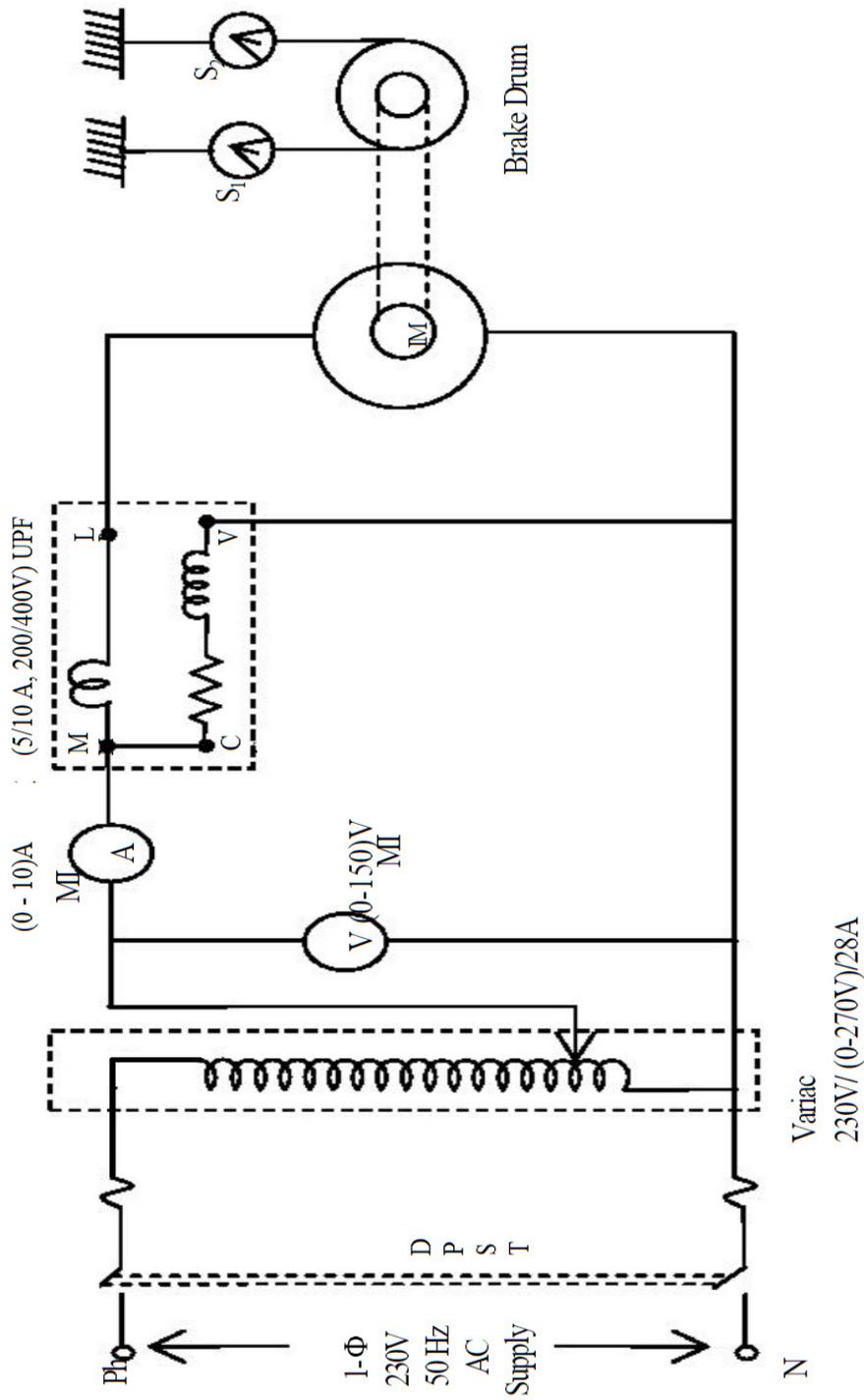

# EQUIVALENT OF A SINGLE PHASE INDUCTION MOTOR

**AIM :** To conduct OC & SC tests on the given 1-Induction motor and to determine its equivalent circuit parameters.

## NAME PLATE DETAILS :

1 $\Phi$ - INDUCTION MOTOR		
S.NO.	NAME	RATING
1	Power	
2	Voltage	
3	Current	
4	Phase	
5	Frequency	
6	Speed	

## APPARATUS REQUIRED :

S.NO.	NAME	TYPE	RANGE	QUANTITY
1.	Voltmeter	MI	0-300V	1
2.	Ammeter	MI	0-10A	1
3.	Wattmeter	MI	300V ,5A UPF	1
		MI	150V ,10A LPF	1

## PROCEDURE :

### NO LOAD TEST:

- 1.Connect the no load circuit as per the circuit diagram.
- 2.Close the DPST & Start the motor with the help of DOL starter without load.
- 3.Note down the No load voltage , No load current and Power .
- 4.Switch off the starter and open the DPST.

### **BLOCKED MOTOR TEST:**

1. Connect the blocked motor circuit as per the circuit diagram.
2. Keep the auto transformer at minimum position and blocked the motor.
3. Close the DPST & Apply the rated current by increasing voltage.
4. Note down the voltage, load current, power.
5. Minimize the auto transformer & open the DPST.

### **CALCULATIONS :**

#### **NO LOAD TEST:**

1. Iron losses ( $W_0$ ) =  $[V_0 I_0 \cos(\phi)]$  watts
2.  $\cos(\phi) = W_0 / (V_0 I_0)$
3. Iron component =  $I_w = I_0 \cos(\phi)$  Amp
4. Magnetizing current  $I_m = I_0 \sin(\phi)$  Amp
5. Loss component  $R_0 = (V_0 / I_0)$  Ohms
6. Magnetizing reactance  $X_m = (V_0 / I_m)$  Ohms

#### **BLOCKED MOTOR TEST:**

1. Equivalent impedance  $Z_{Eq} = (V_{SC} / I_{SC})$  Ohms
2. Total resistance  $R_{eq} = (W_{SC} / I_{SC}^2)$  Ohms
3. Leakage reactance  $X_{eq} = \text{square root of } (Z_{eq}^2 - R_{eq}^2)$

#### **PRECAUTIONS :**

- 1) The Dimmerstat should be kept at minimum O/P position initially.
- 2) In the rotor-blocked test, the rotor should be blocked firmly.
- 3) In SC test, the Dimmerstat should be varied slowly such that current should not exceed the rated value.
- 4) If the wattmeter shows negative deflection, then reverse either pressure coil or current coil & take that reading as negative.
- 5) Loose connections should be avoided.
- 6) Load current should not be exceeding their rating.

## OBSERVATIONS :

S.No.	NO LOAD TEST			BLOCKED MOTOR TEST		
	V <sub>0</sub> (V)	I <sub>0</sub> (A)	W <sub>0</sub> (W)	V <sub>sc</sub> (V)	I <sub>sc</sub> (A)	W <sub>sc</sub> (W)

## OBSERVATIONS:

### O.C.Test:

V <sub>0</sub>	I <sub>0</sub>	W <sub>0</sub>
220	5.56	30x8=240

### S.C. Test:

V <sub>sc</sub>	I <sub>sc</sub>	W <sub>sc</sub>
30	8.18	20X8=160

## MODEL CALCULATIONS:

### (A) No-load Test:

$$\text{Power factor } \cos\phi = \frac{W_0}{V_0 I_0} =$$

$$\sin\phi =$$

$$\text{Reactive component } I_c = I_0 \cos\phi$$

=

$$\text{Magnetizing Component } I_m = I_0 \sin\phi$$

=

$$R_0 = \frac{V_0}{I_c} =$$

$$X_0 = \frac{V_0}{I_m} =$$

$$R_{01} = R_{dc} \times 1.3$$

$$=R_0 \times 1.3$$

=

### Blocked Rotor Test:

$$\text{Power factor } \cos\phi = \frac{W_{sc}}{V_{sc} I_{sc}} =$$

$$\sin\phi = 0.7583$$

$$R_{1e} = \frac{W_{sc}}{(I_{sc})^2} =$$

$$Z_{1e} = \frac{V_{sc}}{I_{sc}} =$$

$$X_{1e} = \sqrt{Z_{1e}^2 - R_{1e}^2}$$

=

=

$$X_1 = X_2' = \frac{X_{1e}}{2}$$

=

$$R_2' = R_{1e} - R_1 \quad [\text{Where } R_1 = 1.1 \text{ to } 1.3]$$

=

$$X_{2f} = X_{2b} = \frac{1}{2} X_2'$$

=

=


$$R_{2r} = R_{2b} = \frac{1}{2} R_2'$$

=

$$X_m/2 = V_o/I_o \sin\phi = [X_1 + \frac{1}{2} X_2']$$

=

**EQUIVALENT CIRCUIT:**

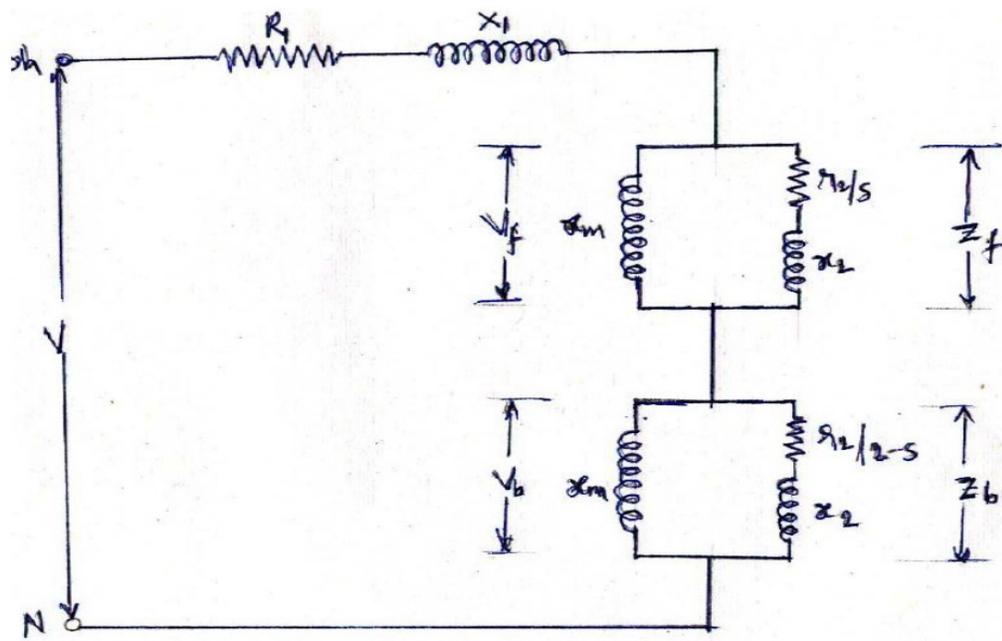


**RESULT:**

## **EXPERIMENT NO 8**
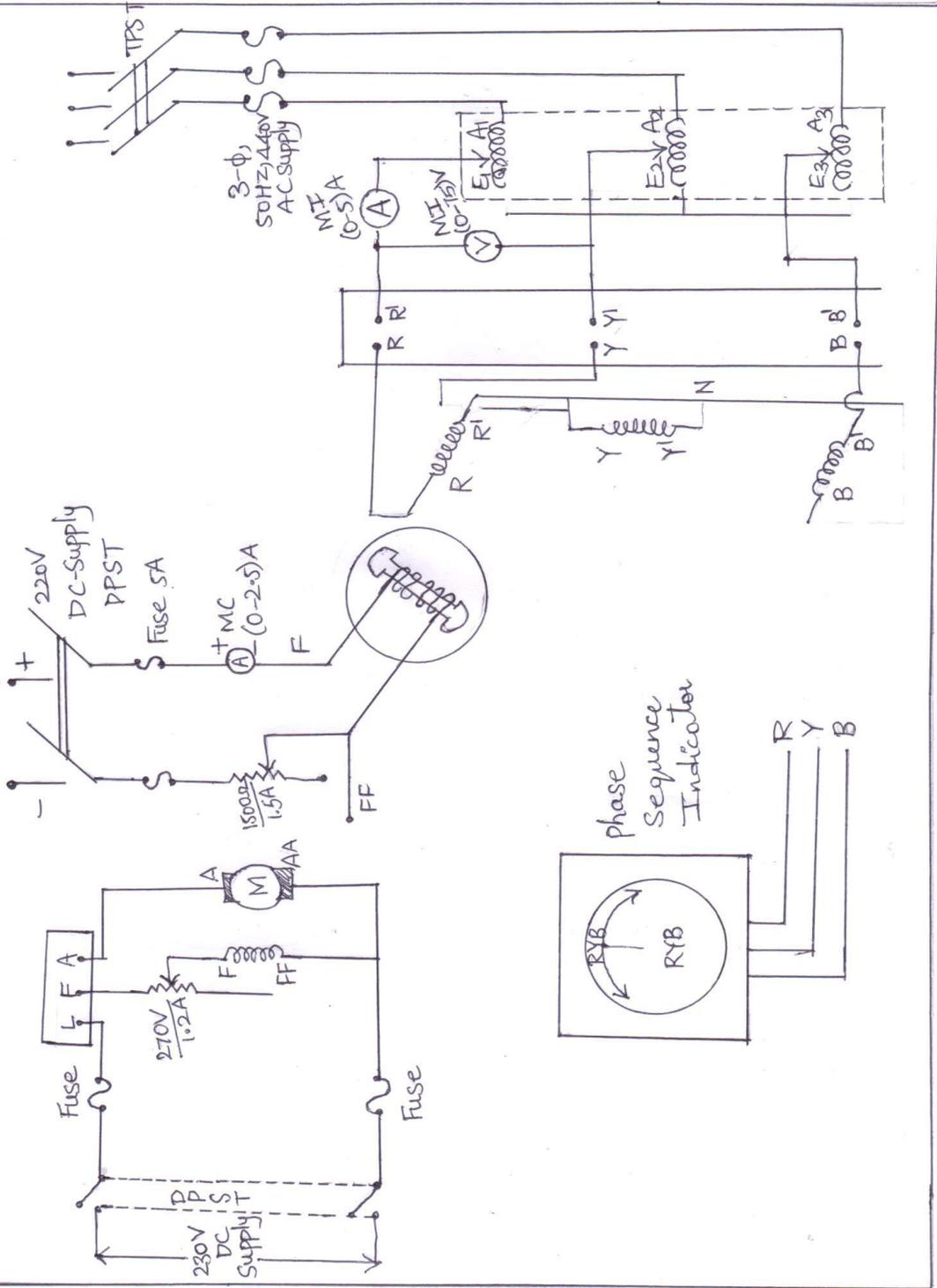
### **DETERMINATION OF $X_d$ AND $X_q$ OF SALIENT POLE SYNCHRONOUS MACHINE**

CIRCUIT FOR DETERMINATION OF  $X_a$ ,  $\xi$ ,  $X_g$  OF SALIENT POLE SYNCHRONOUS MACHINE



## DETERMINATION OF $X_d$ AND $X_q$ OF SALIENT POLE SYNCHRONOUS MACHINE

**AIM:** To determine  $X_d$  and  $X_q$  of salient pole type of synchronous machine

### NAMEPLATE DETAILS:

S.No.	DESCRIPTION	D.C. SHUNT MOTOR	3- $\phi$ ALTERNATOR
1	Capacity		
2	Voltage		
3	Current		
4	Speed		
5	Frequency		

### APPARATUS REQUIRED:

S.No.	NAME	TYPE	RANGE	QUANTITY
1	Ammeter	MC	(0-25)A	1
2	Ammeter	MI	(0-7.5)A,(0-2.5)A	2
3	Voltmeter	-		1
4	Rheostat	-	-	1
5	Tachometer	-	-	1
6	3- $\phi$ variac	-	(0-600)V , 290 $\Omega$ /1.2A	1
7	3- $\phi$ alternator with prime mover	Salient	3.3KVA/415V/1500RPM	1

**PROCEDURE:**

1. Make connections as per the circuit diagram
2. Run the alternator through DC motor at near synchronous speed, keeping AC supply OFF
3. Note down field winding is to be kept open through out.
4. Keeping the variac output voltage at minimum connect the AC supply to variac.
5. Increase the variac output voltage so that a reasonable current passes through the armature .
6. If directions of rotation of rotor and stator fields are same then a slight adjustment of speed causes significant oscillation of armature current
7. When ammeter shows below wide oscillations note  $I_{\max}$  and  $I_{\min}$  and corresponding voltages  $V_{\min}$  and  $V_{\max}$  and calculate  $X_d$  &  $X_q$
8. Using  $x_d$  &  $x_q$  the regulation of silent pole alternator at specified load condition can be determined using appropriate phasor diagram .

**PRECAUTIONS:**

- 1) Check the phase sequence of the machine with that of external supply before closing the switches.
- 2) Disconnect the excitation supply of the alternator while giving external supply.
- 3) Slip should be made as small as possible.

**TABULAR FORM:**

S.No.	$V_{ph \min}$	$V_{ph \max}$	$I_{\min}$	$I_{\max}$	$X_d(\Omega)$	$X_q(\Omega)$

**CALCULATIONS:**


$$X_d = (\text{max volts per phase}/\text{max current per phase})=(V_{\max}/I_{\min})$$

$$X_q = (\text{min volts per phase}/\text{min current per phase})=(V_{\min}/I_{\max})$$

**RESULT:**

## **EXPERIMENT NO 9**
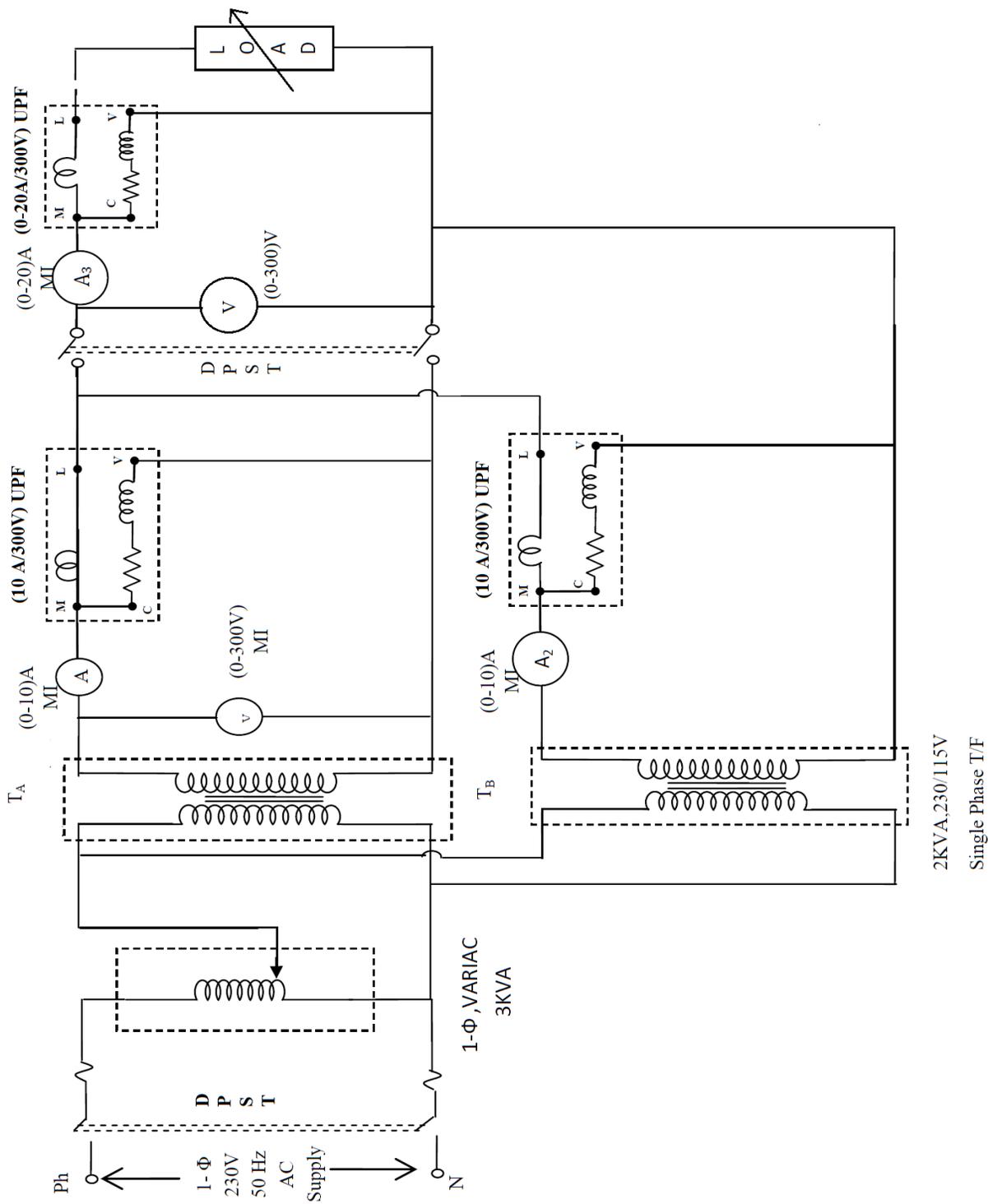
### **PARALLEL OPERATION OF SINGLE PHSE TRANSFORMERS**



2KVA, 230/115V  
 Single Phase T/F

## PARALLEL OPERATION OF SINGLE PHSE TRANSFORMERS

**AIM :** To operate the given two 3KVA, 230/110V single phase Transformers in parallel and study the load sharing between them when supplying resistive load .

### NAME PLATE DETAILS :

TWO 1-Φ TRANSFORMERS		
S.No.	NAME	RATING
1	Power	3KVA
2	No. of phases	1-PHASE
3	Voltage	230V
4	Frequency	50 Hz
5	Taps on HV	100% ,86.6% 50% ,25%

### APPARATUS :

S.NO.	NAME	TYPE	RANGE	QUANTITY
1.	1-phase transformer	-	3KVA ,230/110V	2
2.	Voltmeter	MI	0-600V , 0-300V	1 1
3.	Ammeter	MI	0-30A , 0-15A	1 1
4.	Resistive Load	-	0-150V/300V 230V ,20A	2

### PROCEDURE :

- 1.Connect the circuit as per the circuit diagram.
- 2.Keep the variac at minimum voltage position &switch on the supply.
- 3.Apply the small voltage & measure the voltage on LV & HV side.
- 4.Increase the load in steps & repeat.
- 5.Note the readings.

## OBSERVATION TABLE

S.NO.	VOLTAGE	LOAD	I <sub>T1</sub> (Amp)	I <sub>T2</sub> (Amp)	I <sub>L</sub> (Amp)
1					
2					
3					
4					
5					

### FORMULA :

$$I_L = I_{T1} + I_{T2}$$

### CALCULATIONS:

### PRECAUTIONS :


- 1.The transformers must have same voltage ratio.
- 2.The transformers must be connected with correct polarities.
3. Load current should not exceed beyond rating.

### RESULT :

**EXPERIMENT NO 10**

**BRAKE TEST ON 3-PHASE INDUCTION MOTOR**

**CIRCUIT DIAGRAM :**

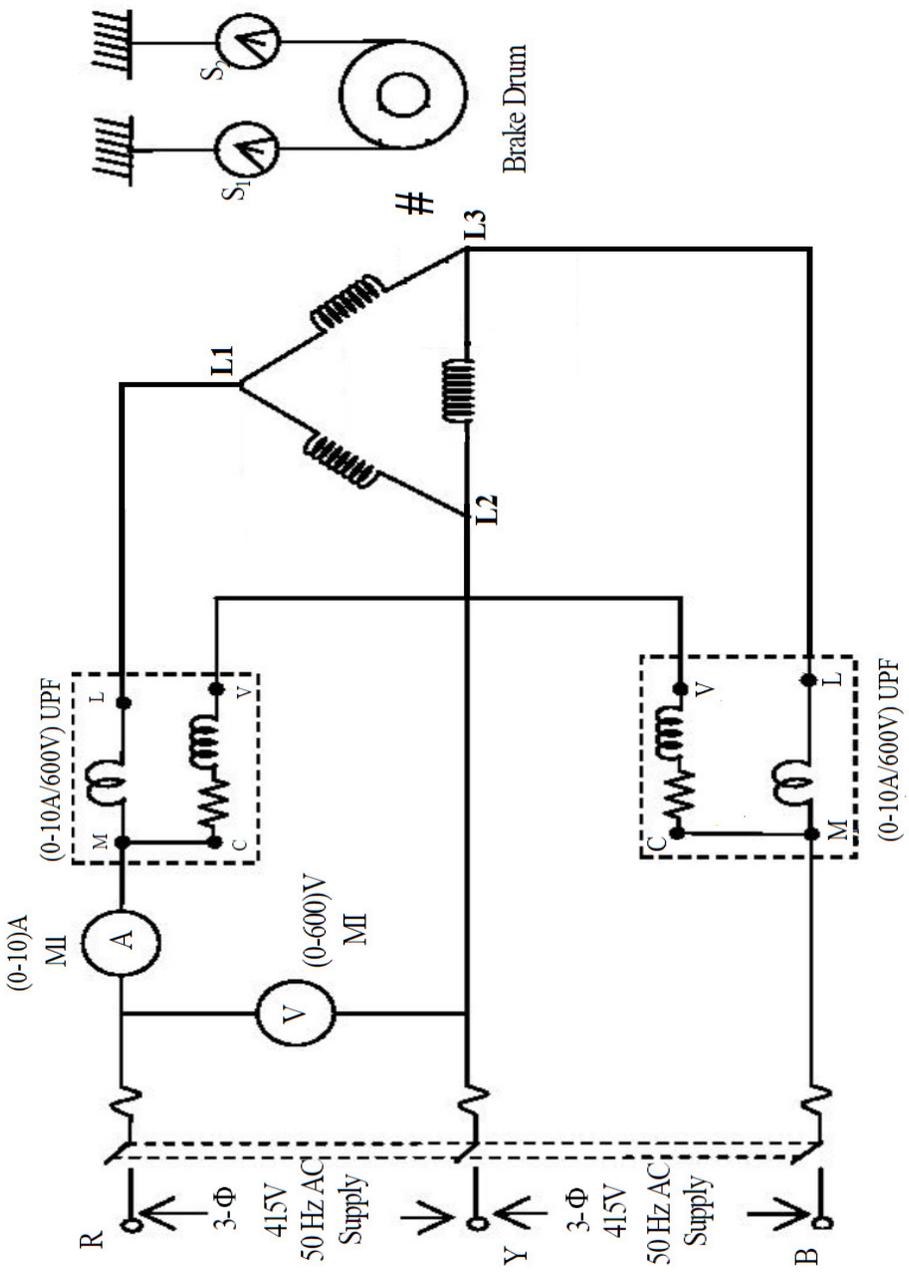

## BRAKE TEST ON 3-PHASE INDUCTION MOTOR

**AIM:** To perform the brake test on 3-phase slip ring induction motor and obtain its performance characteristics.

### APPARATUS REQUIRED:

S.NO	NAME	TYPE	RANGE	QUANTITY
1.	Wattmeter	UPF	(0-10)A/600V	1No.
2.	Ammeter	MC	(0-10)A	1No.
3.	Voltmeter	MI	(0-600)V	1No.
4.	Tachometer	Digital	(0-1500)rpm	1No.

### NAME PLATE DETAILS:

3-PHASE INDUCTION MOTOR		
S.NO	NAME	RANGE
1.	Voltage	
2.	Rated current	
3.	Rated power	
4.	Rated speed	

### PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Start the 3-phase induction motor on no load by means of 3-phase auto transformer.
3. Note down the meter readings and the speed at no load.
4. Apply brake by tightening the best of brake drum and note down the readings of the meter spring balance and speed.
5. Repeat the above step-4 until motor draws F-L current
6. Calculate torque slip power factor for each readings.
7. Draw the performance curves of output vs efficiency, torque, speed,  $I_a$ , Power factor on graph sheet.

### OBSERVATION TABULAR FORM:

S.No.	V <sub>L</sub>	I <sub>L</sub>	W <sub>1</sub>	W <sub>2</sub>	S <sub>1</sub>	S <sub>2</sub>	N	T	%S	O/P	I/P	EFFICIENCY

Where  $T = (S_1 - S_2) \cdot R + 9.81$     $O/P = 2\pi N T / 60$     $Slip = (N_s - N) / N_s$

### CALCULATIONS:

1. Power i/p = wattmeter readings x multiplying factor

2. Torque  $\tau = w \times g \times r$  N-m

(Where  $r$  is the radius of the brake drum power o/p)

3. O/p Power =  $2\pi N T / 60$  Watts

$$\% = (N_s - N) / N_s \times 100$$


4.  $\cos \Phi = R / \sqrt{3} V_L I_L$

### PRECAUTIONS:

1. There shouldn't be any load on motor initially.
2. The brake drum should be filled with water to cool it.
3. If wattmeter shows negative deflection reverse either pc or CC and take that readings are negative.
4. The rotor external resistance should be kept at maximum Position.

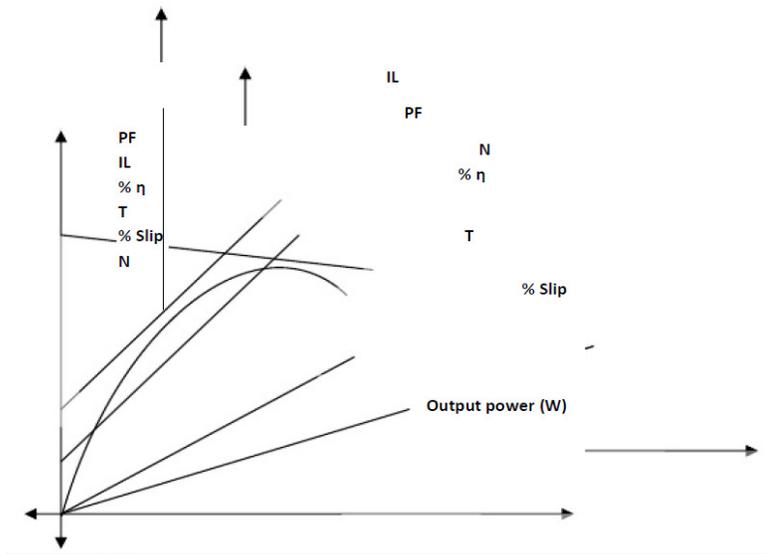**MODEL GRAPH:**

A graph is drawn b/w output power, speed, torque, current, slip and efficiency.




**RESULT:**

# **EXPERIMENT NO 11**

**REGULATION OF 3-PHASE ALTERNATOR BY ZPF AND ASA METHODS**

CIRCUIT DIAGRAM

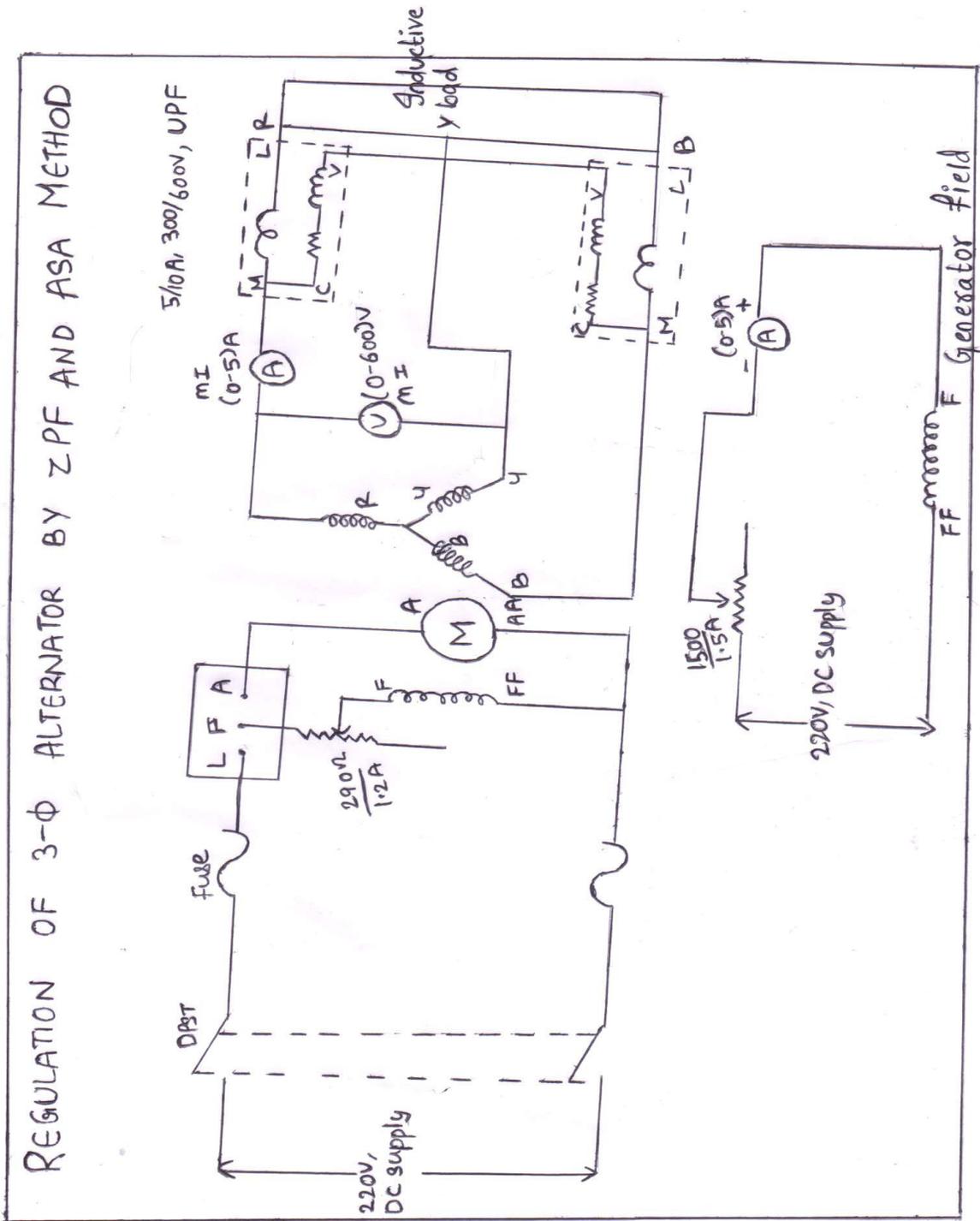

# REGULATION OF 3-PHASE ALTERNATOR BY ZPF AND ASA METHODS

**AIM :** To determine the regulation of a 3-phase alternator by ZPF and ASA method.

## NAME PLATE DETAILS:

S.NO.	MOTOR		3 PHASE ALTERNATOR	
	PARAMETER	RATINGS	PARAMETER	RATINGS
1	RATED POWER			
2	RATED VOLTAGE			
3	RATED CURRENT			
4	RATED SPEED			

## APPARATUS REQUIRED:

S.NO.	EQUIPMENT	TYPE	RANGE	QUANTITY
1	3-Phase alternator	-	-	1
2	Ammeter	MC	(0-15)A	1
3	Ammeter	MI	(0-5)A	1
4	Voltmeter	MI	(0-600)V	1
5	Tachometer	Digital	-	1

**PRECAUTION:**

1. The motor field rheostat should be kept in the minimum resistance position.
2. The Alternator field potential divider should be in the position of minimum potential.
3. Initially all switches are in open position.

**PROCEDURE FOR BOTH POTIER AND ASA METHODS:**


1. Note down the complete nameplate details of motor and alternator.
2. Connections are made as per the circuit diagram.
3. Switch on the supply by closing the DPST main switch.
4. Using the Three point starter, start the motor to run at the synchronous speed by varying the motor field rheostat.
5. Conduct an Open Circuit Test by varying the Potential Divider for various values of Field current and tabulate the corresponding Open circuit voltage readings.
6. Conduct a Short Circuit Test by closing the TPST knife switch and adjust the potential divider the set the rated Armature current, tabulate the corresponding Field current.
7. Conduct a ZPF test by adjusting the potential divider for full load current passing through either an inductive or capacitive load with zero power and tabulate the readings.
8. Conduct a Stator Resistance Test by giving connection as per the circuit diagram and tabulate the voltage and Current readings for various resistive loads.

**RESULT:**

## **EXPERIMENT NO 12**

### **LOAD TEST ON THREE PHASE ALTERNATOR**

# CIRCUIT DIAGRAM

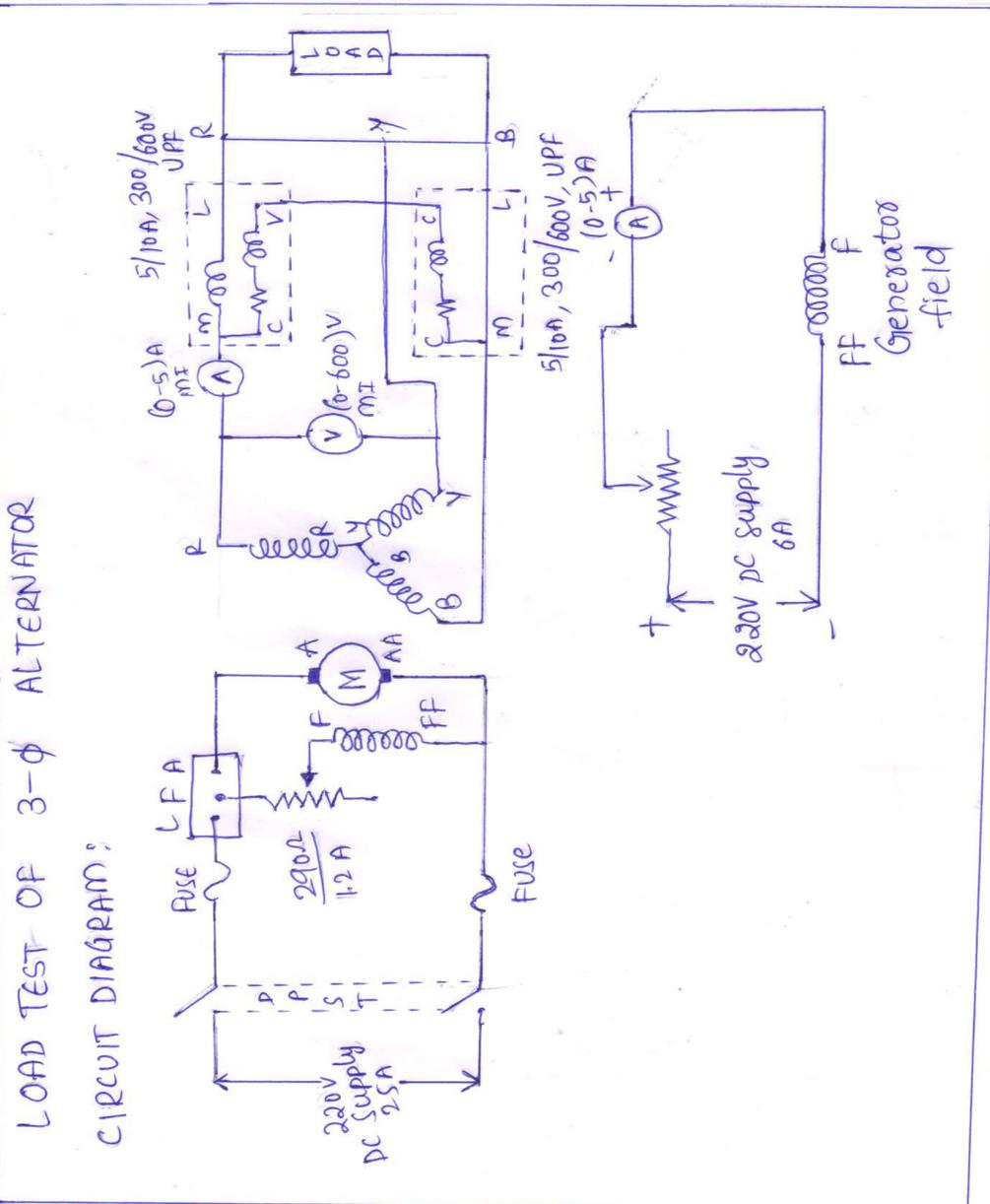

## LOAD TEST ON OF 3-PHASE ALTERNATOR

**AIM:** To determine the efficiency of a 3-phase alternator.

### NAME PLATE DETAILS:

S.NO.	MOTOR		3 PHASE ALTERNATOR	
	PARAMETER	UNITS	PARAMETER	UNITS
1				
2				
3				
4				

### APPARATUS REQUIRED:

S.NO	EQUIPMENT	TYPE	RANGE	QUANTITY
	3-Phase alternator	-	-	1
1	Ammeter	MC	(0-1.5A/3A)	1
3	Voltmeter	MC	(0-600)V	1
4	Wattmeter	-	(0-5)A/600V	1
5	Tachometer	Digital	-	1

### PROCEDURE:

1. Connect the circuit as per the circuit diagram.
2. Ensure that motor field Rheostat is minimum and alternator field rheostat is maximum
3. Start the motor as with the help of starter and by adjusting motor field rheostat if rated speed synchronous speed of machine.



**CALCULATION TABULAR FORM:**

<b>S.NO.</b>	<b>INPUT POWER</b>	<b>OUTPUT POWER</b>	<b>EFFICIENCY</b>

**RESULT:**